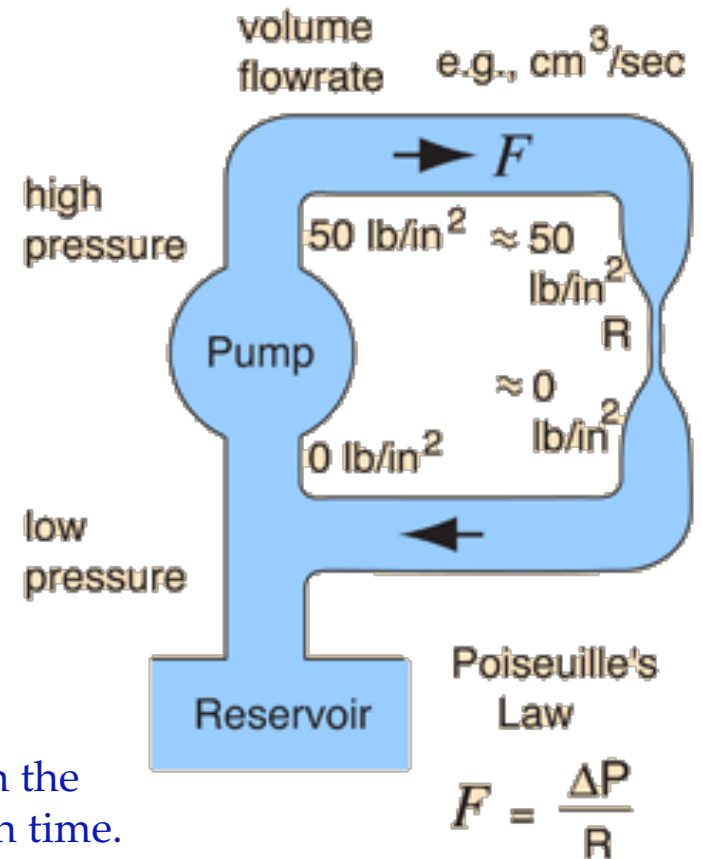


Electrostatics vs. Circuits

- Thus far, we've focused on electrostatics and electric fields and potentials: the behavior of individual charges, stationary or in an electric field, and the principles behind those behaviors
- We have not yet talked about electric **current**, or the behavior of charges in **circuits**
- The best way to begin thinking about electrical current in circuits is by thinking about water in a pipe system...like this...

Water circuit analogy

- Consider the picture to the right.
 - What is flowing through the pipes?
Water (duh)
 - What causes it to flow?
The pump, which provides high pressure to force water to move.
 - Which way does it flow?
From the high pressure side to the low pressure side, around the pipe circuit.
 - What controls how much flows?
The available space in the pipes - the narrow part on the right side limits how much water can flow in a given time.
 - How do we measure how much flows?
A flow rate - for water, a "volume" flow rate. How much water per second -- NOT a velocity!



Now a circuit

□ Same questions for this picture:

- What is flowing through the circuit?

Something in the wires - charge!
(is it positive charge? Negative charge? Why?)

- What causes it to flow?

The battery, which acts like a pump.

- Which way does it flow?


From the high potential energy side to the low potential energy side. (Does that change your answer to #1? How does it relate to #1?)

- What controls how much flows?


How difficult the path to flow through is - what do you think "R" means in the diagram?

- How do we measure how much flows?

A flow rate - **current!**

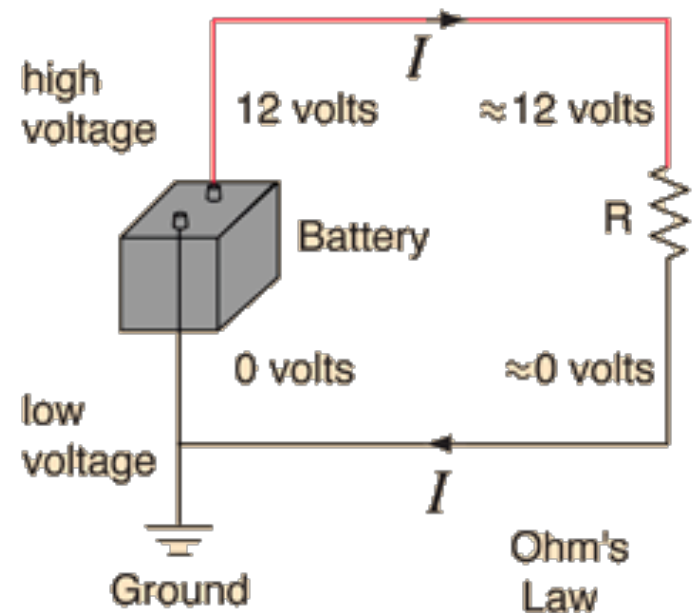

Water vs. electricity

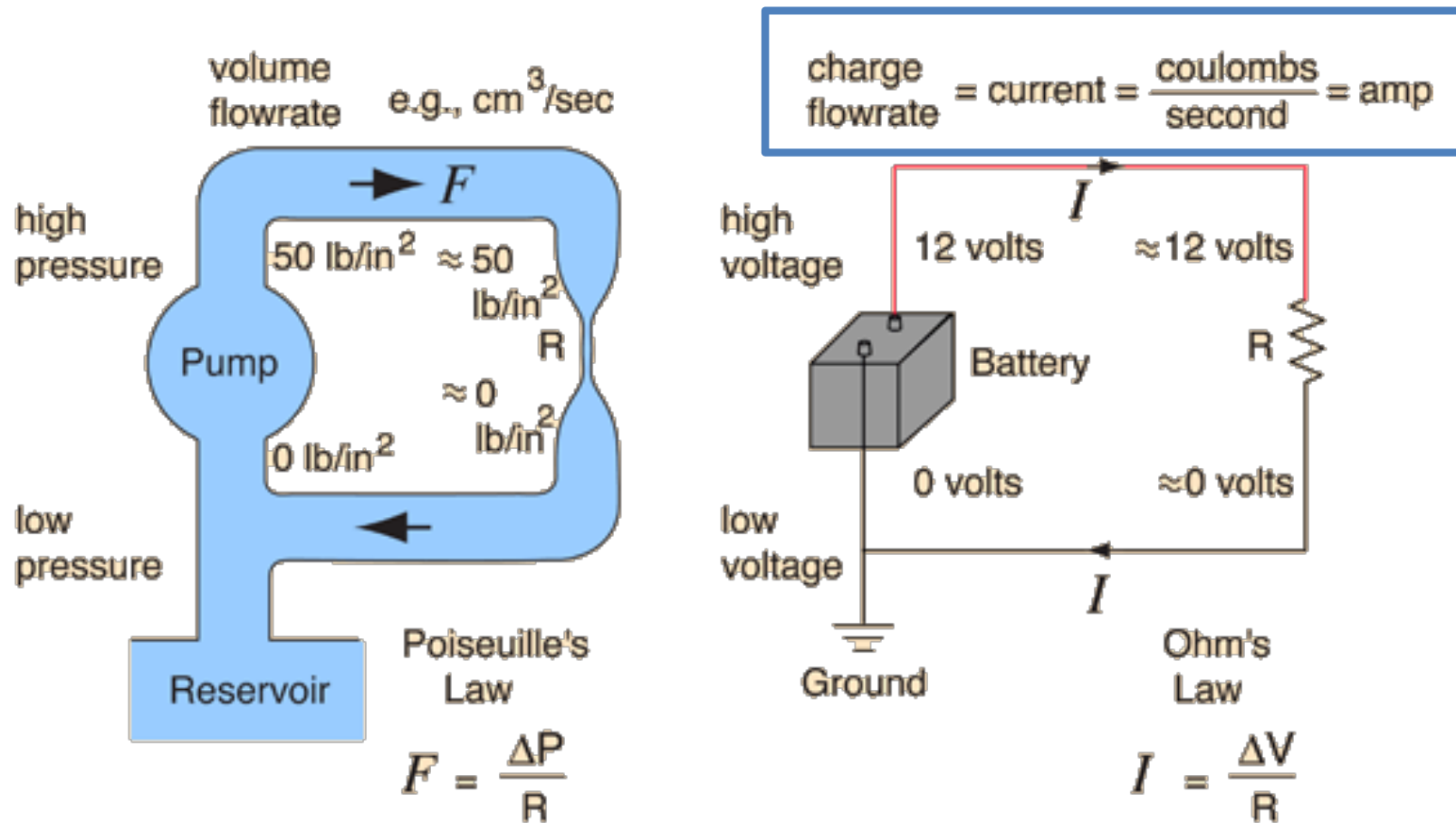

Note: as we continue through this unit, we will point out ways in which this analogy is both good and bad. Remember that charge is not water, and there are some big differences we will explore!

Charge flow rate


- We talk about the “charge flow rate” in a circuit in terms of amount of charge per second -- this is called **current**
 - This is not a speed! It’s how much, not how fast, per second.
 - Current (symbol: I) is measured in Amperes (A), where 1 A = 1 C/second

$$I = \frac{\Delta Q}{\Delta t}$$


- What could affect the amount of current in a circuit?
 - Battery (big vs. small voltage)
 - Wire properties (e.g. thicker wire, more conductive wire)
 - Circuit properties (e.g. resistors!)
- For a current to flow, we need:
 - A closed loop of conductors (this is what we mean by ”circuit”)
 - A potential difference (aka voltage, produced by the battery)

Basic battery


- An electric battery consists of an anode (negative node) and a cathode (positive node) which are both immersed in an electrolytic solution like an acid or a base. The nodes are usually called terminals.
- The solution oxidizes the cathode and reduces the anode, resulting in opposite charges, and thus a potential difference, between the nodes.
- **Here's the key!**
 - If the nodes aren't connected, the voltage doesn't change - it stores this potential energy
 - If the nodes are connected, charge flows due to the potential difference
 - As long as the oxidation/reduction reactions continue, the battery will maintain its voltage

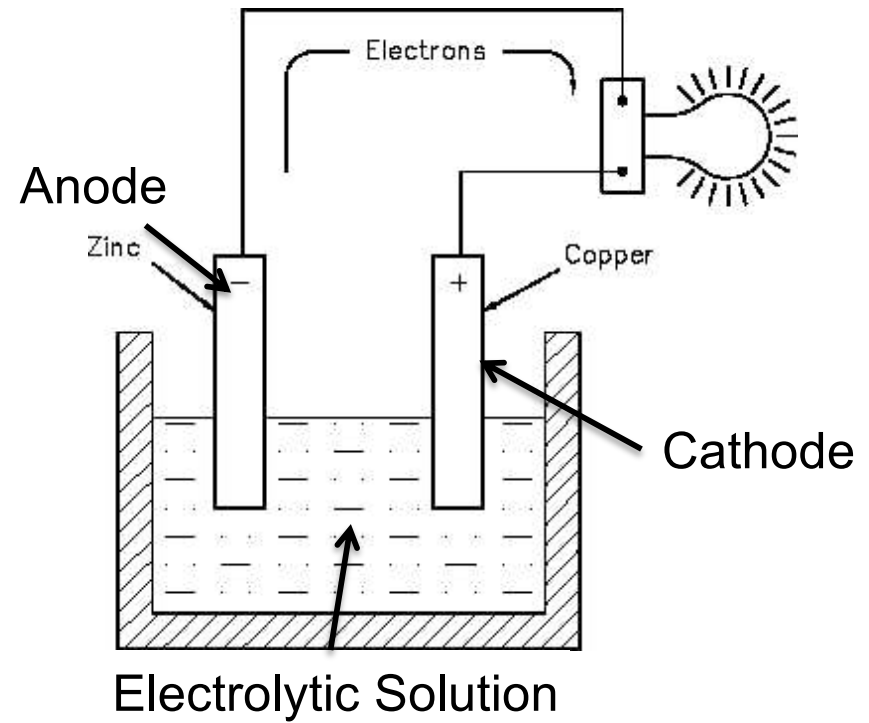

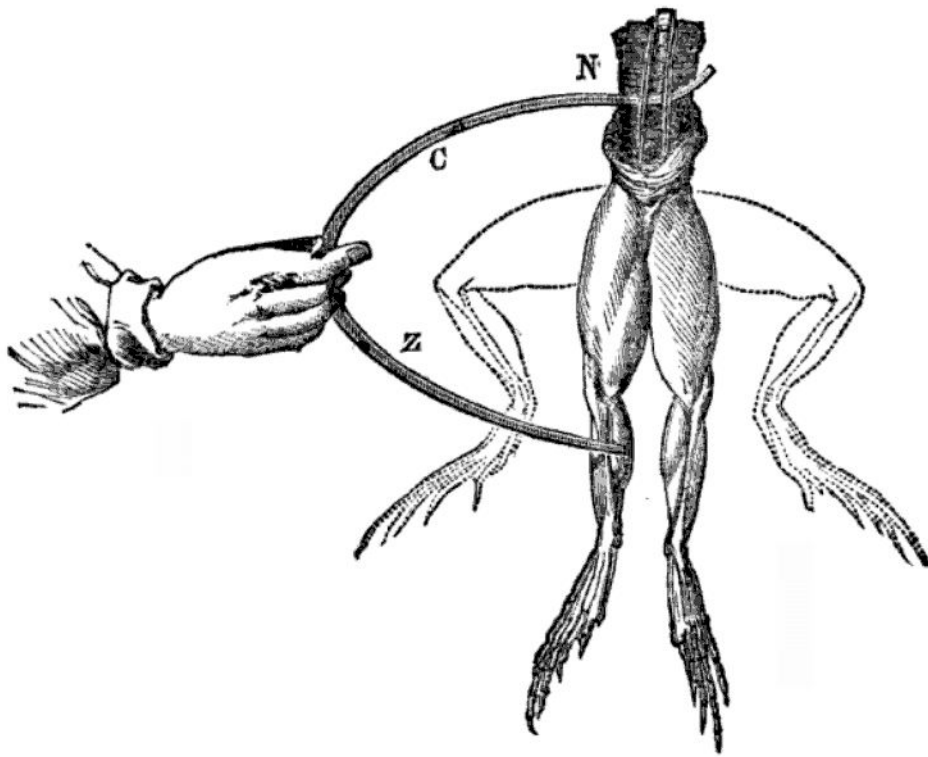Early batteries - Galvani vs. Volta (1780s)



Cloth or paper soaked in salt or acid.

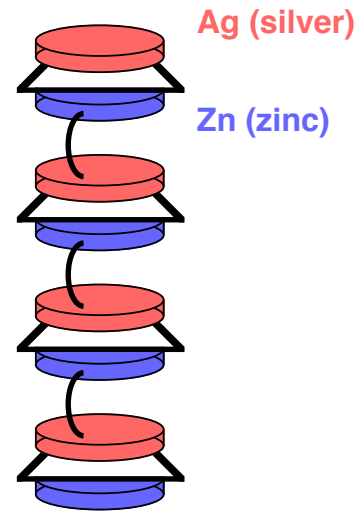

This slide courtesy of Mr. White!

Battery as a “pump”


- In the water circuit, the pump took in water at low pressure, did work on it (compressed it), then released it at high pressure to cause the flow through the pipes
- In an electrical circuit, what does the battery do?


pressure = $\frac{\text{energy}}{\text{volume}}$

pressure = $\frac{F}{A}$

$\frac{F}{A} = \frac{F d}{A d} = \frac{W}{V}$

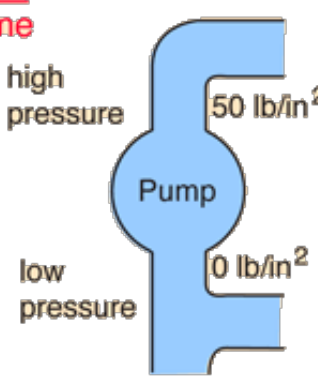
= $\frac{\text{energy}}{\text{volume}} = \frac{\text{joule}}{\text{m}^3}$




 A closed faucet has pressure behind it, but no flow. (resistance →)

voltage = $\frac{\text{energy}}{\text{charge}}$

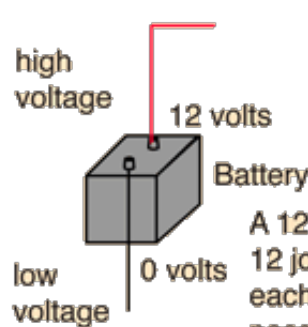volt = $\frac{\text{joule}}{\text{coulomb}}$



A 12 volt battery does 12 joules of work on each unit of charge which passes through it.


 A receptacle has voltage behind it, but no current if nothing is plugged in. (resistance →)

A battery takes charge, does work on it, then releases it at high potential energy. **It does not create or provide charge, it merely pumps the charge already in the wires.**

Remember that the voltage of a battery is the potential difference between the terminals!

Conventional current

- Electrons will flow from the negative node, anode, to the positive node, cathode, as long as a potential difference exists.
 - More generally, **charge carriers** will flow in a direction determined by the electric field
- Conventional current is visualized as flowing from the cathode to the anode. Conventional current aligns with the electric field within the conductor.
- The electric field within the conducting path drives the current.
 - Remember, an electric field does not exist within a conductor when the charges are not moving, but it does exist within the conductor when charges do move!

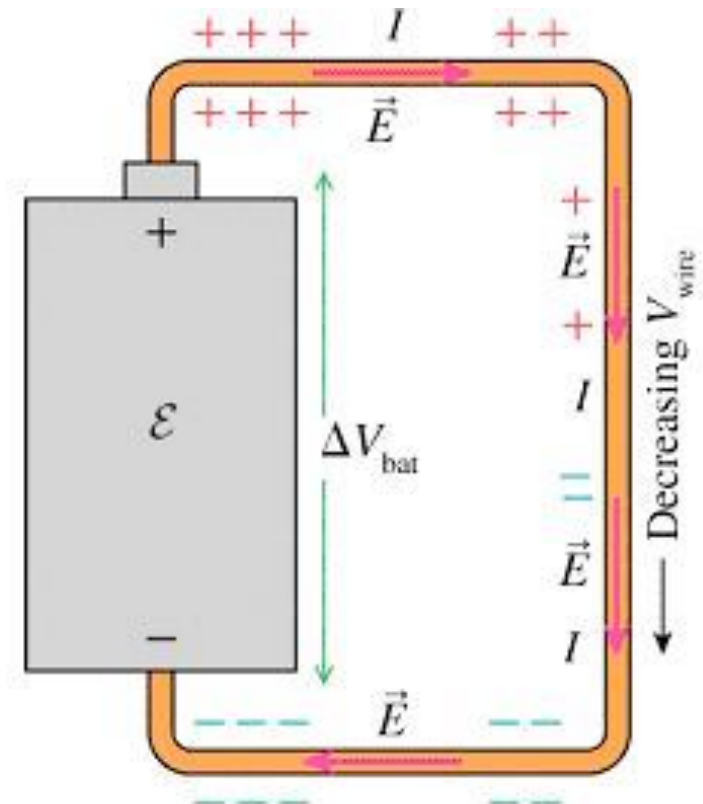

More about current and energy

- In electrostatics, why was the electric potential the same everywhere in a conductor?
- In circuits, this is no longer true. Charge moving along the wire moves from high to low potential, meaning they lose energy (and it doesn't go to KE, like a test charge did before).
 - The relationship $\Delta U = q\Delta V$ still holds! The electrons lose energy $q\Delta V$, and energy $-q\Delta V$ is deposited in the wire.
 - That energy goes into whatever the circuit is trying to do: make light, heat, run an appliance, etc.
 - If you can calculate the ΔU , dividing it by the time elapsed gives the power in Watts: $P = W/t = \Delta U/t$

Example problem

- 4 C of charge flows through a lightbulb filament in 2 seconds.
 - What's the (average) current in the lightbulb?

$$I = \frac{\Delta Q}{\Delta t} = \frac{4 \text{ C}}{2 \text{ s}} = 2 \text{ A}$$

- How many electrons pass through the filament in 5 seconds?

$\Delta Q = I\Delta t$, and ΔQ can also be thought of as Nq (where N is the number of electrons (q)), so...

$$N = \frac{I\Delta t}{q} = \frac{(2 \text{ A})(5 \text{ s})}{1.6 \times 10^{-19} \text{ C}} = 6.7 \times 10^{19} \text{ electrons}$$

- If connected to a 12-V battery for 2 seconds, what's the total energy and the power delivered?

$$\Delta U = q\Delta V = (4 \text{ C})(12 \text{ V}) = 48 \text{ J}$$

$$P = \frac{\Delta U}{t} = \frac{48 \text{ J}}{2 \text{ s}} = 24 \text{ W}$$