

Analyzing a complex circuit by the “seat of your pants”


- First step will almost always be to find the equivalent resistance of the circuit
 - This allows you to find the current through the battery, e.g. the total current in the circuit
 - Remember to break down internal pieces step by step, redrawing the circuit if necessary, to find total resistance
 - Also remember that ammeters and voltmeters are irrelevant to the behavior of the circuit! They merely measure what’s going on.
- Then, use Ohm’s Law on as many segments as needed to find the current through a particular branch and/or the voltage across a resistor. Repeat!
- *There is a more formal way to do this we will learn in a bit. This is the “seat of your pants” way that can work for moderately complex circuits.*

Quick conceptual warm-up

13.27) Using as many $12\ \Omega$ resistors as you need, produce a resistor circuit whose equivalent resistance is:

- a.) $18\ \Omega$; and
- b.) $30\ \Omega$.


Where are we going with this?
Complex circuits - like this one! How would you go about finding the equivalent resistance of this circuit?

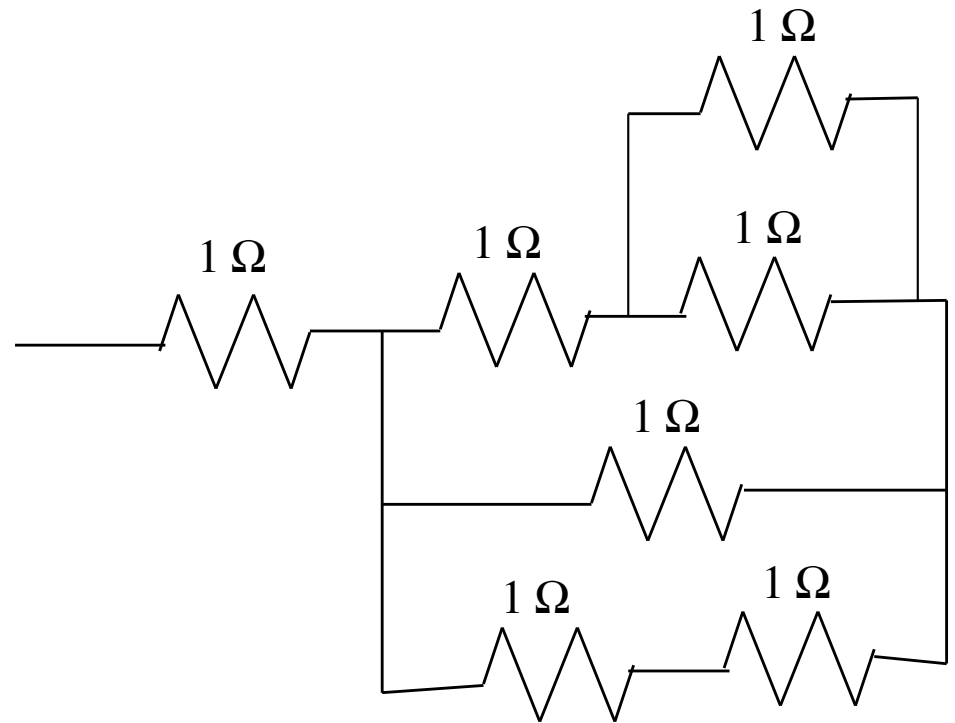

Problem 18.6

Problem 18.6

a.) Equivalent resistance?

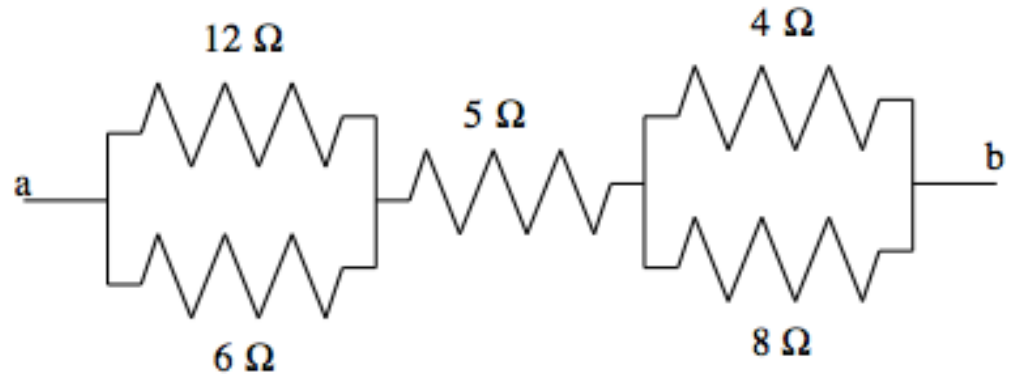

b.) If the voltage between "a" and "b" is 35 volts, what are the currents through each branch.

Reminders about power

- Power is how much electrical energy is being turned into heat/light/etc. each second:

$$P = IV$$

- Using Ohm's law, we can also substitute:

$$P = I^2R = V^2/R$$

- What does the power rating of a bulb or resistor really mean?
 - A “100 W” rated resistor means that when plugged into a standard voltage outlet (120 V, in the US), it dissipates 100 W of power. Knowing that, we could figure out, say, its resistance...or the current when plugged into that outlet by itself...