

### Problem 18.36


A 10 microfarad cap is charged by a 10 volts through a resistor R. The cap reaches 4 volts in 3 seconds after charging begins. What's R?

This isn't a great problem, but it won't hurt you to think a little about the time characteristics of charge build-up on a capacitor.

From its definition:

$$\begin{aligned}C &= \frac{q(t)}{V_c} \\ \Rightarrow V_c &= \frac{q(t)}{C} \\ &= \frac{1}{C} (Q_{\max} (1 - e^{-t/RC})) = \frac{Q_{\max}}{C} (1 - e^{-t/RC}) \\ &= \epsilon (1 - e^{-t/RC})\end{aligned}$$

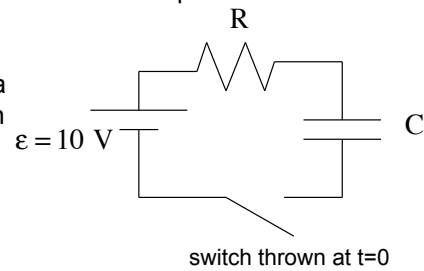
where  $V_c$  is the voltage across the capacitor plates at time "t."



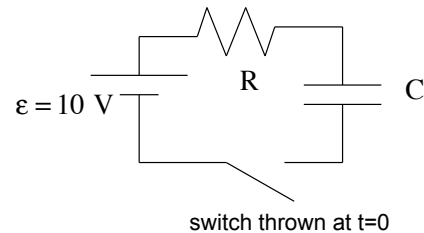1.

Solving this for R yields:

$$\begin{aligned}V_c &= \epsilon (1 - e^{-t/RC}) \\ \Rightarrow \frac{V_c}{\epsilon} - 1 &= -e^{-t/RC} \\ \Rightarrow \ln\left(1 - \frac{V_c}{\epsilon}\right) &= \ln(e^{-t/RC}) \\ \Rightarrow \ln\left(1 - \frac{V_c}{\epsilon}\right) &= \frac{-t}{RC} \\ \Rightarrow R &= \frac{-t/C}{\ln\left(1 - \frac{V_c}{\epsilon}\right)} \\ \Rightarrow R &= \frac{-(3 \text{ sec}) / (10 \times 10^{-6} \text{ f})}{\ln\left(1 - \frac{(4 \text{ V})}{(10 \text{ V})}\right)} \\ \Rightarrow R &= 5.87 \times 10^5 \Omega\end{aligned}$$



2.