

Problem 17.10

What is the resistance if a voltage of 120 volts generates a current of 13.5 amps?

1.)

Problem 17.10

What is the resistance if a voltage of 120 volts generates a current of 13.5 amps?

$$V = i R$$

$$\Rightarrow R = \frac{V}{i}$$

$$\Rightarrow R = \frac{120 \text{ V}}{13.5 \text{ A}}$$

$$\Rightarrow R = 8.89 \Omega$$

2.)