
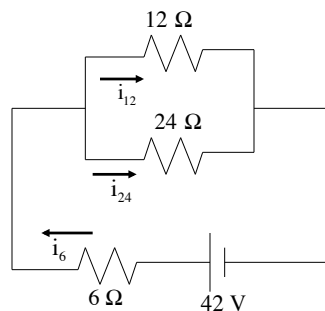


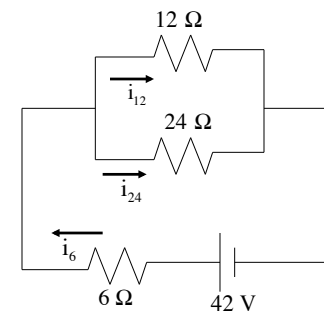Problem 18.16a

Use seat of pants to determine each current.



1.




3.

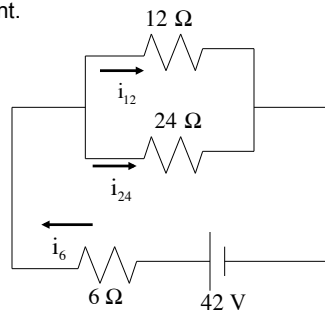18.16a) Use seat of pants to determine each current.

$$\begin{aligned} R_{\text{eq}} &= 6 + \left(\frac{1}{12} + \frac{1}{24} \right)^{-1} \\ &= 6 + \left(\frac{1}{12} + \frac{1}{24} \right)^{-1} \\ &= 14 \Omega \end{aligned}$$

$$\begin{aligned} V &= i_6 R_{\text{eq}} \\ \Rightarrow 42 &= i_6 (14) \\ \Rightarrow i_6 &= \frac{42 \text{ V}}{14 \Omega} \\ \Rightarrow i_6 &= 3 \text{ A} \end{aligned}$$



2.

The voltage across the two parallel resistors is:

$$\begin{aligned} V_{\text{parallel}} &= 42 - (6 \Omega)(3 \text{ A}) \\ &= 24 \text{ V} \end{aligned}$$


For the 12 ohm resistor, then:

$$\begin{aligned} V_{\text{parallel}} &= 24 = (i_{12})(12 \Omega) \\ \Rightarrow i_{12} &= 2 \text{ A} \end{aligned}$$

For the 24 ohm resistor, then:

$$\begin{aligned} V_{\text{parallel}} &= 24 = (i_{24})(24 \Omega) \\ \Rightarrow i_{24} &= 1 \text{ A} \end{aligned}$$

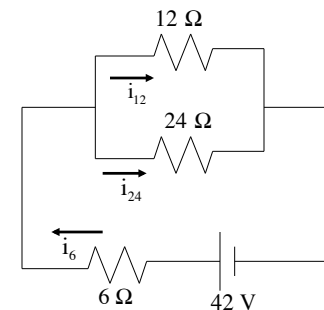Note that this makes sense. Because its resistance is lower by half, the 12 ohm resistor should have twice the current as the 24 ohm resistor . . . and the two currents have to sum to 3 amps.



4.

b) Using Kirchoff's Laws:

node equation:


$$\sum i_{\text{into node A}} = \sum i_{\text{out of node A}}$$
$$i_6 = i_{12} + i_{24}$$

Loop 1 (including 24 ohm resistor):

$$\sum V = 0$$
$$\Rightarrow 42 - 6i_6 - 24i_{24} = 0$$

Loop 2 (including 12 ohm and 24 ohm resistor):
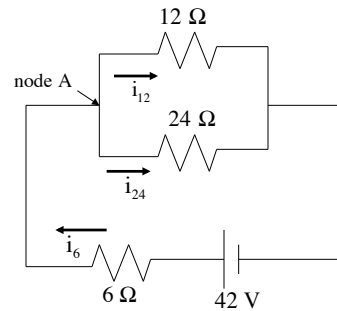
$$\sum V = 0$$
$$\Rightarrow -12i_{12} + 24i_{24} = 0$$



5.

b) Solving:

From Loop 1:


$$42 - 6i_6 - 24i_{24} = 0$$
$$\Rightarrow i_6 = \frac{42 - 24i_{24}}{6}$$
$$\Rightarrow i_6 = 7 - 4i_{24}$$

From Loop 2:

$$-12i_{12} + 24i_{24} = 0$$
$$\Rightarrow i_{12} = 2i_{24}$$

From Node Equ:
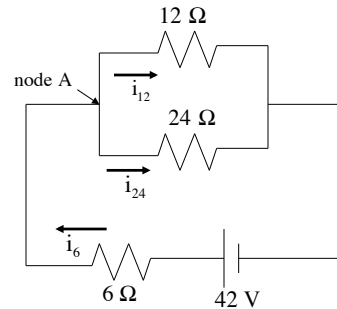
$$i_6 = i_{12} + i_{24}$$
$$\Rightarrow (7 - 4i_{24}) = (2i_{24}) + i_{24}$$
$$\Rightarrow i_{24} = 1 \text{ A}$$
$$\Rightarrow i_{12} = 2 \text{ A}$$
$$\Rightarrow i_6 = 3 \text{ A}$$



6.