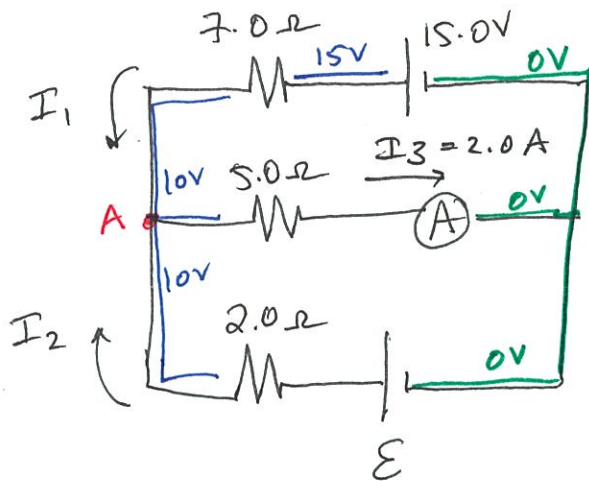


Problem 18.17



Find unknowns (I_1, I_2, ϵ).

$$I_1 + I_2 = 2.0 \text{ A} \rightarrow \text{combine @ A}$$

① Need to go piecemeal: start w/ what we know about ΔV in places:

— line = 0V (low V side of both batteries)

② @ 15V battery, know V on high V side is 15V

③ ~~2.0 A~~ for middle branch, know $R + I$ so...

$$\Delta V = IR = (2.0 \text{ A})(5.0 \Omega) = 10 \text{ V}$$


That means V @ A is 10V

④ so, $\Delta V_{7\Omega} = 5 \text{ V}$. $I = \frac{\Delta V}{R} = \frac{5 \text{ V}}{7.0 \Omega} = \boxed{0.714 \text{ A}} = I_1$

⑤ back to $I_1 + I_2 = 2.0 \text{ A}$, so $I_2 = 2.0 \text{ A} - 0.714 \text{ A} =$

$$\boxed{1.286 \text{ A}} = I_2$$

⑥ to find ϵ : here's what we know:

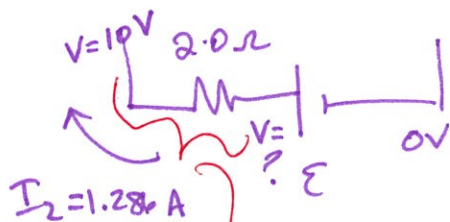

$$\Delta V = IR = (1.286 \text{ A})(2.0 \Omega) = 2.572 \text{ V}$$

$$\text{so } V @ \epsilon_+ = 10 + 2.572 = \boxed{12.572 \text{ V}}$$