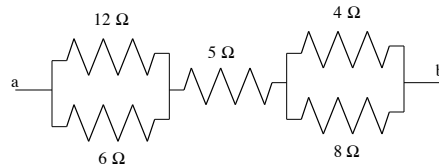


### Problem 18.6


a.) Equivalent resistance?



b.) If the voltage between “a” and “b” is 35 volts, what are the currents through each branch.

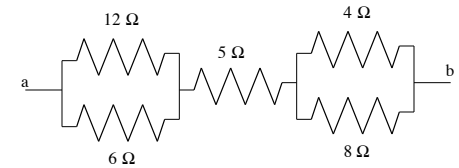1.)

b.) If the voltage between “a” and “b” is 35 volts, what are the currents through each branch.



With the equivalent resistance being 11.67 ohms, the current into the group will be:

$$i_{in} = \frac{\epsilon}{R_4} = \frac{35V}{11.67\Omega} = 3 \text{ amps}$$

That means that 3 amps flows through the 5 ohm resistor in the middle.

As for the first parallel combination, the 12 ohm resistor is twice as large as the 6 ohm resistor, so it will have *half as much* current through it as does the smaller 6 ohm resistor. In other words, 2 amps will go through the 6 ohm resistor while 1 amp flows through the 12 ohm resistor. (As a minor side point: notice that the voltage across the 12 ohm resistor is  $iR=(1 \text{ amp})(12 \text{ ohms}) = 12 \text{ volts}$ . This is the same as the voltage across the 6 ohm resistor ( $iR=(2 \text{ amp})(6 \text{ ohms}) = 12 \text{ volts}$ ), as expected.

3.)

a.) Equivalent resistance?

$$R_{eq1} = \left( \frac{1}{12\Omega} + \frac{1}{6\Omega} \right)^{-1} = 4\Omega$$


$$R_{eq2} = \left( \frac{1}{8\Omega} + \frac{1}{4\Omega} \right)^{-1} = 2.67\Omega$$

so:

$$R_{eq} = R_{eq1} + R_5 + R_{eq2} = 4\Omega + 5\Omega + 2.67\Omega = 11.67\Omega$$

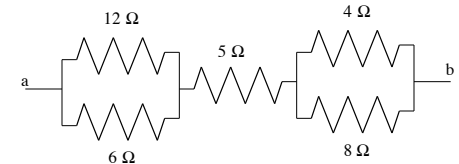2.)

Similarly to the first parallel combination, the second parallel circuit has an 8 ohm resistor which is twice as large as the 4 ohm resistor in the combination. That means *half as much* current will flow through it as does the smaller 4 ohm resistor. 3 amps flows into the combination, so 2 amps must go through the 4 ohm resistor while 1 amp flows through the 8 ohm resistor. (And again: notice that the voltage across the 8 ohm resistor is  $iR=(1 \text{ amp})(8 \text{ ohms}) = 8 \text{ volts}$ . This is the same as the voltage across the 4 ohm resistor ( $iR=(2 \text{ amp})(4 \text{ ohms}) = 8 \text{ volts}$ ), as expected.



As an additional side point: Notice that 12 volts is across the first parallel combination, 8 volts is across the second parallel combination which would suggest that 15 volts must be across the 5 ohm resistor ( $35 - 12 - 8 = 15$ ). Low and behold,

$$V_5 = i_0 R_5 = (3 \text{ A})(5 \Omega) = 15 \text{ volts}$$

Damn! We are good!

4.)