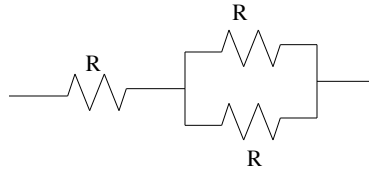


Problem 18.12

The maximum power to the circuit is 24 W.


a.) What's the equivalent resistance?



b.) Maximum voltage? We need to determine the current first. Using Ohm's Law:

4.

c.) The power values for each resistor:

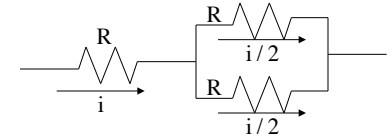


6.

The maximum power to the circuit is 24 W.

a.) What's the equivalent resistance?
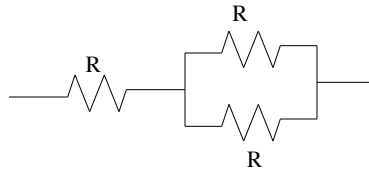
$$R_{\text{equ}} = R + \left(\frac{1}{R} + \frac{1}{R} \right)^{-1}$$
$$= \frac{3}{2}R$$



b.) Maximum voltage? We need to determine the current first. Using Ohm's Law:

$$V_o = iR_{\text{eq}} \quad \text{and} \quad P = i^2 R_{\text{eq}} = iV_o = 24$$
$$\Rightarrow V_o = i(1.5R) \quad \text{and} \quad 24 = iV_o$$
$$\Rightarrow i = \frac{24}{V_o}$$
$$\Rightarrow V = \left(\frac{24}{V} \right) (1.5R)$$
$$\Rightarrow V^2 = 36R$$
$$\Rightarrow V = 6R^{1/2}$$

5.

c.) The currents are identified in the sketch. The power value for the first resistor is, therefore:

$$P_{R1} = i^2 R$$

For each of the two resistors in parallel, the power value is:

$$P_{\text{parallel}} = \left(\frac{i}{2} \right)^2 R$$
$$= \left(\frac{1}{4} \right) i^2 R$$

So if $i^2 R$ goes to the first resistor and a quarter of that amount goes to each of the parallel resistors, the first resistor evidently dissipated 16 watts and each of the other two dissipated 4 watts. (I.e., the power is cut into 6 parts with 4 parts going to the first resistor and 1 part going to each of the parallel resistors.)

7.

