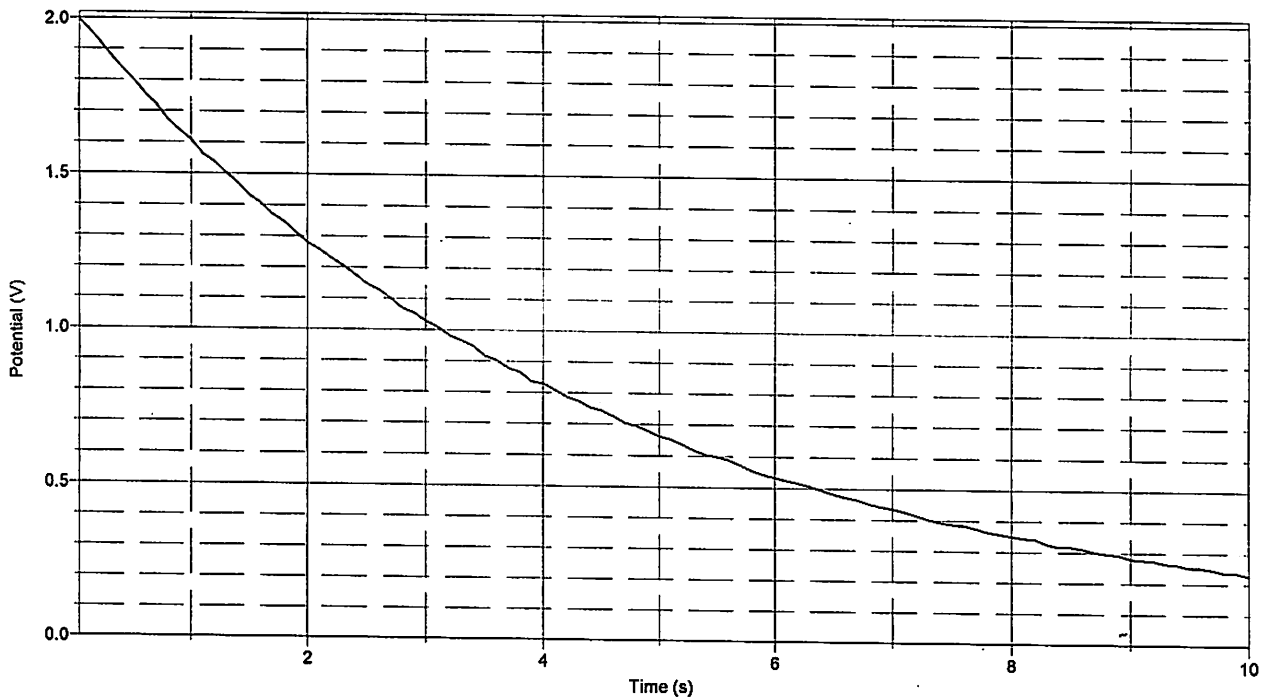


CAPACITORS LAB



$$R = 41.8 \times 10^3 \Omega$$

$$C_1 = 96.8 \times 10^{-6} \text{ f}$$

$$C_2 = 48.5 \times 10^{-6} \text{ f}$$

$$C_{\text{series}} = 32.3 \times 10^{-6} \text{ f}$$

$$C_{\text{parallel}} = 145.8 \times 10^{-6} \text{ f}$$