

GAME CIRCUITS

For each circuit, determine the current through each resistor and each meter. (Make a note of your results as you will be turning in this page and your work at the beginning of the period.) Assume the power supplies are ideal (that is, the internal resistance of the battery is zero).

