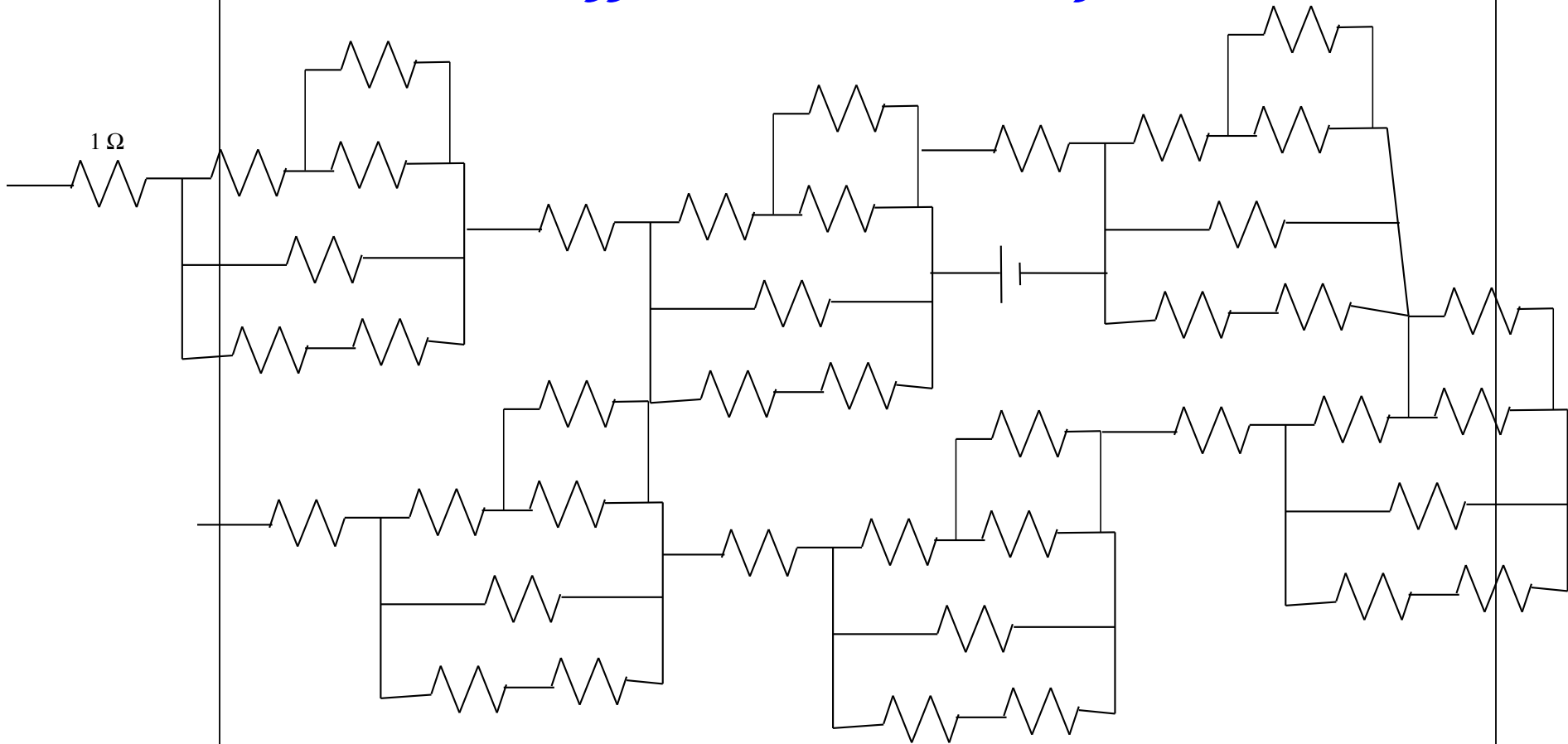


# CHAPTER 28B (extended): Kirchoff's Laws and Capacitors




1.)
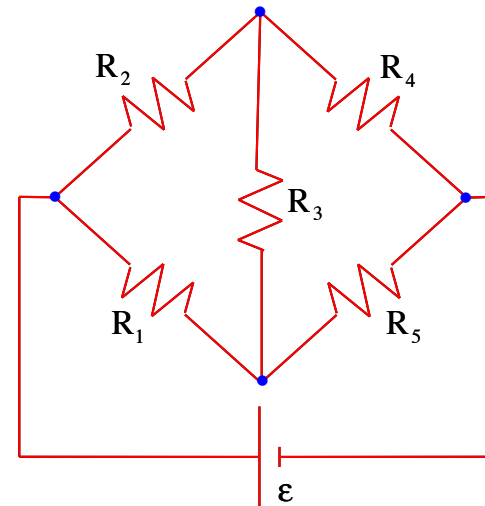
## *The Island Series:*

You have been kidnapped by a crazed physics nerd and left on an island with twenty-four hours to solve the following problem. Solve the problem and you get to leave. Don't solve the problem and you don't.

*The problem:* Determine the equivalent resistance for the combination of resistors found in the circuit to the right.




1.)

# Some Definitions

**A branch:** A section of a circuit in which the current is the same everywhere.

--elements in series are a part of a single branch (look at sketch).

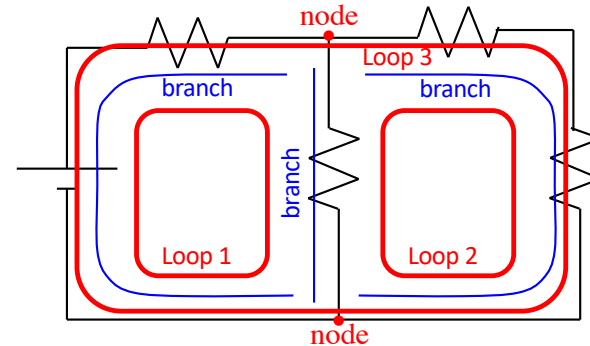--in the circuit to the right, there are three branches.



**A node:** A junction where current can split up or be added to.

--elements in parallel have nodes internal to the combination.

--in the circuit above, there are two nodes.

**A loop:** Any closed path inside a circuit.

--in a circuit, loops can be traverse in a clockwise or counterclockwise direction.

--in the circuit above, there are three loops.

## For the Amusement

For the circuit to the right:

a.) How many *branches* are there?


six

b.) How many *nodes* are there?

four

c.) How many *loops* are there?

seven

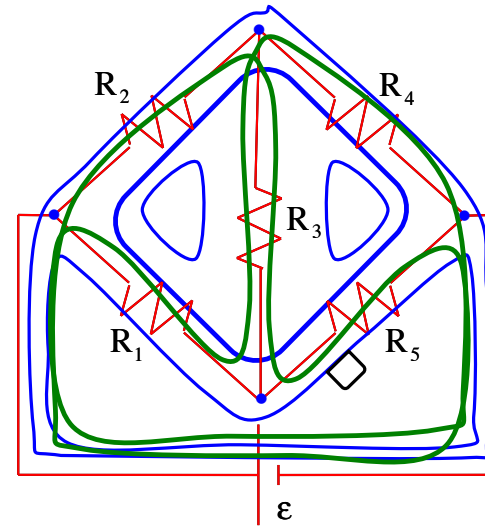

*And that last* little nubbin is supposed to be a tooth, cause this looks like a face to me!

## For the Amusement

For the circuit to the right:

a.) How many *branches* are there?


six

b.) How many *nodes* are there?

four

c.) How many *loops* are there?


seven

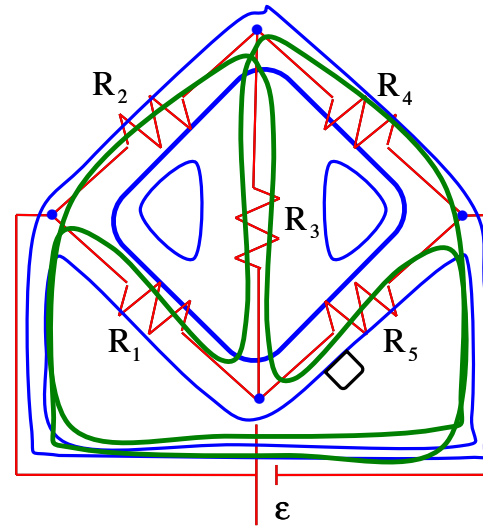

*And that last* little nubbin is supposed to be a tooth, cause this looks like a face to me!
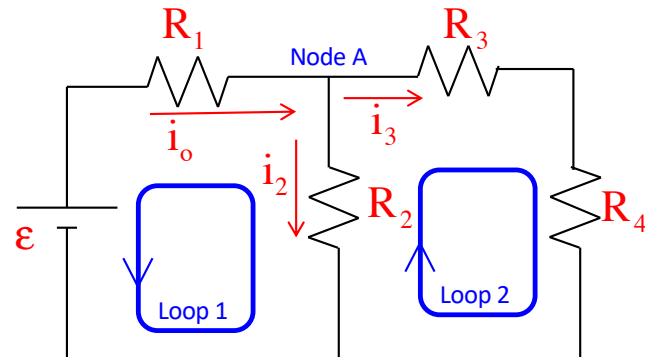
# Kirchoff's Laws—the Formal Approach

*With the definitions* under your belt, Kirchoff's Laws are simple (and you've been inadvertently using them in the seat-of-the-pants evaluations). They are:



*Kirchoff's First Law:* The **sum of the currents into a node equals** the **sum of the currents out of a node**. Mathematically, this is written as:  $\sum i_{\text{into node}} = \sum i_{\text{out of node}}$

*Example* from the circuit's **Node A**:  $i_0 = i_2 + i_3$

*Kirchoff's Second Law:* The **sum of the voltage changes around a closed path** (a loop) **equals ZERO**. Mathematically, this is written as:  $\sum \Delta V = 0$

*Examples:* starting at **Node A**:

**Loop 1 traversing counterclockwise:**

$$R_1 i_0 - \varepsilon + R_2 i_2 = 0$$

**Loop 2 traversing clockwise:**

$$-R_3 i_3 - R_4 i_3 + R_2 i_2 = 0$$

*Note:* Current moves from **hi to lo** voltage, so **traversing against the current** through a resistor **produces a  $\Delta V$  that is positive**; traversing **with current** makes it **negative**.

# Kirchoff's Laws—Using the Approach

*Example 8: Determine* the *meter reading* in the circuit to the right using Kirchoff's Laws. Assume the power supply is ideal with an EMF of 10 volts, and assume the resistor values are the same as their subscripts (this is essentially *Example 4*).


*Step 0:* Remove the meters.

*Step 1:* Define one *current* for each branch.


*Step 2.* Write out *node equations* for as many nodes as you can (see note below). Be sure to identify which node you are working with. For this problem: Node A:

$$i_0 = i_2 + i_3$$

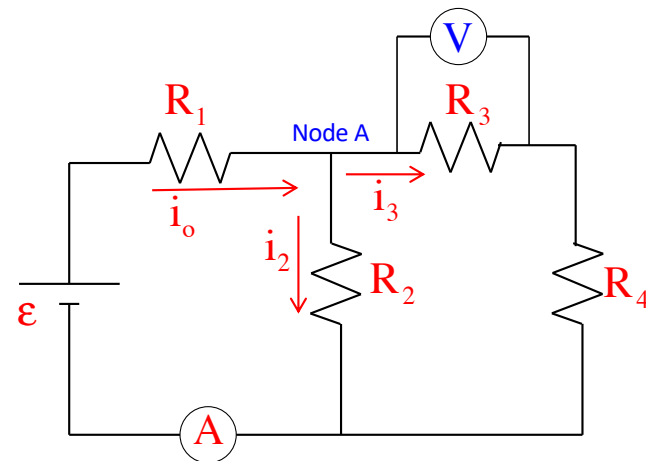*Important note:* If you had written out the node equation for the node at the bottom, you would have gotten  $i_2 + i_3 = i_0$ . This is the same equation as above. There will *always* be *fewer independent node equations than actual nodes* in a circuit. In this case, there were *two nodes* and only *one independent node equation*.



*Additional note:* You have three branches and three unknown currents, which means you will need *three equations to solve*. You have *one node equation*, which means you will need *two more equations*, presumably from your *loops*. *Kindly note:* there are *three loops in this circuit*, but you can *only get TWO INDEPENDENT LOOP EQUATIONS* from them. *Any two* of those equations *will do*, and any two will produce the third, which means that if you try to do this problem using nothing but loop equations, you'll end up with mush. (Try it if you don't believe me!)

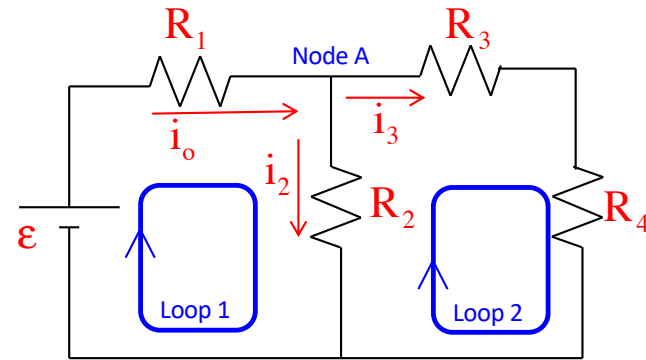

*Step 3.* Identify and label the *loops* you will use. Use an arrow in each to show the *direction* you intend to *traverse* that loop.

*Note 1:* If there is a power supply in the loop, I prefer to start at the low voltage terminal and proceed through the supply. That way, the voltage change through the supply will be positive. With that in mind:

Loop 1:

$$\epsilon - R_1 i_0 - R_2 i_2 = 0$$

Loop 2:

$$R_2 i_2 - R_3 i_3 - R_4 i_3 = 0$$

*Note 2:* Put resistance terms first as they'll usually be assumed known whereas currents will not be.



## Solving 3 Equations with 3 Unknowns

*We have* three equations and three unknowns. The ammeter is in the branch whose current is  $i_o$ . So how to solve for  $i_o$ ? There are three approaches.

*Our equations:*

$$\varepsilon - R_1 i_o - R_2 i_2 = 0 \quad (\text{equ. A}) \qquad R_2 i_2 - R_3 i_3 - R_4 i_3 = 0 \quad (\text{equ. B})$$

$$i_o = i_2 + i_3 \quad (\text{equ. C})$$

*Putting in the numbers* to make life easier:

$$10 - i_o - 2i_2 = 0 \quad (\text{equ. A}) \qquad 2i_2 - 3i_3 - 4i_3 = 0 \quad (\text{equ. B})$$

$$\Rightarrow 2i_2 - 7i_3 = 0$$

$$i_o = i_2 + i_3 \quad (\text{equ. C})$$

*Approach 1—Brute force algebra:*

*I'll lay this out* on the next page, just to convince you it's not the way to go.

*Like I said, NASTY!*

$$i_o = i_2 + i_3 \quad (\text{equ. C})$$

$$\text{as } 2i_2 - 7i_3 = 0 \quad (\text{equ. B})$$

$$\Rightarrow i_3 = \frac{2}{7}i_2$$

$$\Rightarrow i_o = i_2 + i_3$$

$$= i_2 + \frac{2}{7}i_2 = \frac{9}{7}i_2$$

$$\text{but } 10 - i_o - 2i_2 = 0 \quad (\text{equ. A})$$

$$\Rightarrow i_2 = \frac{10 - i_o}{2} = \frac{10}{2} - \frac{1}{2}i_o$$

$$\text{so } i_o = \frac{9}{7}i_2 = \frac{9}{7} \left( \frac{10}{2} - \frac{1}{2}i_o \right)$$

$$\Rightarrow i_o = \frac{90}{14} - \frac{9}{14}i_o$$

$$\Rightarrow 14i_o = 90 - 9i_o$$

$$\Rightarrow i_o = \frac{90}{23}$$

$$\Rightarrow i_o = 3.91 \text{ A}$$

*Approaches 2 and 3: Matrices:*

--Begin by rewriting each equation so their  $i_o$  term is in the first column, its  $i_2$  term is in the second column, etc., and its voltage term (if there is one) is on the right side of the equal sign.

*Our equations become:*

$$\varepsilon - R_1 i_o - R_2 i_2 = 0 \quad \text{becomes} \quad R_1 i_o + R_2 i_2 + 0 i_3 = \varepsilon$$

$$R_2 i_2 - R_3 i_3 - R_4 i_3 = 0 \quad \text{becomes} \quad 0 i_o + R_2 i_2 - (R_3 + R_4) i_3 = 0$$

$$i_o = i_2 + i_3 \quad \text{becomes} \quad i_o - i_2 - i_3 = 0$$

--Put the information into a matrix:

$$\begin{array}{ccc} i_o & i_2 & i_3 \\ \text{column} & \text{column} & \text{column} \end{array} \begin{array}{c} \\ \\ \\ \end{array} \begin{array}{ccc} R_1 & R_2 & 0 \\ 0 & R_2 & -(R_3 + R_4) \\ 1 & -1 & -1 \end{array} \begin{array}{c} \\ \\ \\ \end{array} \begin{array}{c} i_o \\ i_2 \\ i_3 \end{array} = \begin{array}{c} \varepsilon \\ 0 \\ 0 \end{array} \begin{array}{c} \text{voltage} \\ \text{column} \\ \end{array}$$

--Using numbers:

$$\begin{vmatrix} R_1 & R_2 & 0 \\ 0 & R_2 & -(R_3 + R_4) \\ 1 & -1 & -1 \end{vmatrix} \begin{vmatrix} i_o \\ i_2 \\ i_3 \end{vmatrix} = \begin{vmatrix} \varepsilon \\ 0 \\ 0 \end{vmatrix} \quad \text{becomes} \quad \begin{vmatrix} 1 & 2 & 0 \\ 0 & 2 & -7 \\ 1 & -1 & -1 \end{vmatrix} \begin{vmatrix} i_o \\ i_2 \\ i_3 \end{vmatrix} = \begin{vmatrix} 10 \\ 0 \\ 0 \end{vmatrix}$$

--You have two options at this point, depending upon your abilities with a calculator and whether there are any variables in your relationship. The first approach is a manual evaluation of the matrices and will always work.

*Noting that* the left-hand 3x3 matrix is called *the determinate*, solving for, say,  $i_o$ , requires the evaluation of two matrices, one divided into the other. Specifically, the *determinate divided into the determinate with the column replaced by the voltage column* (the far column to the right). That is:

$$i_o = \frac{\begin{vmatrix} 10 & 2 & 0 \\ 0 & 2 & -7 \\ 0 & -1 & -1 \end{vmatrix}}{\begin{vmatrix} 1 & 2 & 0 \\ 0 & 2 & -7 \\ 1 & -1 & -1 \end{vmatrix}}$$

--How to evaluate a matrix? Start by reproducing the first two columns at the end of the matrix.

$$i_o = \frac{\begin{array}{c|cc|c} \varepsilon & R_2 & 0 \\ 0 & R_2 & -(R_3 + R_4) \\ 0 & -1 & -1 \end{array}}{\begin{array}{c|cc|c} R_1 & R_2 & 0 \\ 0 & R_2 & -(R_3 + R_4) \\ 1 & -1 & -1 \end{array}} \frac{\begin{array}{c|c} \varepsilon & R_2 \\ 0 & R_2 \\ 0 & -1 \end{array}}{\begin{array}{c|c} R_1 & R_2 \\ 0 & R_2 \\ 1 & -1 \end{array}}$$

--With numbers:

$$i_o = \frac{\begin{array}{c|cc|c} 10 & 2 & 0 \\ 0 & 2 & -7 \\ 0 & -1 & -1 \end{array}}{\begin{array}{c|cc|c} 1 & 2 & 0 \\ 0 & 2 & -7 \\ 1 & -1 & -1 \end{array}} \frac{\begin{array}{c|c} 10 & 2 \\ 0 & 2 \\ 0 & -1 \end{array}}{\begin{array}{c|c} 1 & 2 \\ 0 & 2 \\ 1 & -1 \end{array}}$$

--The first part of the execution is shown below:

$$i_o = \frac{\begin{vmatrix} \textcircled{10} & 2 & 0 & | & 10 & 2 \\ 0 & \overset{x}{2} & -7 & | & 0 & 2 \\ 0 & -1 & -1 & | & 0 & -1 \end{vmatrix}}{\begin{vmatrix} 1 & 2 & 0 & | & 1 & 2 \\ 0 & 2 & -7 & | & 0 & 2 \\ 1 & -1 & -1 & | & 1 & -1 \end{vmatrix}} = \frac{(10)[(2)(-1) - (-7)(-1)] + \dots}{\text{etc.}}$$

$$i_o = \frac{\begin{vmatrix} 10 & 2 & 0 & | & 10 & 2 \\ 0 & 2 & -7 & | & 0 & 2 \\ 0 & -1 & -1 & | & 0 & -1 \end{vmatrix}}{\begin{vmatrix} 1 & 2 & 0 & | & 1 & 2 \\ 0 & 2 & -7 & | & 0 & 2 \\ 1 & -1 & -1 & | & 1 & -1 \end{vmatrix}}$$

--The second part:

$$i_o = \frac{\begin{vmatrix} 10 & \textcircled{2} & 0 & | & 10 & 2 \\ 0 & 2 & \overset{x}{-7} & | & 0 & 2 \\ 0 & -1 & -1 & | & 0 & -1 \end{vmatrix}}{\begin{vmatrix} 1 & 2 & 0 & | & 1 & 2 \\ 0 & 2 & -7 & | & 0 & 2 \\ 1 & -1 & -1 & | & 1 & -1 \end{vmatrix}} = \frac{(10)[(2)(-1) - (-7)(-1)] + (2)[(-7)(0) - (0)(-1)] + \dots}{\text{etc.}}$$

--Once you get the hang of the pattern, you can do these in your head without writing much of anything down:

$$i_o = \frac{\begin{vmatrix} 10 & 2 & 0 \\ 0 & 2 & -7 \\ 0 & -1 & -1 \end{vmatrix} \begin{vmatrix} 10 & 2 \\ 0 & 2 \\ 0 & -1 \end{vmatrix}}{\begin{vmatrix} 1 & 2 & 0 \\ 0 & 2 & -7 \\ 1 & -1 & -1 \end{vmatrix} \begin{vmatrix} 1 & 2 \\ 0 & 2 \\ 1 & -1 \end{vmatrix}} = \frac{(10)[(-2)-(7)]+0+0}{1[-2-(7)]+2[(-7)-0]+0} = \frac{-90}{-23} = 3.91 \text{ A}$$

--The other alternative has to do with matrix manipulation on a calculator. Specifically, if you multiply everything by the inverse determinate, you end up with a 1x3 matrix whose elements are the solution for the three unknowns.

$$\underbrace{\begin{vmatrix} D & E & T \end{vmatrix}^{-1} \begin{vmatrix} D & E & T \end{vmatrix}}_{=1} \begin{vmatrix} i_o \\ i_2 \\ i_3 \end{vmatrix} = \begin{vmatrix} V_o \\ V_2 \\ V_3 \end{vmatrix} \begin{vmatrix} D & E & T \end{vmatrix}^{-1}$$

$$\Rightarrow \begin{vmatrix} i_o \\ i_2 \\ i_3 \end{vmatrix} = \begin{vmatrix} V_o \\ V_2 \\ V_3 \end{vmatrix} \begin{vmatrix} D & E & T \end{vmatrix}^{-1}$$

--the *alternate alternate* is to have your calculator execute an rref (reduce row echelon format) operation. The following is courtesy of Mr. White.

$$\begin{array}{l}
 i_o + 2i_2 + 0i_3 = 10 \\
 0i_o + 2i_2 - 7i_3 = 0 \\
 i_o - i_2 - i_3 = 0
 \end{array}
 \Rightarrow
 \begin{array}{cccc}
 1 & 2 & 0 & 10 \\
 0 & 2 & -7 & 0 \\
 1 & -1 & -1 & 0
 \end{array}$$

*Using your calculator:*

- Math -> Matrix -> Edit -> A (for name of matrix) . . . note that some calculators just have a “matrix” key you can use (versus starting with “math”)
- 3 [Enter] 4 [Enter] (this gives you a 3x4 matrix)
- Enter coefficients and values into Matrix; exit, then go back to “matrix” and:
- In “math,” use “rref” A (reduced row echelon form)
- You’ll end up with 1’s and the last row will give you the current values.

$$\begin{bmatrix} 1 & 2 & 0 & 10 \\ 0 & 2 & -7 & 0 \\ 1 & -1 & -1 & 0 \end{bmatrix}
 \Rightarrow
 \begin{bmatrix} 1 & 0 & 0 & 3.91 \\ 0 & 1 & 0 & 3.04 \\ 0 & 0 & 1 & .87 \end{bmatrix}
 \Rightarrow
 \begin{array}{l}
 i_o = 3.91 \text{ A} \\
 i_2 = 3.04 \text{ A} \\
 i_3 = .87 \text{ A}
 \end{array}$$



*Example 9: Example 8* using a clever shortcut. Again the power supply is ideal with an EMF of 10 volts, and assume the resistor values are the same as their subscripts.


*Step 0:* Remove the meters.

*Step 1:* Define one *current* for each branch.

*And here is* the clever move.

*Think about it.* If current  $i_0$  comes into node A, and current  $i_2$  goes out of node A and through  $R_2$ , how much current must go through  $R_3$ ? Must be  $i_0 - i_2$ . So why not just call it that (instead of  $i_3$ )? Doing so *eliminates one unknown*, which makes the solving a lot easier.

*Consequence:* You only need to write two loop equations (you've already used the node information in defining the currents).

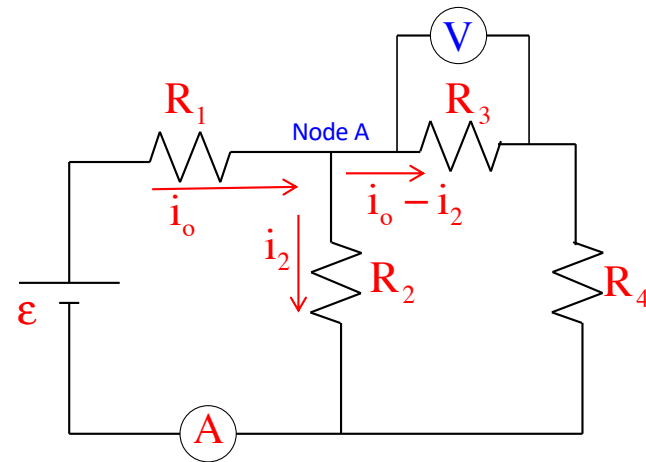

Loop 1:

$$\varepsilon - R_1 i_o - R_2 i_2 = 0$$

$$\Rightarrow i_o + 2i_2 = 10$$

Loop 2:


$$R_2 i_2 - R_3 (i_o - i_2) - R_4 (i_o - i_2) = 0$$

$$\Rightarrow 2i_2 - 3(i_o - i_2) - 4(i_o - i_2) = 0$$

$$\Rightarrow -7i_o + 9i_2 = 0$$

*Solving:*
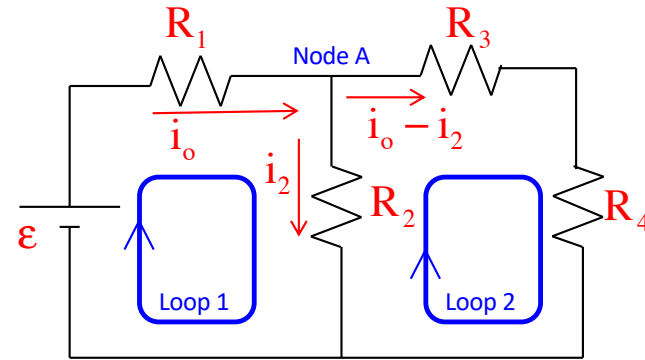
$$\Rightarrow i_o = \frac{\begin{vmatrix} 10 & 2 \\ 0 & 9 \end{vmatrix}}{\begin{vmatrix} 1 & 2 \\ -7 & 9 \end{vmatrix}} = \frac{90 - 0}{9 - (-14)} = 3.91\text{A}$$



## *The Island Series:*


You have been kidnapped by a crazed physics nerd and left on an island with twenty-four hours to solve the following problem. Solve the problem and you get to leave. Don't solve the problem and you don't.

*The problem:* You are given a **small spotlight**, the **outline of a bat** that can go **over the lamp's face**, **two copper serving platters**, some **wire** and a **car battery**. You find that if you hook the battery to the lamp, it doesn't shine very brightly. You need it to shine brightly, but only for a second (you want to project the bat-signal onto a cloud so Batman will come rescue you). What clever thing might you do to light up the lamp for just a moment?

*Solution:* Set the two plates close without touching and parallel to one another (they have to be rigidly separated). Hook one lead from the battery to one of the plates and the second lead to the other plate. This will allow the plates to charge up, acting like a capacitor. Disconnect the lead. Hook one lamp lead to one of the plates. When you hook the other lead to the other plate, the cap will discharge very quickly through the lamp, providing a burst of energy that should light it up nicely.

# CHAPTER 26: Capacitors

*discharging capacitor:*

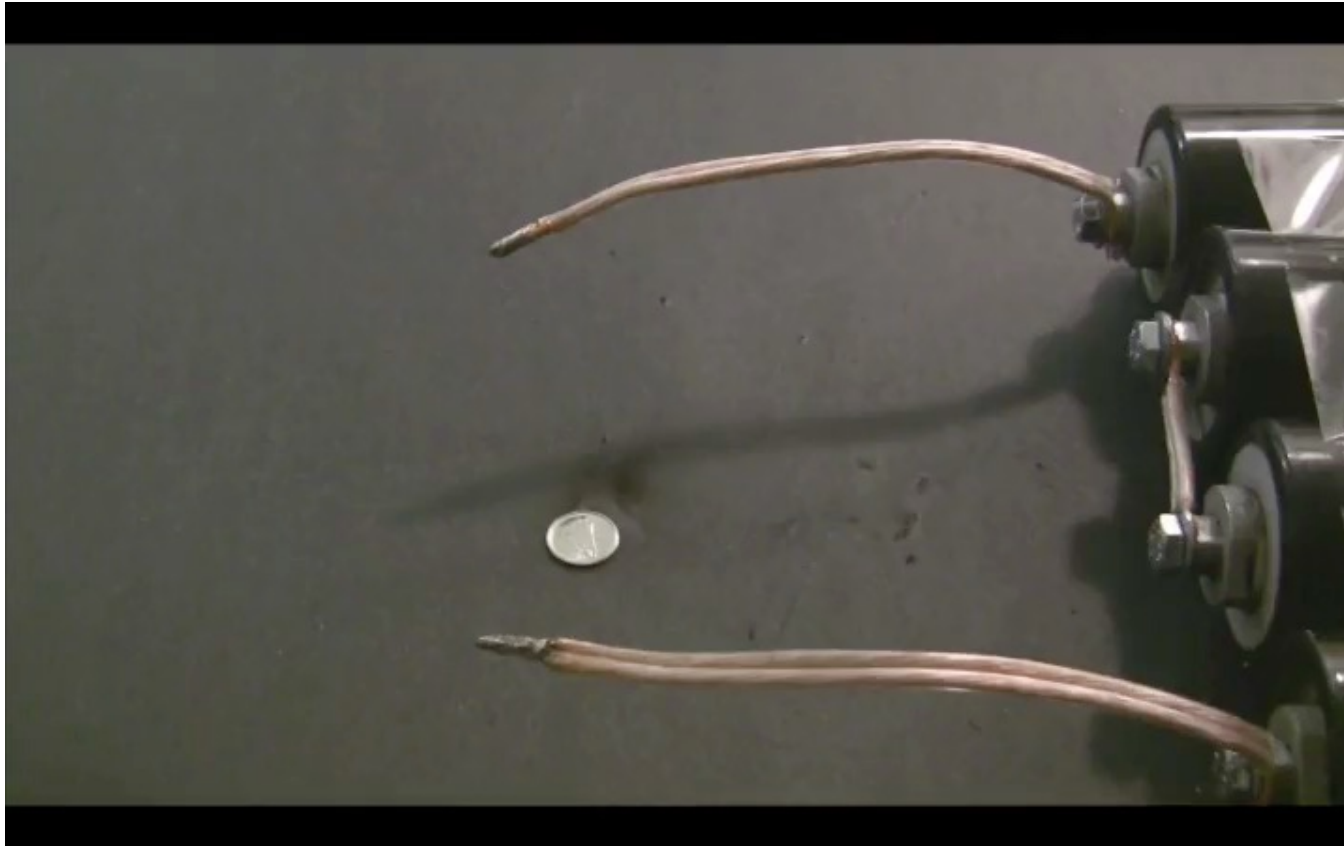

# General Review

*Electric fields:* exist in presence of charge configurations; are *modified force-fields*

*Gauss's Law:* used to generate electric field functions for symmetric charge configurations

*Electrical potentials:* voltage fields that exist in the presence of charge configurations; are *modified potential energy functions*; the potential *difference* between two points equals *work-per-unit-charge* available to a secondary charge due to presence of field-producing charge

$$|\vec{F}_{\text{coulomb}}| = k \frac{q_1 q_2}{r^2}$$

$$\mathbf{E} = \frac{\mathbf{F}}{q}$$

$$\Phi_E = \int_S \vec{E} \cdot d\vec{S}$$

$$\int_S \vec{E} \cdot d\vec{S} = \frac{q_{\text{encl}}}{\epsilon_0}$$

$$\Delta U = -\int \vec{F} \cdot d\vec{r} = -\int (q\vec{E}) \cdot d\vec{r}$$

$$\Delta V = -\int \vec{E} \cdot d\vec{r}$$

$$V_{\text{pt chg}} = -\int k \frac{dq}{r^2}$$

$$\mathbf{E} = -\frac{dV}{dr}$$


# Capacitors

A *physical capacitor* is quite literally two metal, parallel plates sitting next to one another, completely insulated from one another.

A *battery* generates an artificially created *electrical potential difference* between its terminals. The + terminal is at higher voltage (the + terminal is the longer, red line in the sketch). The “voltage” of the battery is the *electrical potential difference* between the terminals.

*Connecting a battery* across an uncharged capacitor will effect an interesting situation.

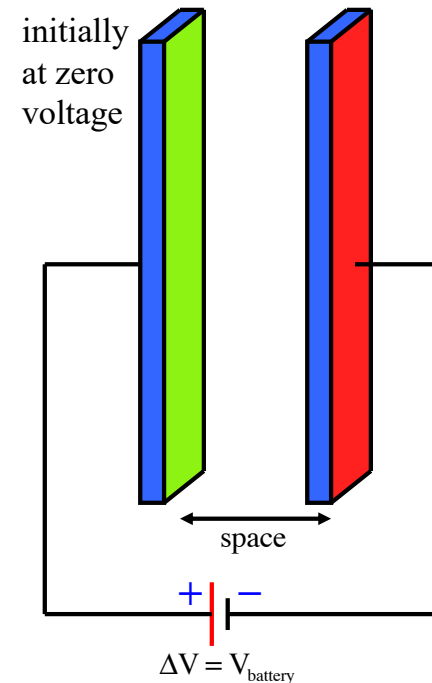*Initially*, there will be a *voltage difference* between the battery’s + terminal and the capacitor’s *uncharged green plate*, motivating charge to move between the two plates. If we assume it is *positive charge that is moving* (controversial, but we’ll talk about that later), the *green plate will begin to charge up positively*.




As the green (left) plate charges up, two things happen:

*Electrostatic repulsion* will motivate a like-amount of positive charge off the yellow plate, leaving it electrically negative; and

*The voltage build-up* on the green plate will diminish the voltage difference between it and the battery's + terminal, and the current will decrease (ultimately to zero once the cap is fully charged).

*What we end up with* in our charged capacitor is an electrical device that has charge stored on it, that has an electric field between its plates, and that has energy stored in that electric field.

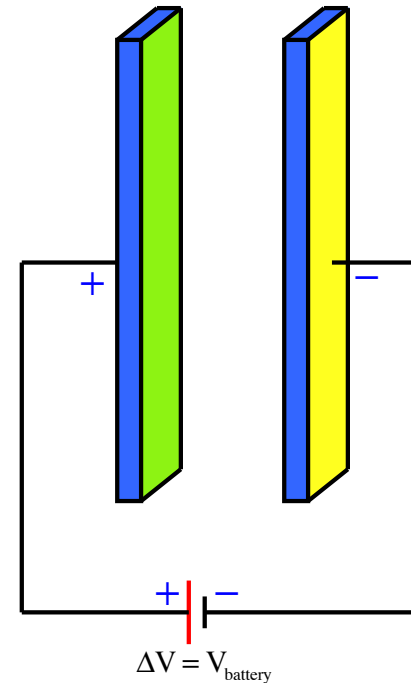*In other words*, in an DC (direct current) electrical circuit, capacitors store electrical energy.



Furthermore, the charge  $Q$  on ONE PLATE will always be proportional to the magnitude of the voltage difference across the plates, with the proportionality constant being the cap's *capacitance*. Mathematically, then:

$$Q_{\text{on one plate}} = C(\Delta V)_{\text{across plates}}$$

Usually written in truncated form as:

$$Q = CV$$


this also means that the capacitance is defined as:

$$C = \frac{Q}{V}$$

This, in turn, means the *capacitance* of a capacitor is a constant that tells you how much *charge per volt* the capacitor has the capacity to hold.

Its unit of *coulombs per volt* is given a special name—the **farad**.

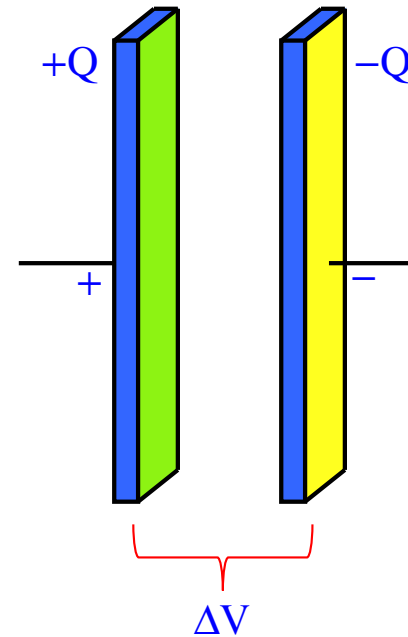It's not uncommon to find capacitors in the range of: **millifarad** ( $\text{mf} = 10^{-3} \text{f}$ ), or **microfarad** ( $\text{Mf}$  or  $\mu\text{f} = 10^{-6} \text{f}$ ), or **nanofarad** ( $\text{nf} = 10^{-9} \text{f}$ ), or **picofarad** ( $\text{pf} = 10^{-12} \text{f}$ ).





## Picky but Important Points

1.) A 1 farad capacitor is a HUGE capacitor. It is much more common to run into capacitors in the:

--millifarad (mf) range: this is  $10^{-3}$  farads

--microfarad (Mf or  $\mu\text{f}$ ) range: this is  $10^{-6}$  farads

--nanofarad (nf) range: this is  $10^{-9}$  farads


--picofarad (pf) range: this is  $10^{-12}$  farads

2.) When traversing between capacitor plates along the electric field lines, the voltage goes from high to low. That is why the negative sign is needed in  $\Delta V = -\vec{E} \cdot \vec{d}$ .

But  $V_{\text{cap}}$  in  $Q = CV_{\text{cap}}$  is the *POSITIVE* voltage-change across the plates, meaning:

$$V_{\text{cap}} = -\Delta V = +\vec{E} \cdot \vec{d}$$

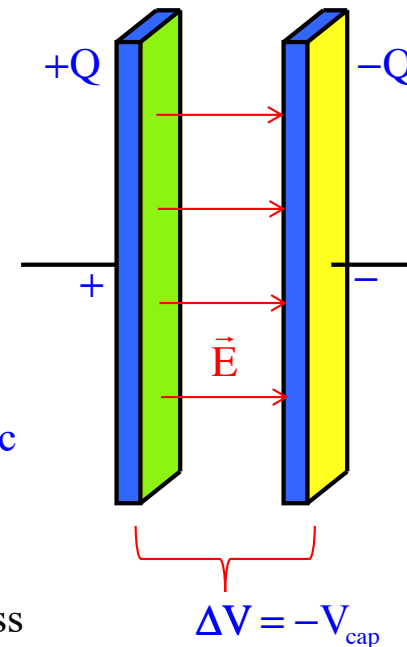
This observation is going to be important shortly!



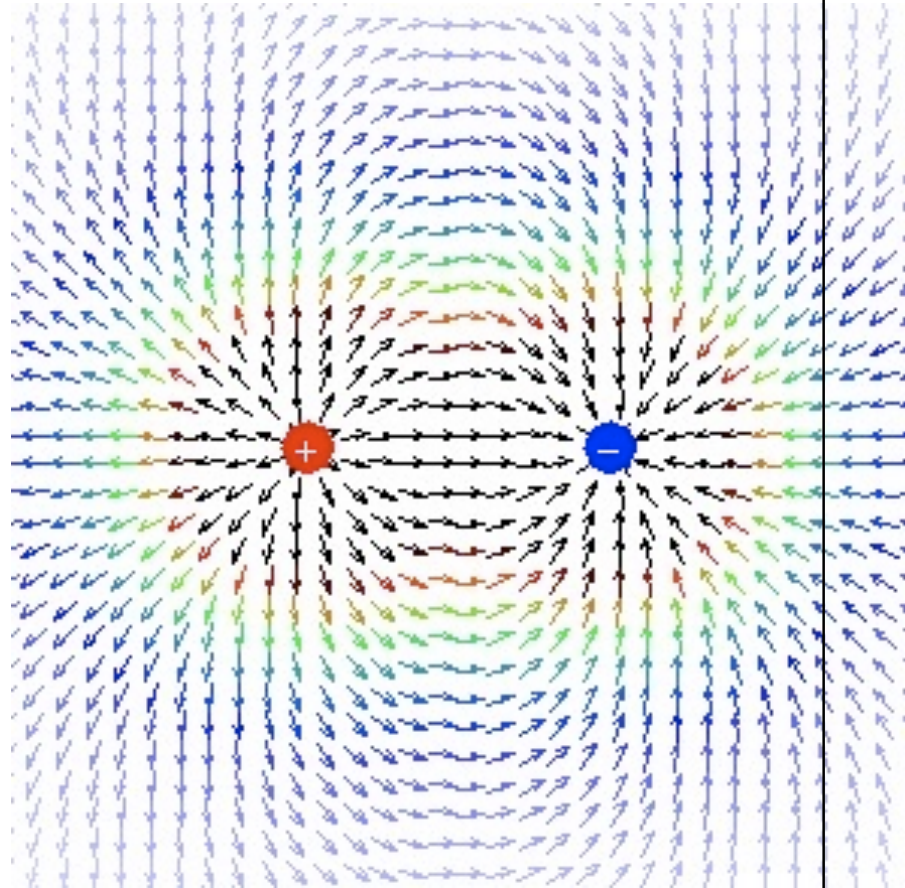*Example 1* (courtesy of Mr. White)

What is the capacitance of this system, where each conductor has a charge of +/- 3 Coulombs, and a 9-Volt potential exists between the two conductors?

$$\begin{aligned} C &= \frac{Q_{\text{on one plate}}}{V_{\text{across plates}}} \\ &= \frac{3 \text{ C}}{9 \text{ V}} \\ &= .33 \text{ farads} \end{aligned}$$




*Example 2* (courtesy of Mr. White)

*Two conducting plates* have a charge of **1.2 mC** on each, with a **6.00-V** potential difference between the two of them. What is the capacitance of this system?


*The only thing* tricky about this problem is that everything has to be in MKS—electrical potential in *volts* and charge in *coulombs*. Sooo . . .

$$\begin{aligned} C &= \frac{Q_{\text{on one plate}}}{V_{\text{across plates}}} \\ &= \frac{1.2 \times 10^{-3} \text{ C}}{6 \text{ V}} \\ &= 2 \times 10^{-4} \text{ farads} \quad (= .200 \text{ mf or } 200 \mu\text{f}) \end{aligned}$$

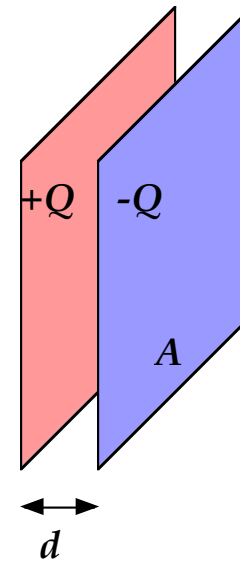*Note:* Clearly you need to become familiar with the prefixes (and symbols) for **milli**, **micro**, **nano** and **picofarads**.




## Demo :Parallel Plate Capacitor

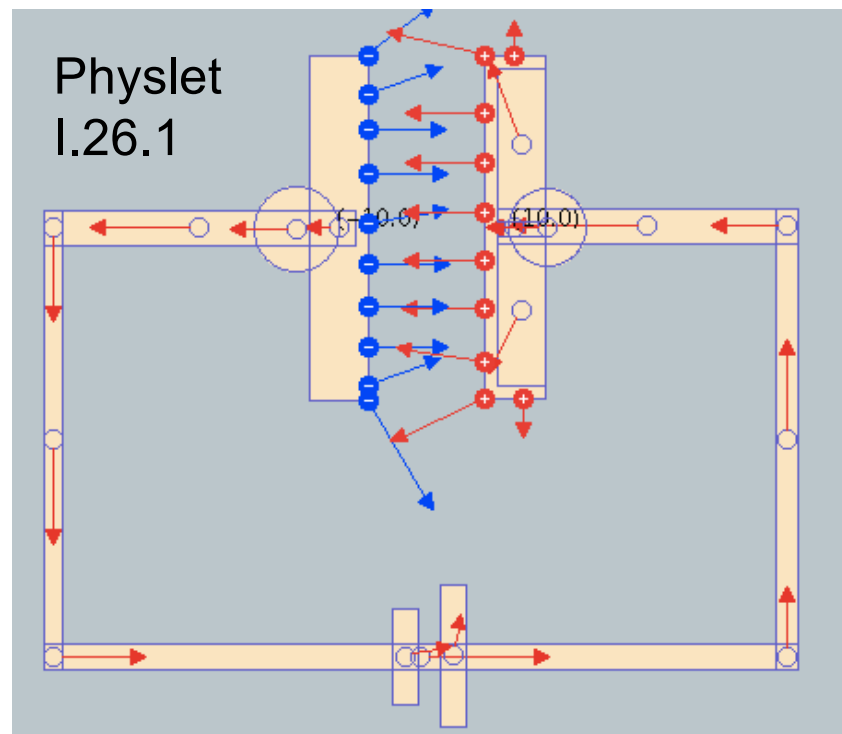
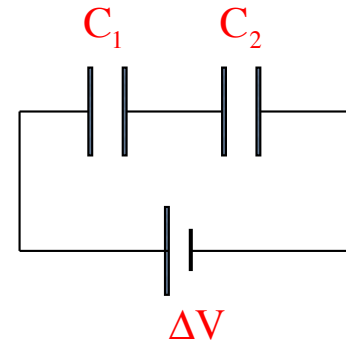
## Series Combinations

*In a series* combination of circuit elements, each element is attached to its neighbor on one side only. What is **common to all series combinations** is **current** (i.e., the **amount of charge that passes through the element per unit time**).



*Think back to how* uncharged capacitors work in electrical circuits. A battery provides a **voltage difference** across its terminals which generates a voltage difference between its **+ terminal** and the left plate (in the circuit above) of  $C_1$ . As such, **charge begins to accumulate** on that plate **electrostatically repulsing like charge off its right plate**.

*In a series combination*, the **repulsed charge from the right plate moved to the next capacitor**, depositing itself on that cap's left plate, **electrostatically repulsing like charge off its right plate** . . . which proceeds back to the battery (hence a complete circuit).

*What's common* in the **series combo of caps**, then, is “*the charge*” on each cap.

## Capacitors in Series

We know the total voltage-change across the battery, and hence across the capacitors, is  $\Delta V$ . Logic additionally dictates that:

$$\Delta V = \Delta V_{C_1} + \Delta V_{C_2}$$



We know, though, that:  $C = \frac{q}{\Delta V} \Rightarrow \Delta V_{C_1} = \frac{q}{C_1}$

If we had a single, equivalent capacitance  $C_{eq}$  that could take the place of the series combination (i.e., a cap that would draw the same charge  $q$  for the same battery voltage  $\Delta V$ ), we could write:

$$\Delta V = \frac{q}{C_{eq}}$$

In other words for a series combination of capacitors:

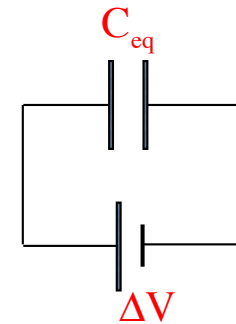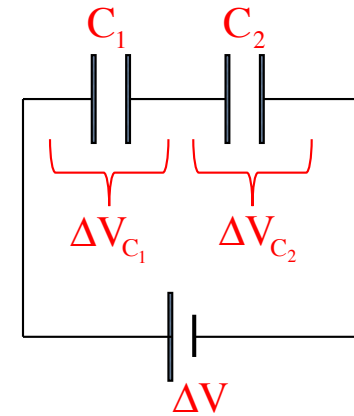Bottom line: 
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$



$$\Delta V = \Delta V_{C_1} + \Delta V_{C_2}$$

$$\frac{q}{C_{eq}} = \frac{q}{C_1} + \frac{q}{C_2}$$

$$\Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

# Capacitors in Parallel

Unlike series combinations, each element in a parallel combination attaches to its neighbors in two places.



What is common in a parallel combination is the voltage drop across each element.

So in the parallel combination of capacitors shown, charge will leave the battery and distribute itself between the two initially uncharged capacitors in such a way that the voltage across each cap is the same. If  $q_{\text{total}}$  is the total charge drawn from the battery over a period of time:

$$q_{\text{total}} = q_{\text{on } C_1} + q_{\text{on } C_2} = q_{\text{on } C_{\text{eq}}}$$

Using  $C = q/\Delta V \Rightarrow q = C\Delta V$  and our equivalent capacitance circuit, we can write:

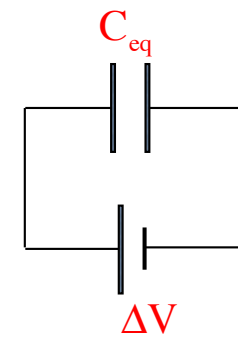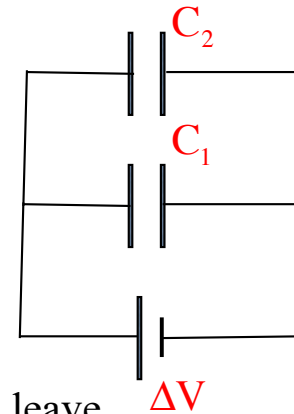Bottom line:  $C_{\text{eq}} = C_1 + C_2 + \dots$



$$\begin{aligned} q_{\text{total}} &= q_{\text{on } C_1} + q_{\text{on } C_2} \\ C_{\text{eq}} \Delta V &= C_1 \Delta V + C_2 \Delta V \\ \Rightarrow C_{\text{eq}} &= C_1 + C_2 \end{aligned}$$


**Example 7:** Derive an expression

for, then determine the equivalent capacitance of the capacitor combination shown to the right. Assume all the capacitors are  $C = 4 \mu\text{f}$ .

--This is essentially a series combination—three caps in series with a parallel combination (remember, what makes a series combo—each element is connected to its neighbor at one place).

--For the three series caps: Technically, we should write:

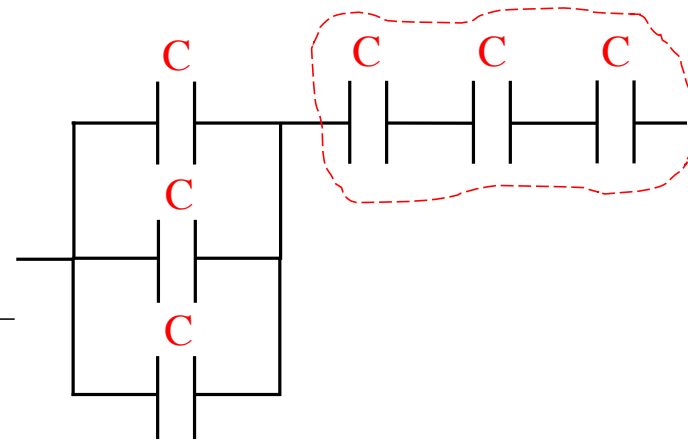**BIG NOTE:** When you have equal-sized caps  $C$  in series, the equivalent capacitance equals  $C$  divided by the number of caps in the combination (look at our problem for confirmation!).




$$\begin{aligned} \frac{1}{C_{\text{eq},1}} &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{C} + \frac{1}{C} + \frac{1}{C} \\ \Rightarrow \frac{1}{C_{\text{eq},1}} &= \frac{3}{C} \\ \Rightarrow C_{\text{eq},1} &= \frac{C}{3} \end{aligned}$$



--Redrawing:

--To continue, we need the equivalent capacitance for the parallel combination.  
As parallels just add, we get:
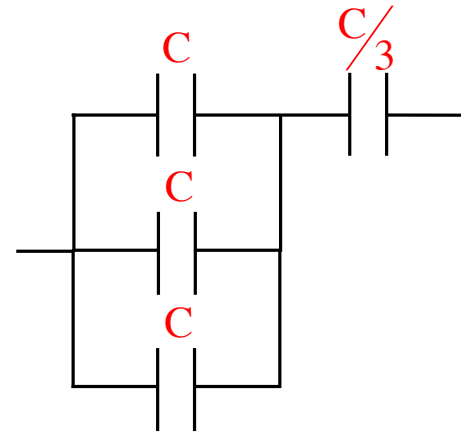
$$\begin{aligned}C_{\text{eq},2} &= C_1 + C_2 + C_2 \\ &= C + C + C \\ &= 3C\end{aligned}$$




--Redrawing:

--For the final series combination:

$$\begin{aligned}\frac{1}{C_{\text{eq}}} &= \frac{1}{C_{\text{eq},1}} + \frac{1}{C_{\text{eq},2}} \\ &= \frac{1}{\left(\frac{C}{3}\right)} + \frac{1}{3C} = \frac{3}{C} + \frac{1}{3C} = \frac{9}{3C} + \frac{1}{3C} \\ \Rightarrow \frac{1}{C_{\text{eq}}} &= \frac{10}{3C}\end{aligned}$$
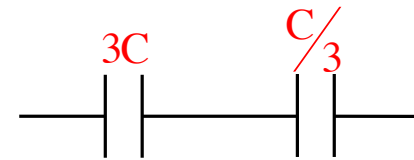
$$\Rightarrow C_{\text{eq}} = \frac{3C}{10} = \frac{3(4 \times 10^{-6} \text{ F})}{10} = 1.2 \times 10^{-6} \text{ F}$$



# Capacitors—Charging Characteristics



**Example 10:** Consider a resistor, an uncharged capacitor, a switch and a power supply all hooked in series. Note also that when the switch is thrown, the voltage across “a” and “b” is equal to both the battery voltage and the sum of voltages across the resistor and capacitor. That is:

$$V_o = V_C + V_R$$

a.) At  $t = 0$ , the switch is closed. What initially happens in the circuit?

As the cap initially has no charge on its plates, it will provide no resistance to charge flow. That means no voltage drop across the capacitor with all the voltage drop happen across the resistor . . . which means:

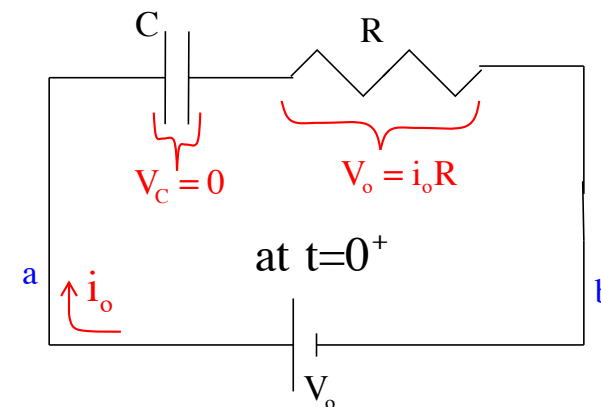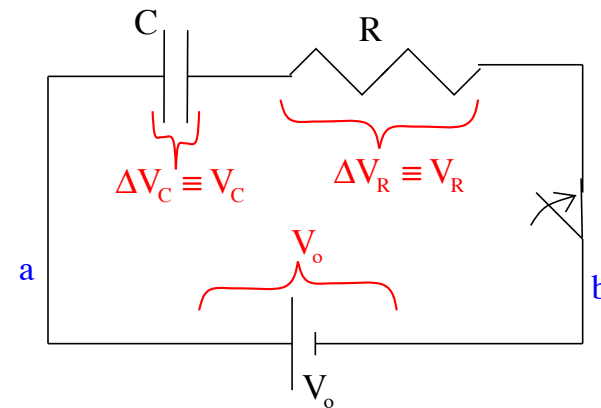
$$\begin{aligned} V_o &= \overset{0}{V_C} + V_R \\ &= i_o R \\ \Rightarrow i_o &= \frac{V_o}{R} \end{aligned}$$



b.) *What happens* as time proceeds?

*As the cap* begins to **charge**, some of the **voltage drop** happens **across the resistor** and some **across the capacitor** leaving us with a Kirchoff expression of:
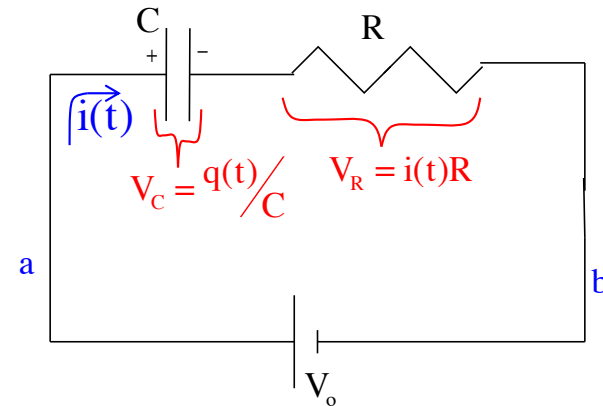
$$V_o - \frac{q_{\text{plates}}}{C} - iR = 0$$
$$\Rightarrow \frac{dq}{dt} + \frac{q_{\text{plates}}}{RC} = \frac{V_o}{R}$$




*The problem?* There are **two different types** of  $q$  in this expression. One refers to the **amount of charge on one capacitor plate**. The other refers to **charge flowing through the circuit** (current is defined as the *time rate of charge flow*).

*Although this won't* always be the case, in this instance the **rate at which charge accumulates** on the cap plates will **equal the rate at which charge passes** by per unit time, and we can write:

$$i = \frac{dq}{dt} = \frac{dq_{\text{plate}}}{dt}$$

*This means* Kirchoff's Law can be written as:
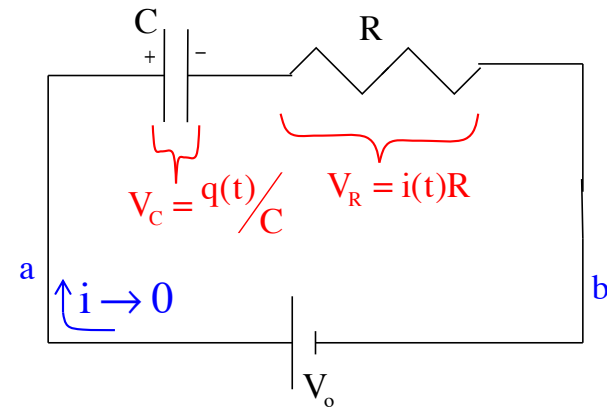
$$\frac{dq}{dt} + \frac{q_{\text{plates}}}{RC} = \frac{V_o}{R}$$
$$\Rightarrow \frac{dq_{\text{plate}}}{dt} + \frac{q_{\text{plates}}}{RC} = \frac{V_o}{R}$$



*Note that as time proceeds* toward infinity, the **charge** on the capacitor plates reaches maximum, all the **voltage drop** happens **across the capacitor**, current in the circuit drops to zero and there is no voltage drop **across the resistor**. In that case:

$$V_o = V_C + V_R \xrightarrow{0}$$
$$= \frac{Q_{\text{max}}}{C}$$
$$\Rightarrow Q_{\text{max}} = V_o C$$

*Solving:*

$$\frac{dq}{dt} + \left(\frac{1}{RC}\right)q = \frac{V_o}{R}$$

$$\Rightarrow \frac{dq}{dt} = \left(\frac{1}{RC}\right)(V_o C - q) = \left(\frac{1}{RC}\right)(Q_{\max} - q)$$

$$\Rightarrow \frac{dq}{(q - Q_{\max})} = -\frac{dt}{RC}$$

$$\Rightarrow \int_0^{q(t)} \frac{dq}{(q - Q_{\max})} = -\int_{t=0}^t \frac{dt}{RC} \Rightarrow \ln|q - Q_{\max}| \Big|_{q=0}^{q(t)} = -\frac{t}{RC}$$

$$\Rightarrow \ln|q(t) - Q_{\max}| - \ln|-Q_{\max}| = -\frac{t}{RC} \Rightarrow \ln(Q_{\max} - q(t)) - \ln(Q_{\max}) = -\frac{t}{RC}$$


$$\Rightarrow \ln\left[\frac{(Q_{\max} - q(t))}{(Q_{\max})}\right] = -\frac{t}{RC} \Rightarrow e^{\ln\left(\frac{Q_{\max} - q(t)}{(Q_{\max})}\right)} = e^{-\frac{t}{RC}}$$

$$\Rightarrow \frac{(Q_{\max} - q(t))}{(Q_{\max})} = e^{-\frac{t}{RC}} \Rightarrow Q_{\max} - q(t) = Q_{\max} e^{-\frac{t}{RC}} \Rightarrow q(t) = Q_{\max} \left(1 - e^{-\frac{t}{RC}}\right)$$

because  $|a - b| = (b - a)$   
if  $b > a$ .
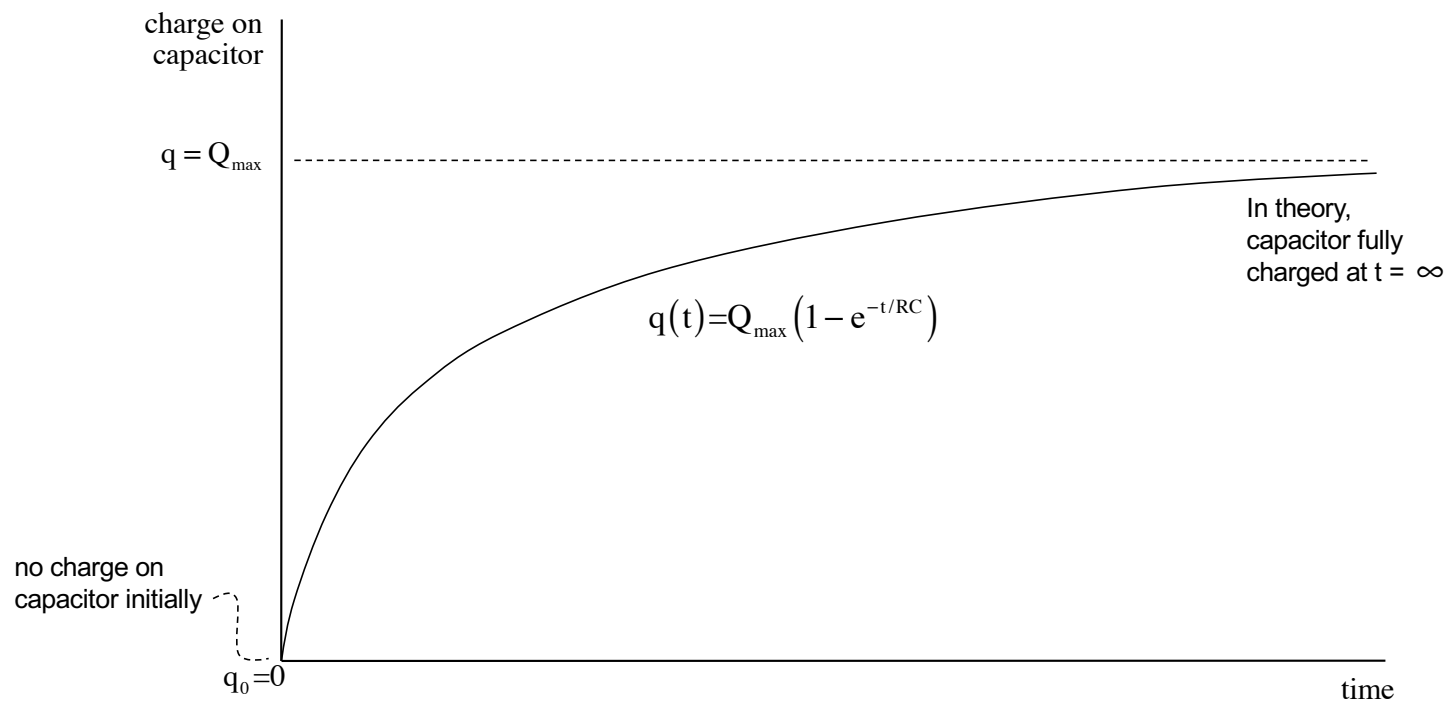
# Time Constant for a Capacitor


A graph of the *charging* characteristic of a charging capacitor is shown below.



*It would* be nice to get a feel for how fast a capacitor/resistor combination will charge or discharge.

*To that end*, how much charge would the cap have accumulated after a time equal to  $RC$ ?

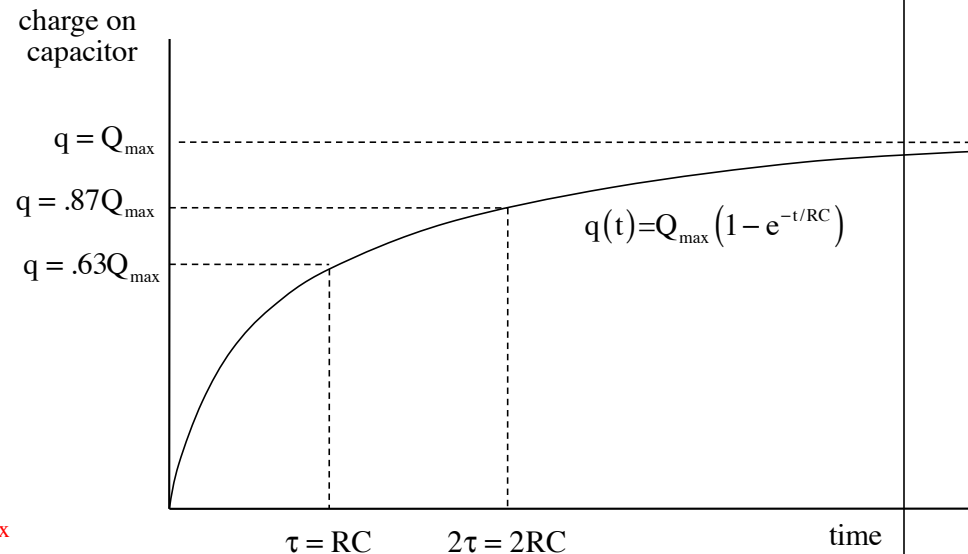
$$\begin{aligned} q(t=RC) &= Q_{\max} \left( 1 - e^{-\frac{RC}{RC}} \right) \\ &= Q_{\max} (1 - e^{-1}) \\ &= Q_{\max} \left( 1 - \frac{1}{e} \right) \\ &= Q_{\max} (1 - .37) = .63Q_{\max} \end{aligned}$$



*This time* is defined as *one time constant*  $\tau$ . It is the amount of time it takes the capacitor to charge to 63% of its maximum. *Two time constants* will charge it to 87% of its maximum (try the calculation if you don't believe me).

c.) *What is* the *current* as a function of time?
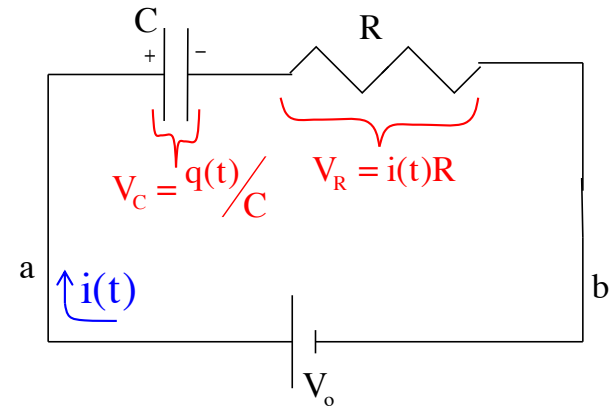
$$\begin{aligned} i(t) &= \frac{dq_{\text{plate}}}{dt} \\ &= \frac{d(Q_{\text{max}} - Q_{\text{max}} e^{-t/RC})}{dt} \\ &= -Q_{\text{max}} \left( -\frac{1}{RC} \right) e^{-t/RC} \\ &= \left( \frac{1}{R} \right) \left( \frac{Q_{\text{max}}}{C} \right) e^{-t/RC} \\ &= \left( \frac{V_o}{R} \right) e^{-t/RC} \\ &= i_o e^{-t/RC} \end{aligned}$$





A graph of the *current* characteristics for a charging capacitor/resistor combination:

Note that after *one time constant*, the current is:

$$\begin{aligned} i(t=RC) &= i_o e^{-\frac{RC}{RC}} \\ &= \frac{i_o}{e} \\ &= .37i_o \end{aligned}$$

current for  
charging  
capacitor

$$i_o = \frac{V_o}{R}$$

$$i(t) = i_o e^{-t/RC}$$

$$i = .37i_o$$

$$i = .13i_o$$

$$\tau = RC$$

$$2\tau = 2RC$$

time

After *one time constant*, the capacitor's current will have dropped 63% and will be at 37% of its maximum. After *two time constants*, it will be at 13% of its maximum.

# Capacitors—Discharging Characteristics

*Example 11:* At  $t = 0$ , the switch is thrown and a charged capacitor begins to discharge.

a.) How are current through the circuit and charge on the capacitor plates related?

When a capacitor is discharging, the rate of change of charge on the plate is **negative** (charge is leaving) and:


$$i = dq/dt = -\left(\frac{dq_{\text{plate}}}{dt}\right)$$

Using this with Kirchoff's Law (tracking along the direction of current flow) yields:

$$-iR + \frac{q_{\text{plates}}}{C} = 0$$

$$\Rightarrow -\frac{dq}{dt} + \frac{1}{RC}q_{\text{plates}} = 0$$
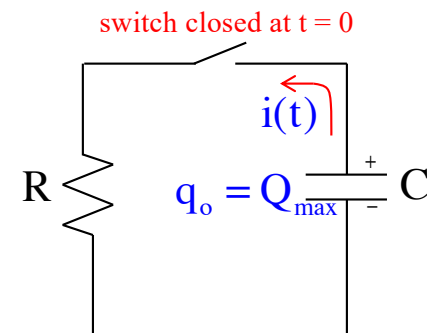
$$\Rightarrow -\left(-\frac{dq_{\text{plates}}}{dt}\right) + \frac{1}{RC}q_{\text{plates}} = 0$$



*Solving:*

$$-\left(-\frac{dq_{\text{plate}}}{dt}\right) + \left(\frac{1}{RC}\right)q_{\text{plates}} = 0$$

$$\Rightarrow \frac{dq_{\text{plate}}}{dt} = -\left(\frac{1}{RC}\right)q_{\text{plates}}$$


$$\Rightarrow \frac{dq_{\text{plate}}}{q_{\text{plate}}} = -\left(\frac{1}{RC}\right)dt$$

$$\Rightarrow \int_{Q_{\text{max}}}^{q(t)} \left(\frac{1}{q_{\text{plate}}}\right) dq_{\text{plate}} = -\left(\frac{1}{RC}\right) \int_{t=0}^t dt$$

$$\ln(q) \Big|_{Q_{\text{max}}}^{q(t)} = \ln[q(t)] - \ln(Q_{\text{max}}) = -\frac{t}{RC}$$

$$\Rightarrow \ln\left(\frac{q(t)}{Q_{\text{max}}}\right) = -\frac{t}{RC} \quad \Rightarrow \quad e^{\ln\left(\frac{q(t)}{Q_{\text{max}}}\right)} = e^{-\frac{t}{RC}}$$

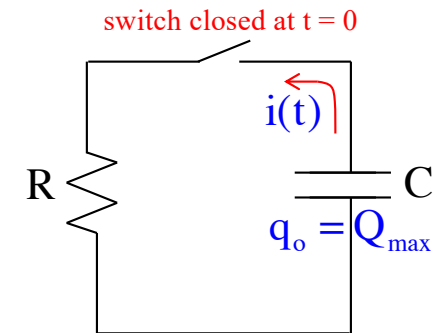
$$\Rightarrow \frac{q(t)}{Q_{\text{max}}} = e^{-\frac{t}{RC}} \quad \Rightarrow \quad q(t) = Q_{\text{max}} e^{-\frac{t}{RC}}$$



A graph of the *charge on plate characteristics* for a discharging capacitor/resistor combination:

Note that after *one time constant*, the charge is:



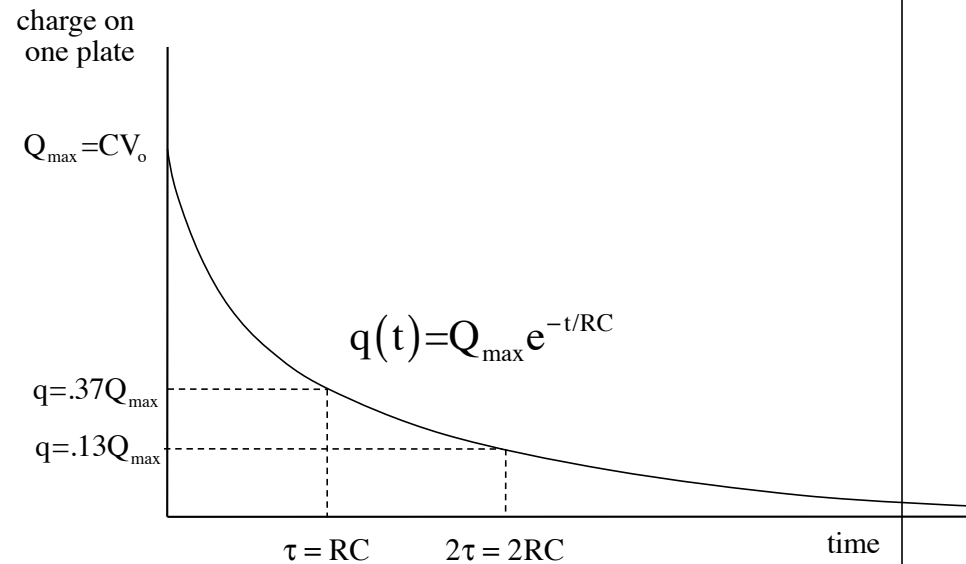
$$\begin{aligned} q(t=RC) &= Q_{\max} e^{-\frac{RC}{RC}} \\ &= \frac{Q_{\max}}{e} \\ &= .37Q_{\max} \end{aligned}$$



After *one time constant*, the capacitor's charge will have dropped **67%** and will be at **37%** of its maximum. After *two time constants*, it will be at **13%** of its maximum.
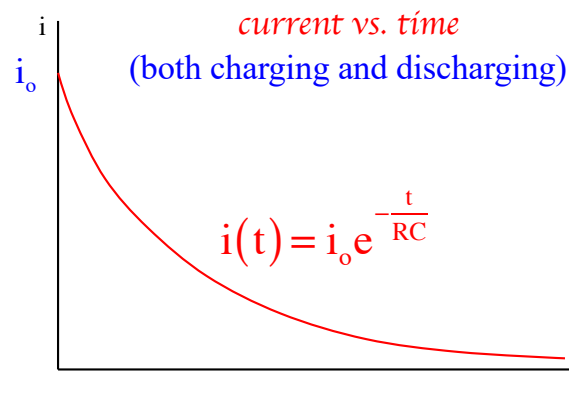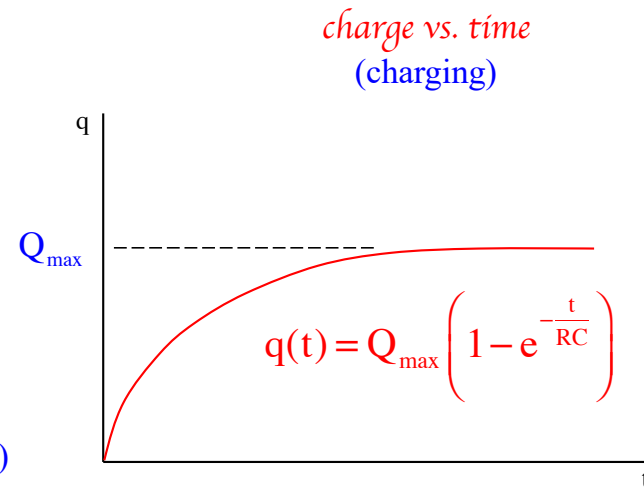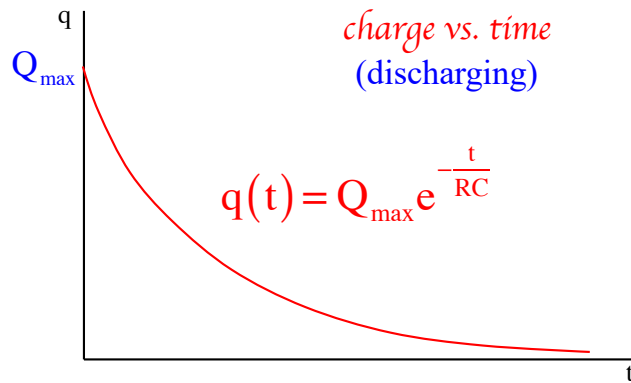
# Summary of Graphs

*Graphs* of capacitor charging and discharging characteristics.



# Dielectrics


*Consider* the **charged, parallel-plate capacitor** shown to the right (complete with its *E-field*).

*Placing an* insulating material (called a *dielectric*) between the plates does a number of things.

1.) *The dielectric* experiences a **van der Waal effect** due to its presence in the electric field between the ~~Plates~~ creates a **reverse electric field** that diminishes the net electric field across the plates (see sketch on next page).

2.) *With the net electric field* diminishing, the **net electrical potential** across the plates **goes DOWN**.  
As  $C=q/V$ , a **diminishing of V** means the **capacitance goes UP**.

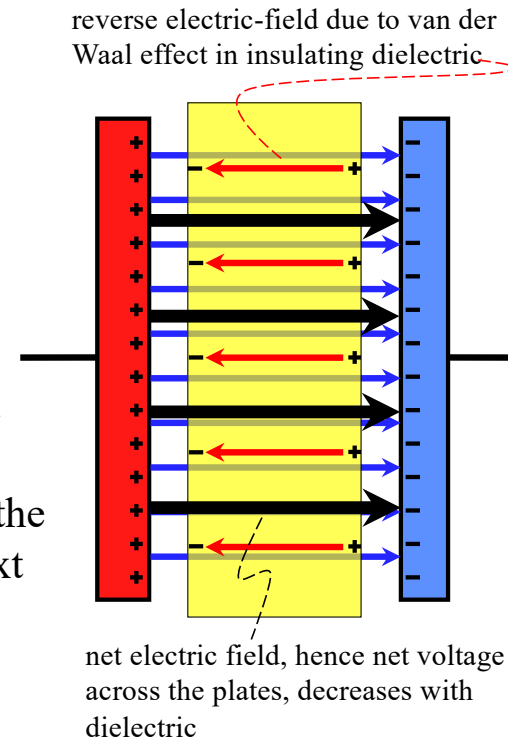3.) *Conceptually*, placing a **dielectric** between the plates effectively **allows the plates to hold more charge per unit volt**. This is why the capacitance increases when a dielectric is placed internal to the cap.



**Net effect:** For the **charged, parallel-plate capacitor** shown to the right.

1.) **The capacitance** of a capacitor **with a dielectric** between its plates will equal:

$$C_{\text{with dielectric}} = \kappa C_{\text{without dielectric}},$$

where  $\kappa$ , sometimes characterized as  $\epsilon_d$ , is the proportionality constant called the **dielectric constant**.

**Note 1:** **This means** there are **three ways** to increase a capacitor's value:

- 1.) **increase** the **plate area**.
- 2.) **bring** the **plates closer together**.
- 3.) **place** an insulating **dielectric** **between** the **plates**.

