

Problem 18.32: An uncharged cap (20 microfarads) and resistor (100 ohms) are in series with an EMF of 9 volts (if there is no internal resistance mentioned for the battery/power-supply, you can assume it is zero).

a.) What's the time constant?

b.) What's the maximum charge on the cap?

b.) After one time constant:

3.

18.33) An uncharged cap (20 microfarads) and resistor (100 ohms) are in series with an EMF of 9 volts (if there is no internal resistance mentioned for the battery/power-supply, you can assume it is zero).

a.) What's the time constant?

$$\begin{aligned}\tau &= RC \\ &= (100\Omega)(20 \times 10^{-6} \text{ F}) \\ &= 2 \times 10^{-3} \text{ seconds}\end{aligned}$$

b.) What's the maximum charge on the cap?

$$\begin{aligned}q_{\text{max}} &= CV_{\text{across cap max}} \\ &= (20 \times 10^{-6} \text{ F})(9 \text{ V}) \\ &= 1.8 \times 10^{-4} \text{ coulombs}\end{aligned}$$

b.) After one time constant:

$$\begin{aligned}q_{1\tau} &= .63q_{\text{max}} \\ &= .63(1.8 \times 10^{-3} \text{ C}) \\ &= 1.134 \times 10^{-3} \text{ coulombs}\end{aligned}$$

4.