

Problem 18.36

An RC circuit is powered by a 48 volt battery and has a maximum current of .5 mA. If the time constant is .96 seconds:

a.) What is the capacitance?


To begin with, the maximum current happens just as (after) the switch is thrown. Additionally, an uncharged capacitor provides no resistance to charge flow in a circuit, so just as the switch is thrown the only element that does provide resistance is the resistor. That means, according to Ohm's Law:

$$i_{\max} = \frac{V}{R}$$

$$\Rightarrow R = \frac{V}{i_{\max}}$$

$$\Rightarrow R = \frac{48 \text{ V}}{.5 \times 10^{-3} \text{ A}}$$
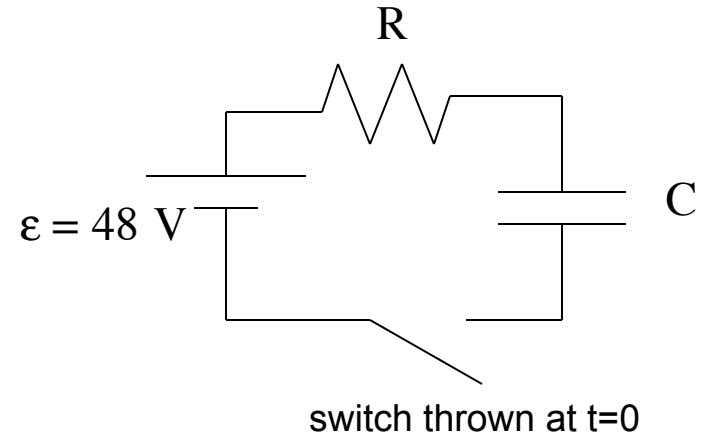
$$\Rightarrow R = 96 \times 10^3 \text{ } \Omega$$




Using the time constant and the now known resistance, we can write:

$$\tau = RC$$

$$\Rightarrow C = \frac{\tau}{R}$$

$$\Rightarrow C = \frac{.96 \text{ sec}}{96 \times 10^3 \Omega}$$
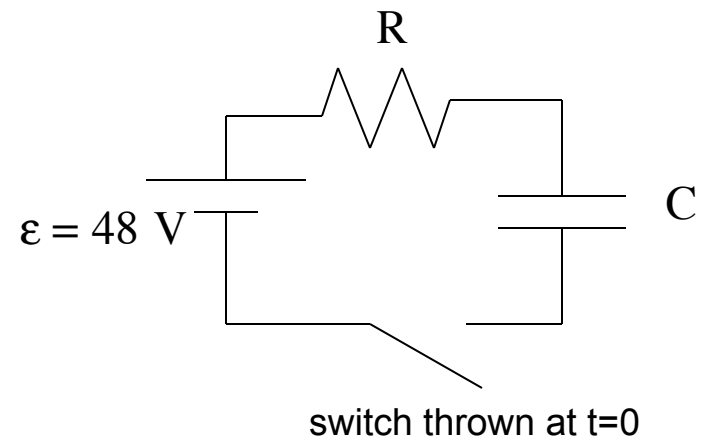
$$\Rightarrow C = 10^{-5} \text{ farads}$$



b.) 1.96 seconds is the same as two time constants. After two time constants, the charge has increased to .87 times its maximum charge. In other words:

$$\begin{aligned}q(2\tau) &= .87q_{\max} \\ &= .87CV_o \\ &= .87(10^{-5} \text{ farads})(48 \text{ V}) \\ &= 41.76 \times 10^{-5} \text{ coulombs}\end{aligned}$$

