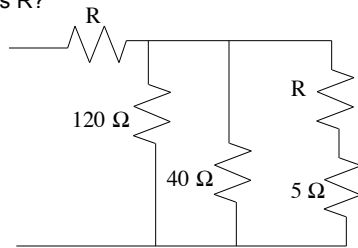


Problem 18.11

If the equivalent resistance is 75Ω , what is R ?




1.

The two series resistors have to equal 75Ω

The three branches in parallel have an equivalent resistance of:
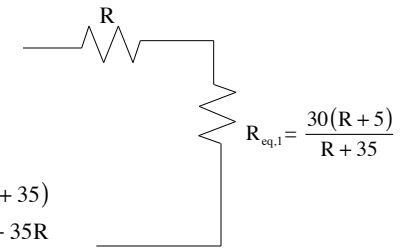
$$\begin{aligned} 75 &= \frac{30(R+5)}{R+35} + R \\ \Rightarrow 75(R+35) &= 30(R+5) + R(R+35) \\ \Rightarrow 75R + 2475 &= 30R + 150 + R^2 + 35R \\ \Rightarrow R^2 - 10R - 2475 &= 0 \\ \Rightarrow R &= 55 \Omega \end{aligned}$$



Check:


$$\begin{aligned} R_{eq} &= \left(\frac{1}{120} + \frac{1}{40} + \frac{1}{(55+5)} \right)^{-1} + 55 \\ &= 75 \Omega \end{aligned}$$

3.

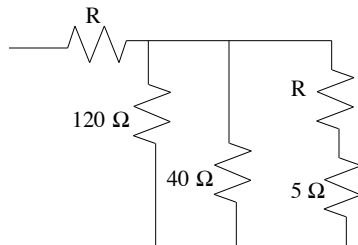18.11) If the equivalent resistance is 75Ω , what is R ?

The three branches in parallel have an equivalent resistance of:

$$\begin{aligned} \frac{1}{R_{eq,1}} &= \frac{1}{120} + \frac{1}{40} + \frac{1}{(R+5)} \\ &= \frac{1}{120} + \frac{3}{120} + \frac{1}{(R+5)} \\ &= \frac{1}{30} + \frac{1}{(R+5)} \\ &= \frac{R+5}{30(R+5)} + \frac{30}{30(R+5)} \\ &= \frac{R+35}{30(R+5)} \\ \Rightarrow R_{eq,1} &= \frac{30(R+5)}{R+35} \end{aligned}$$



2.