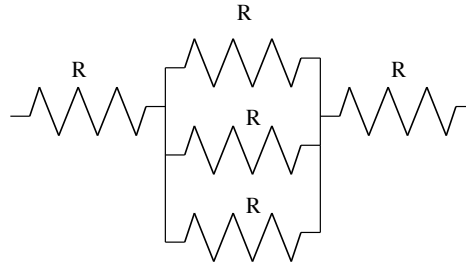


## Problem 18.7

a.) Equivalent resistance?




1.)
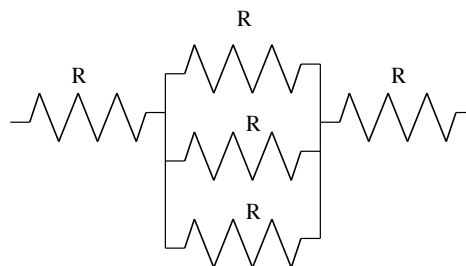
## Problem 18.7

a.) Equivalent resistance?

This is, in general, a series combination (the two R's in series with the three parallel R's). What's interesting here is that IF THE RESISTANCE VALUES ARE THE SAME in a parallel combination, the equivalent resistance for the combination will be the single resistance value divided by the number of resistors in the combination. That is:



For 2 R's in parallel:

$$\begin{aligned}\frac{1}{R_{\text{eq}}} &= \frac{1}{R} + \frac{1}{R} \\ &= \frac{2}{R} \\ \Rightarrow R_{\text{eq}} &= \frac{R}{2}\end{aligned}$$

For 4 R's in parallel:

$$\begin{aligned}\frac{1}{R_{\text{eq}}} &= \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \\ &= \frac{4}{R} \\ \Rightarrow R_{\text{eq}} &= \frac{R}{4}\end{aligned}$$

Etc.

Using this information, we can automatically write:

$$\begin{aligned}R_{\text{eq}} &= R + \frac{R}{3} + R \\ &= 2.33R\end{aligned}$$

2.)