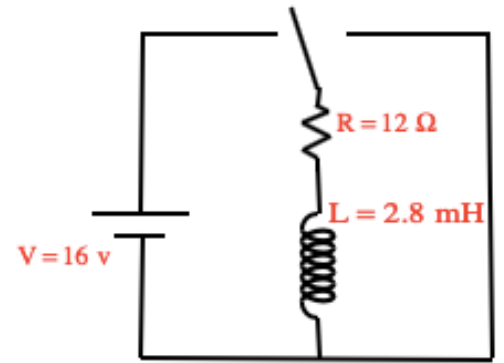


RL circuit in DC setting:

A $12\ \Omega$ resistor is in series with a $2.8\ \text{mH}$ inductor whose internal resistance is negligible. The two are in a circuit that has a switch that can connect the two to a $16\ \text{V}$ battery, or can be toggled so as to connect the two to themselves alone.



- a.) At $t = 0$, the switch is toggled to the left connecting the resistor and inductor to the power supply. What is the initial current in the circuit?

- b.) After a long period of time, what is the current in the circuit?

- c.) What is the circuit's time constant?

- d.) What does the time constant tell you?

After a long period of time, the switch is toggled to the right.

- e.) What will the current in the circuit do as time proceeds?