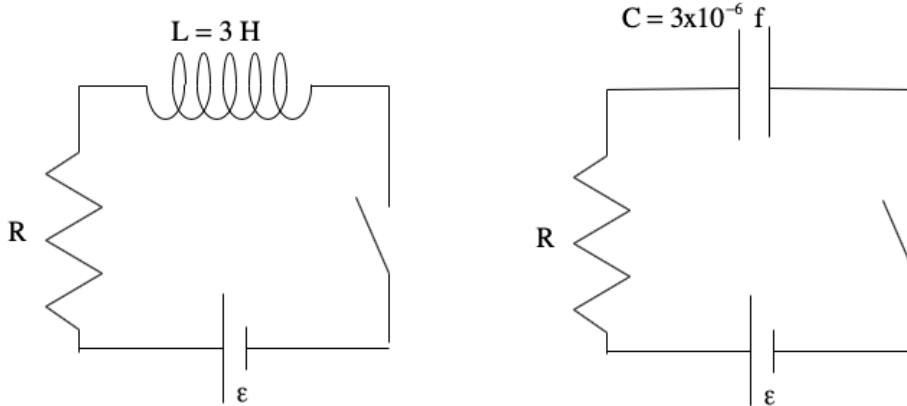



Chapter 20 and 21—XtraWrk—AC Circuits

20.44) If the time constants are the same for the RC and RL circuits shown below, what must R be?



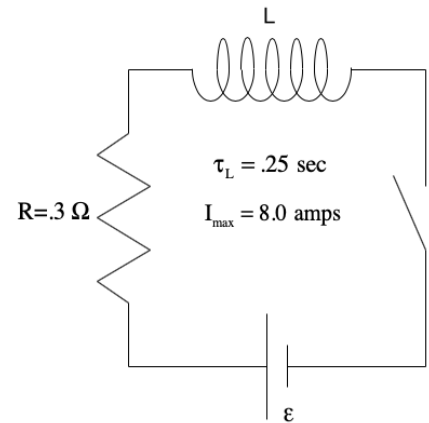
20.45) For the circuit shown to the right, determine:

- the battery voltage.
- the inductance in the circuits.
- the current after one time constant.
- the voltage across the resistor after one time constant.
- the voltage across the inductor after one time constant.



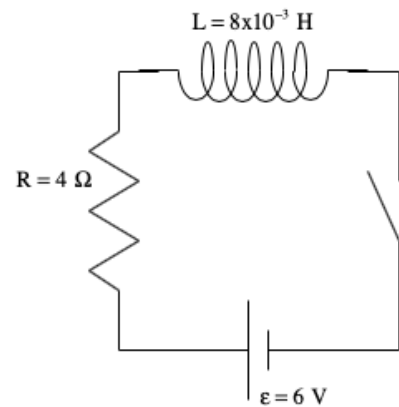
20.48) For the circuit, determine:

- what is the time constant?
- what is the current in the circuit after two-hundred fifty microseconds (250×10^{-6})?
- what is the final steady-state current?
- how long does the current take to reach 80% of its maximum value?



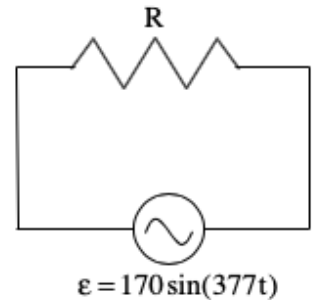21.1) A lightbulb uses an average power of 75 W.

- What is the resistance if used in the circuit to the right?
- What is its resistance if the bulb is 100 W?




21.2) 60 W bulb operates at 60 Hz when the AC power supply has an RMS rating of 120 volts.

- What is the peak (maximum) voltage applied to the bulb?
- What is the resistance of the bulb?
- Does a 100 W bulb have a greater or lesser resistance than the 60 W bulb?


RC #1) Consider the RC circuit shown to the right.

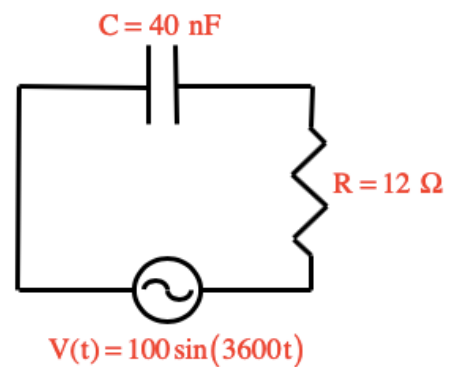- What is the RMS value of the power supply?
- At what frequency is the power supply acting?
- What is the circuit's capacitive reactance?
- What is the circuit's impedance/
- What is the circuit's current?



RL #1) Consider the RL circuit shown to the right.

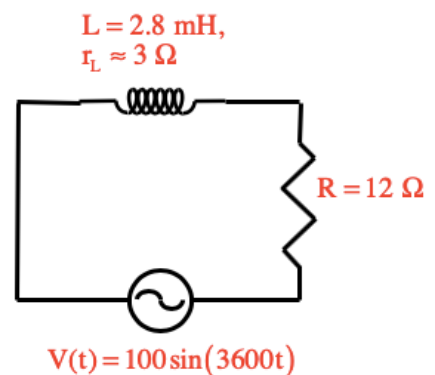- What is the circuit's inductive reactance?
- What is the circuit's impedance?
- What is the circuit's current?



RLC #1) Consider the RLC circuit shown to the right.

- What is the circuit's impedance?
- What is the circuit's current?
- What is the circuit's resonance frequency?

