


### 3.) RLC circuit:

Consider the RLC circuit shown to the right.

a.) What is the circuit's impedance?

b.) What is the circuit's current?

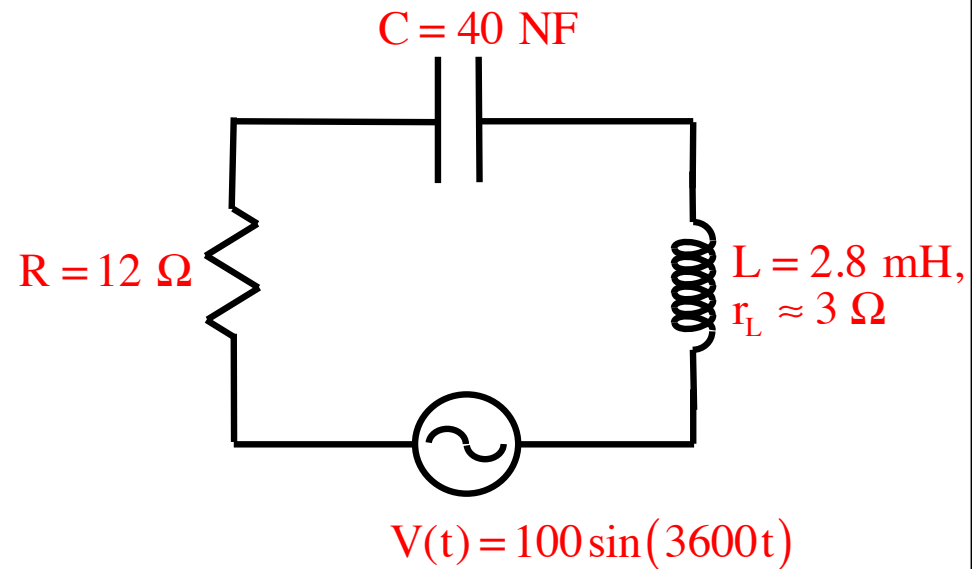c.) What is the circuit's resonance frequency?




### 3.) RLC circuit:

Consider the RLC circuit.

a.) What is the circuit's impedance?
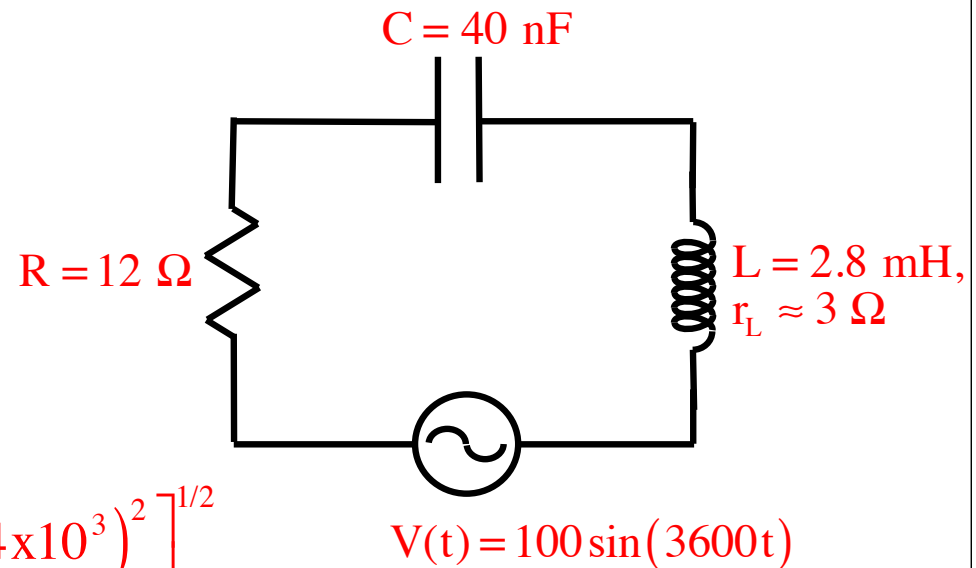
$$Z = \left[ (R + r_L)^2 + (X_L - X_C)^2 \right]^{1/2}$$
$$= \left[ (12 \Omega + 3 \Omega)^2 + (1.76 \times 10^{-2} - 6.94 \times 10^3)^2 \right]^{1/2}$$
$$= 6.94 \times 10^3 \Omega$$



b.) What is the circuit's resonance frequency?

$$v = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \frac{1}{2\pi} \sqrt{\frac{1}{(2.8 \times 10^{-3} \text{ H})(40 \times 10^{-9} \text{ F})}}$$
$$= 1.5 \times 10^3 \text{ Hz}$$

c.) What is the circuit's current at the resonance frequency?

As the *inductive reactance* and *capacitive reactance* add to zero at resonance, the current will simply be due to the circuit's frequency independent resistor-like resistance, or:

$$i_{\text{RMS}} = \frac{V_{\text{RMS}}}{R_{\text{net}}} = \frac{(70.7 \text{ V})}{(15 \Omega)}$$
$$= 4.71 \text{ A}$$