

Ch 26 - Capacitance



Photo: Hannes Grobe, Wikimedia

Review

$$F = k \frac{q_1 q_2}{r^2}$$

- *Electric Fields*

Exist in the presence of charged particles, apply forces to other charges

$$E = \frac{F}{q_0}$$

- *Gauss's Law*

Can be used to determine electric field in certain situations

$$\Phi = \oint E \cdot dA = \frac{q_{in}}{\epsilon_0}$$

- *Electric Energy*

Measure of how much work it takes to move charges through electric fields

$$U = - \int F \cdot dr = - \int qE \cdot dr$$

$$\Delta V = \frac{\Delta U}{q}$$

- *Electric Potential*

Measure of how much *energy per unit charge* it takes to move through fields

$$V = \int k \frac{dq}{r}$$

$$V = - \int E \cdot ds$$

$$E = - \frac{dV}{dr}$$

What's Next


- *Capacitance*
One week unit that has both theoretical and practical applications
- *Current & Resistance*
Moving charges, finally!
- *Direct Current Circuits*
Practical applications of all the stuff that we've been talking about

Capacitance

Capacitance = “the ability to store charge.”


$$C \equiv \frac{Q}{\Delta V}$$
$$[\textit{Farads}] \equiv \frac{[\textit{Coulombs}]}{[\textit{Volts}]}$$

Capacitance is always positive, and is a measure of *how much charge can be stored at a given electric potential.*

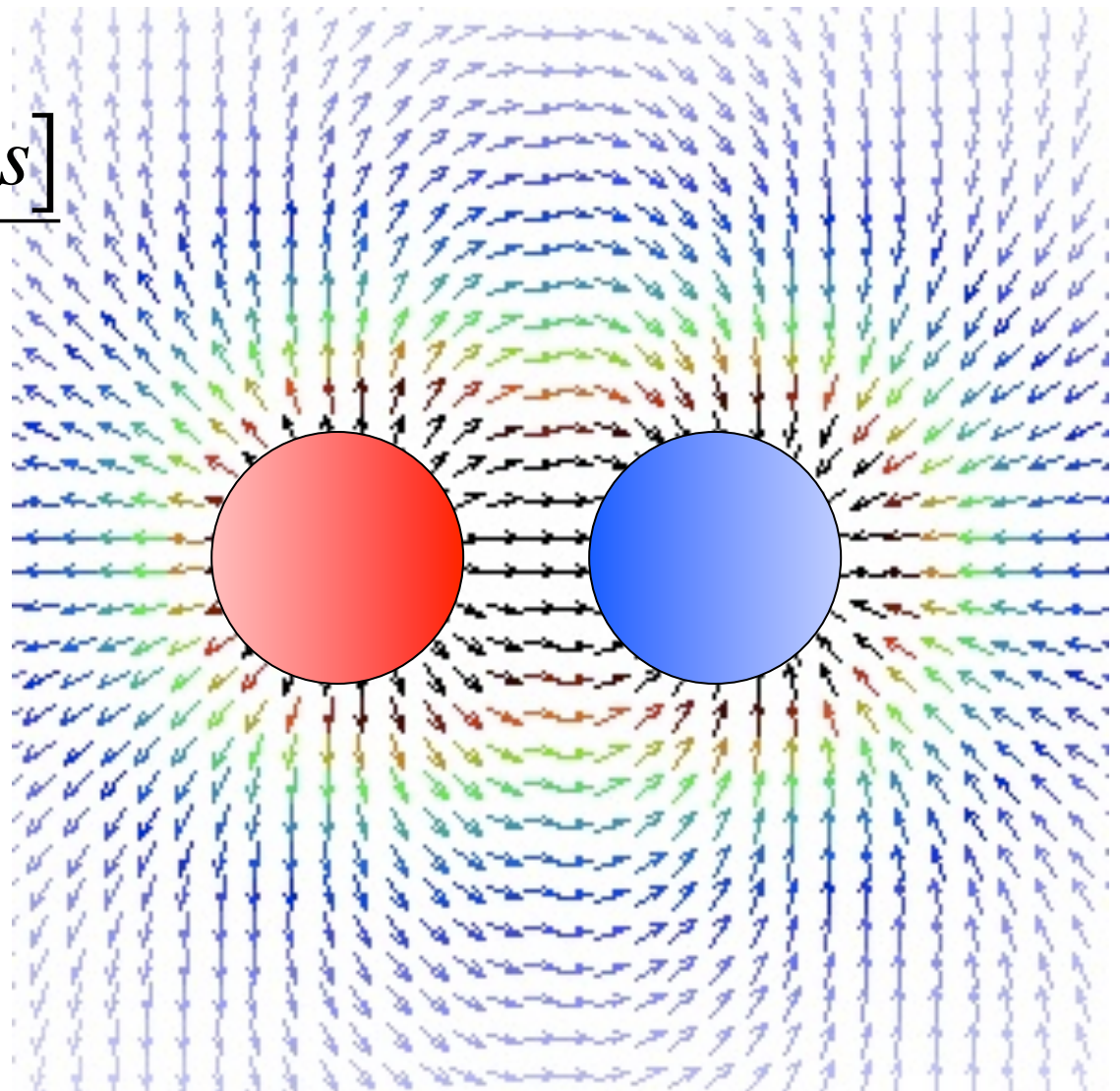

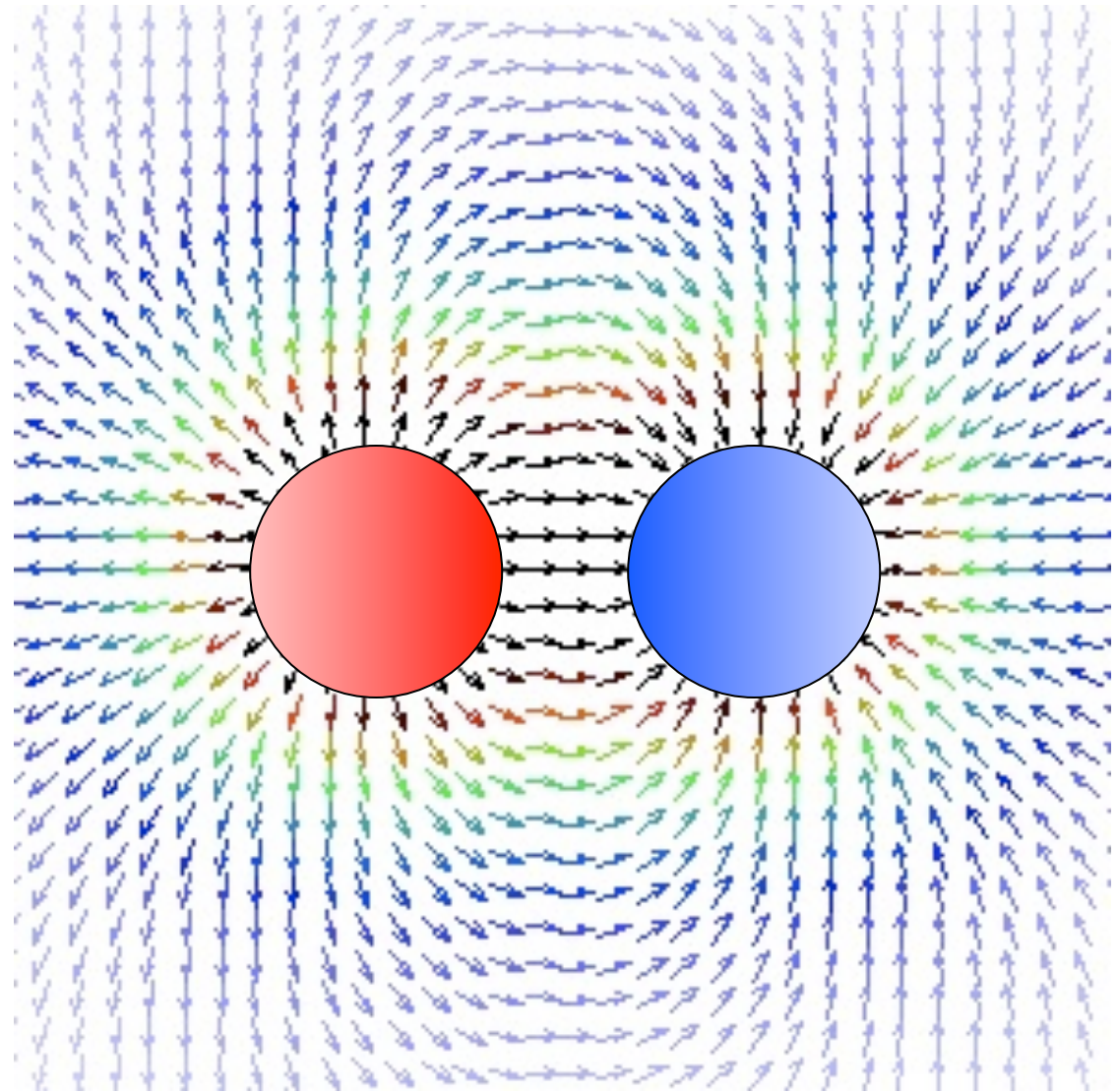
Example 1

What is the capacitance of this system, where each conductor has a charge of +/- 3 Coulombs, and a 9-Volt potential exists between the two conductors?




$$C = \frac{Q}{V} = \frac{3C}{9V} = 0.33C/V = 0.33F$$

Demo I Parallel Plate Capacitor

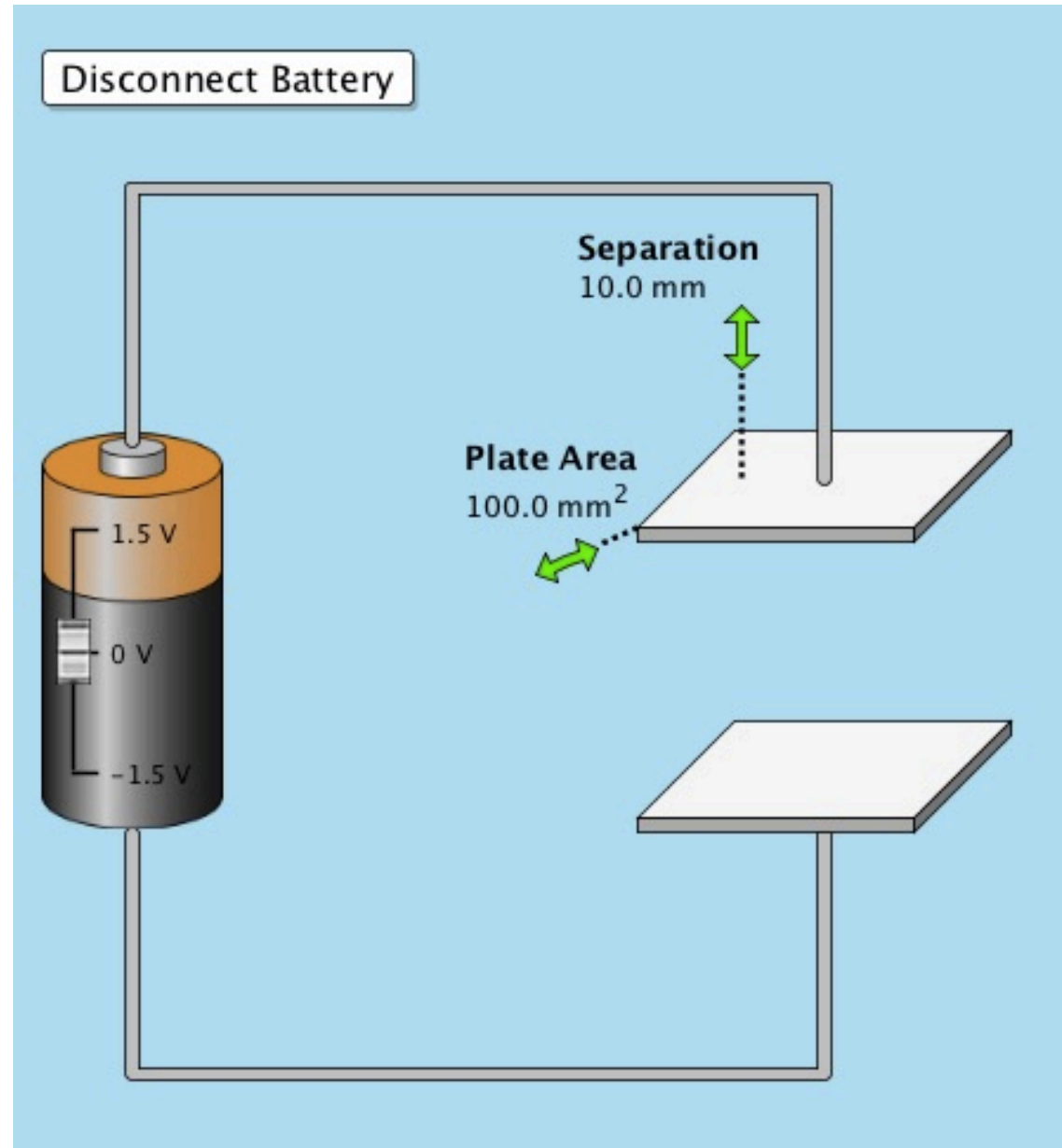

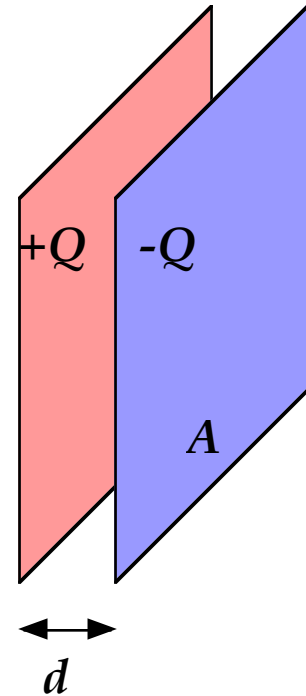Example 2


2 conducting plates have a charge of 1.2mC on each, with a 6.00-V potential difference between the two of them. What is the capacitance of this system?



$$C = \frac{Q}{V} = \frac{1.2e-3C}{6.00V} = 2.0e-4F = 200\mu F$$

Demo 2

Parallel Plate Capacitor

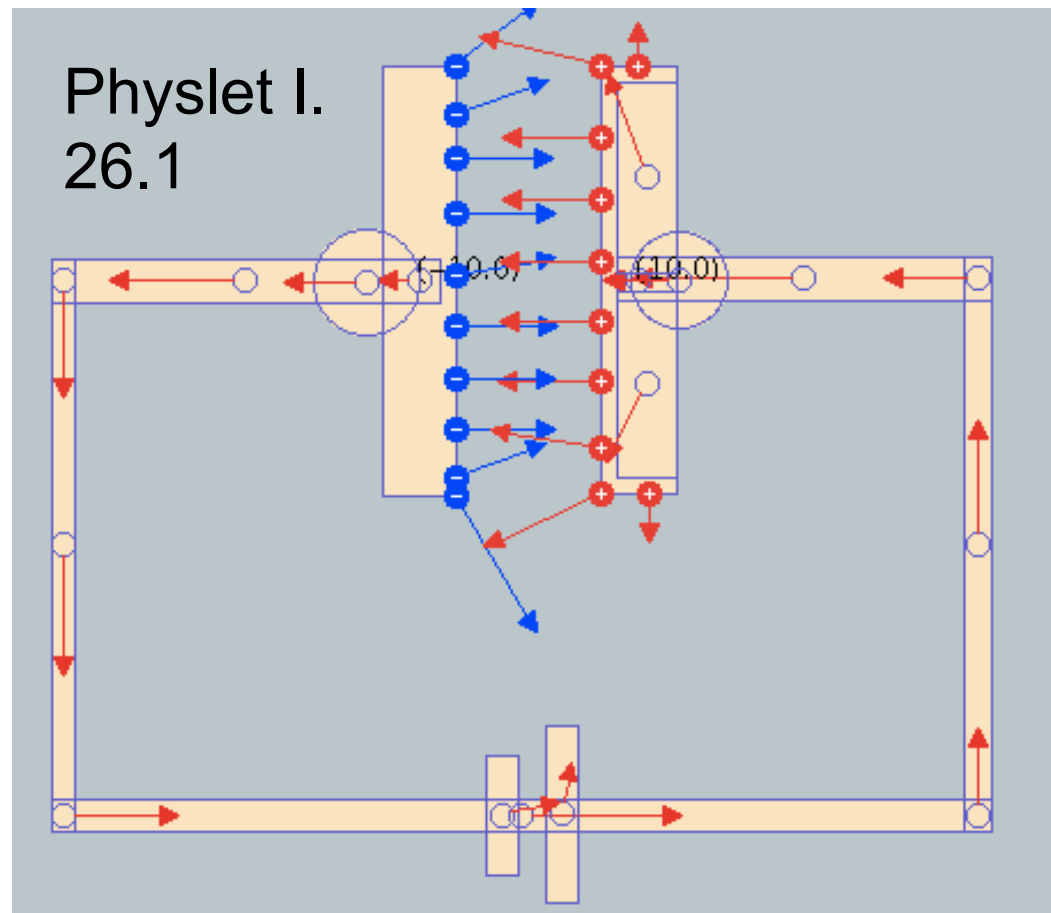


Theoretical Capacitance

Calculate the capacitance of an isolated conductor with a charge Q and radius R . (Assume that a second, concentric, hollow conductor exists with $r=\infty$.)

$$V = k \frac{Q}{R} \text{ (for this sphere, so...)}$$

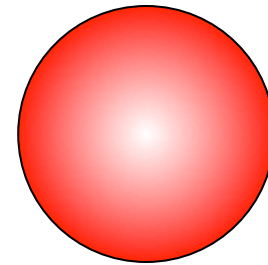
$$C = \frac{Q}{V} = \frac{Q}{k \frac{Q}{R}} = \frac{R}{k} = 4\pi\epsilon_0 R$$



Strategy


We can calculate the capacitance of other types of systems, using this basic strategy:

1. Assume a charge of magnitude Q
2. Calculate the potential V of the system (using techniques from last chapter)
3. Use $C=Q/V$ to evaluate the capacitance

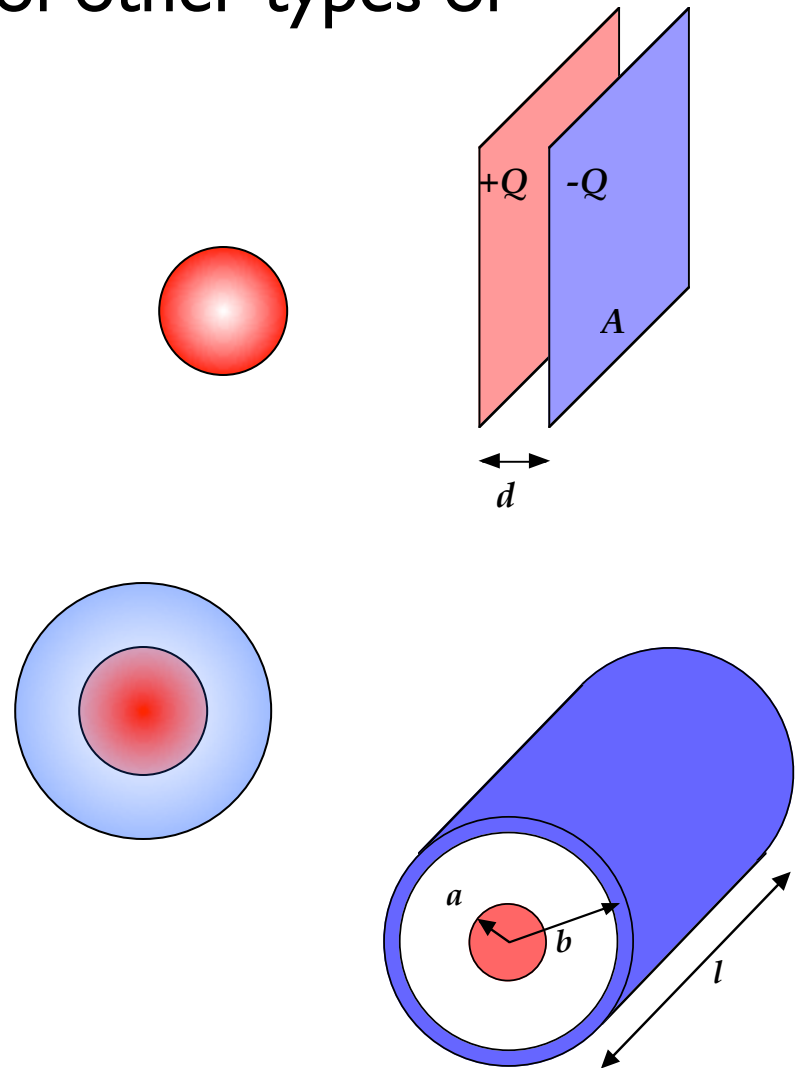

Example 3 - Parallel Plate Capacitor

Consider two parallel plates, each with area A , separated by a distance d and with equal and opposite charges on them. Assume that plates are close together compared to their area so that we can neglect the edge effects and assume that E is constant between them. Calculate the capacitance of this system.

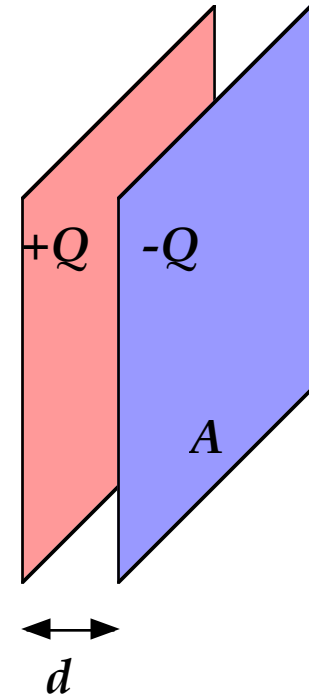

Example 3 - Parallel Plate Capacitor

$V = -Ed$ (between parallel plates)

E for a plane is...

(Using Gaussian surface):

$$\oint E \cdot dA = \frac{q_{in}}{\epsilon_0}$$


Because electric field is only on one side (why?):

$$E \cdot A = \frac{\sigma A}{\epsilon_0}$$

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$


$$V = \frac{Qd}{\epsilon_0 A}$$

$$C = \frac{Q}{V} = \frac{Q}{\frac{Qd}{\epsilon_0 A}} = \frac{\epsilon_0 A}{d}$$

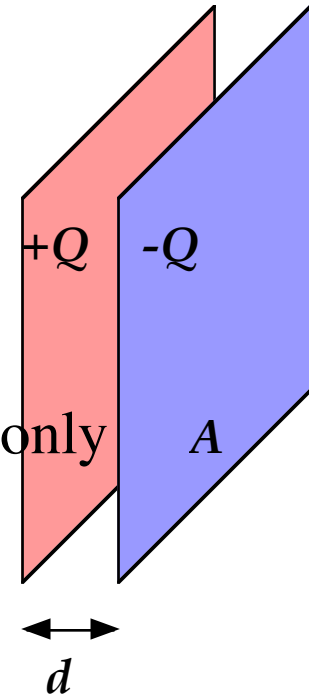

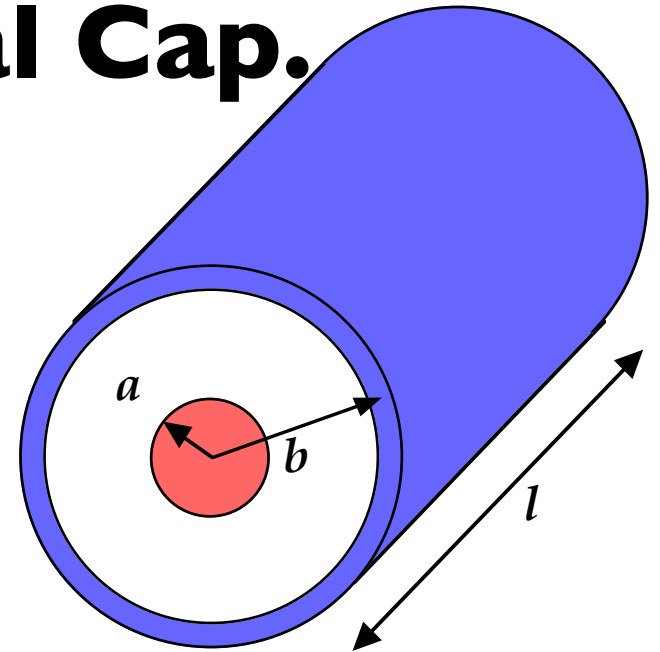Example 4 - Cylindrical Cap.

A cylindrical conductor of radius a and charge Q is coaxial with a larger cylindrical shell of radius b and charge $-Q$. Find the capacitance of the system if its length is l .



$$E = \frac{2k\lambda}{r} \quad (\text{developed using Gauss's Law})$$

$$V_a - V_b = -\int_b^a E \cdot dr$$

$$V_a - V_b = -\int_b^a \frac{2k\lambda}{r} \cdot dr$$

$$V_a - V_b = 2k\lambda \ln\left(\frac{b}{a}\right)$$

$$C = \frac{Q}{V} = \frac{l}{2k \ln\left(\frac{b}{a}\right)}$$

Example 5 - Spherical Cap.

Determine the capacitance of a spherical capacitor, with an inner sphere of radius a charged to $+Q$, and an outer sphere of radius b charged to $-Q$.

$$E = \frac{kq}{r^2} \text{ (developed using Gauss's Law)}$$

$$V_b - V_a = -\int_a^b E \cdot dr$$


$$V_b - V_a = -\int_a^b \frac{kq}{r^2} \cdot dr$$

$$V = kQ \left[\frac{a-b}{ab} \right]$$


$$C = \frac{Q}{V} = \frac{ab}{k(b-a)}$$

(Have to change sign, because C is always positive.)

Lab this week

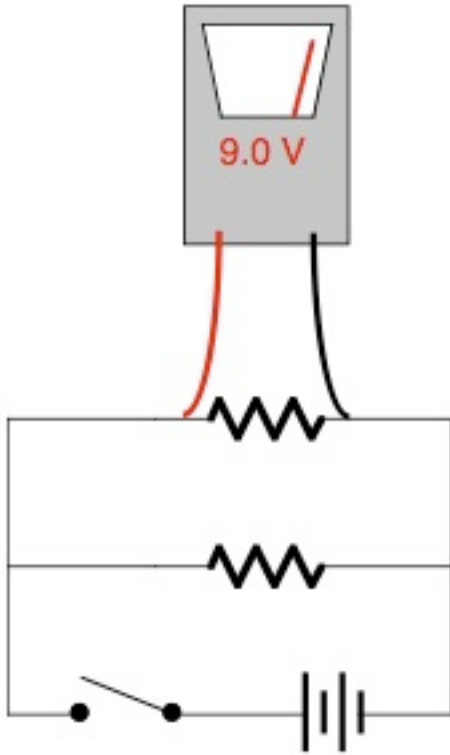


Measuring voltage

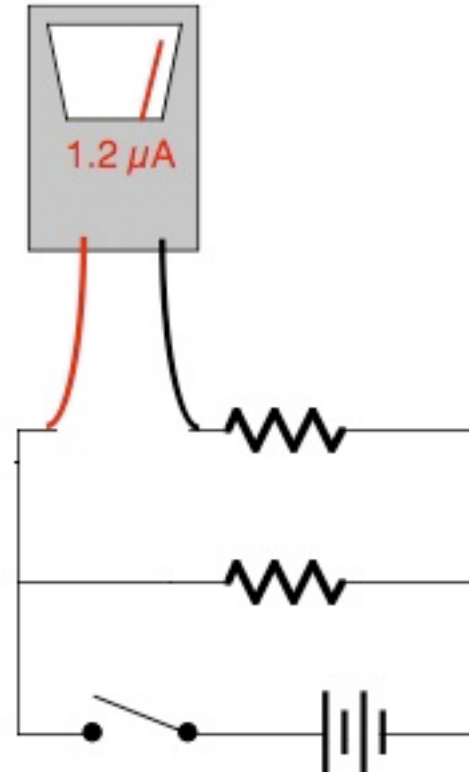

Measuring current


The Electric Battery

1780s - Galvani vs. Volta

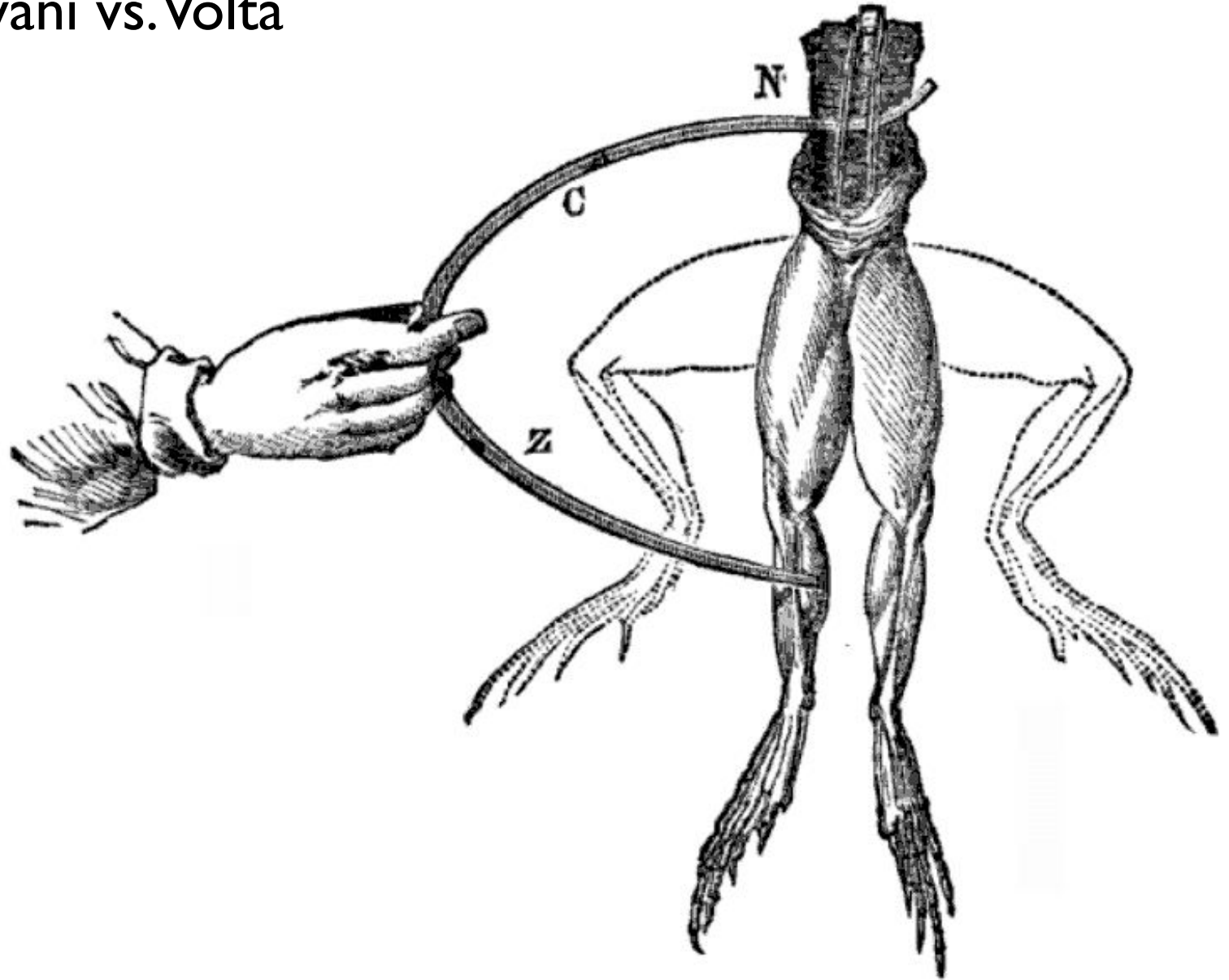


The Electric Battery

1780s - Galvani vs. Volta

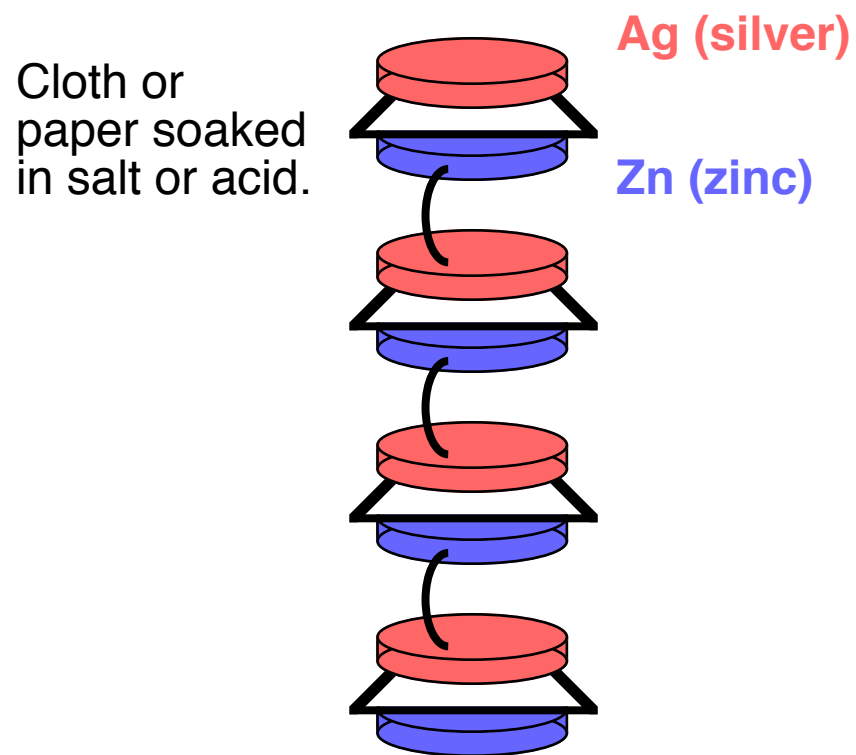


How It Works

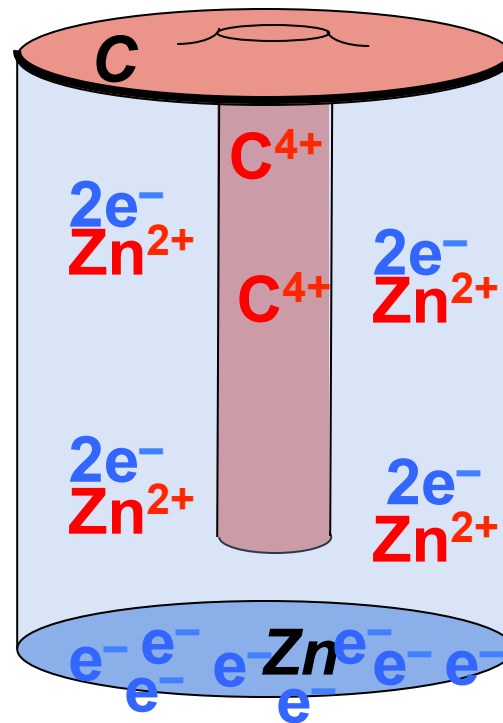Two electrodes (carbon and zinc) are immersed in a dilute acid (the electrolyte).




Charging a Capacitor

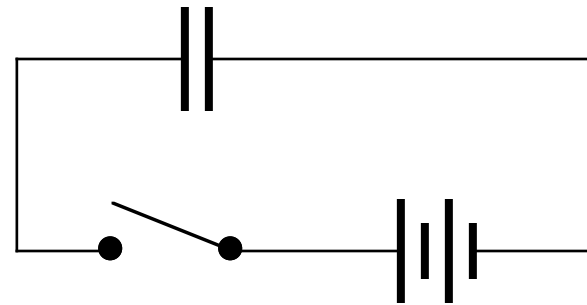If a 9V battery is connected to a 300 μF capacitor, how much charge builds up on the plates?



Capacitors in Parallel

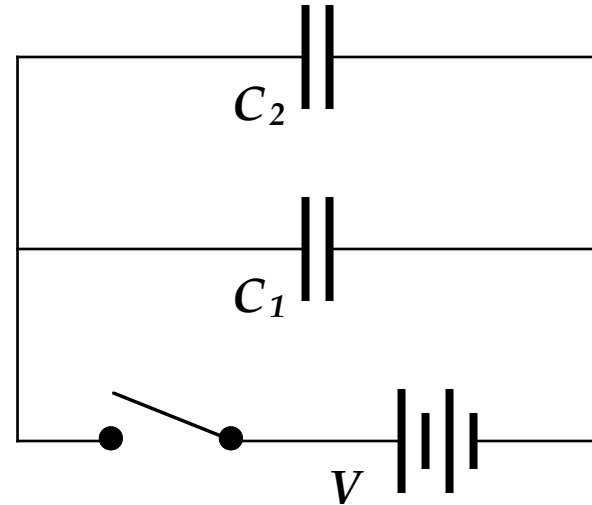
Capacitors with both of their ends connected as shown are said to be connected *in parallel*.



$$C_{\text{effective}} = C_1 + C_2$$

Capacitors in Series

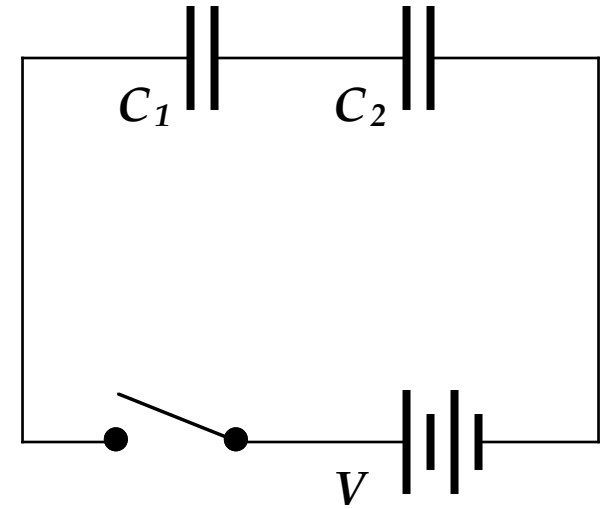Capacitors connected in a row as shown are said to be connected *in series*.




$$\frac{1}{C_{effective}} = \frac{1}{C_1} + \frac{1}{C_2}$$

Capacitors store Energy

A capacitor can store charge, and then discharge through a device, doing Work.

But how much Work?

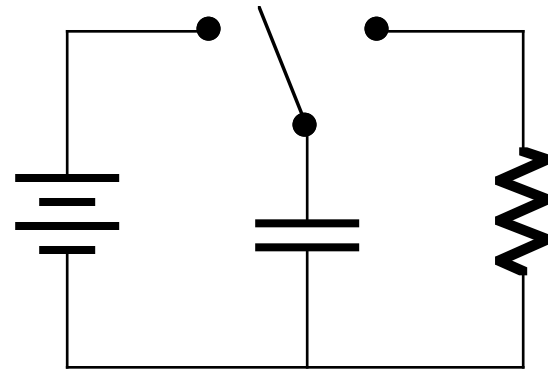

Capacitor energy derivation

With q_{inst} on capacitor plates, there is a ΔV potential difference across them.

$$\Delta V_{across\ plates} = \frac{q_{inst\ on\ plates}}{C}$$

How much Work is required to separate those charges so they can be stored on those plates?

$$dU = \Delta V \cdot dq$$

$$dU = \frac{q_{inst}}{C} \cdot dq$$

We can solve this using a model that is different from the actual charging process, but which yields the same result: how much work to transfer a charge dq across the plates?

$$U = \int_0^Q \frac{q_{inst}}{C} \cdot dq$$

$$U = \frac{Q^2}{2C}$$

Another derivation

The final potential difference across the plates is?

$$V = \frac{Q}{C}$$

What is the average potential difference during this charging process?


$$\frac{V_o + V_f}{2} = \frac{Q}{2C}$$

What is the work necessary to achieve that potential?

$$U = Vq = \frac{Q^2}{2C}$$


Other energy formulae

$$U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2 = \frac{1}{2} QV$$

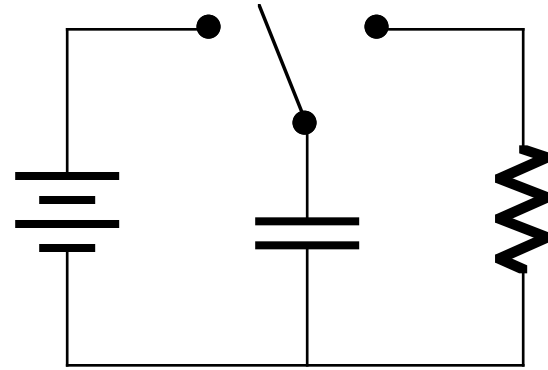

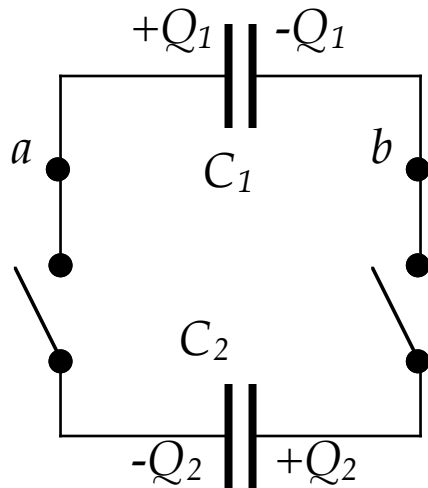Example 6

Examine the circuit here, where $C_1 > C_2$ and both have been charged to the same potential V .



- What is the potential between points a and b before the switches are closed?
 Q_1/C_1
- What happens to charges after the switches are closed?

$Q_1 > Q_2$, so excess Q_1 flows until $V_1 = V_2$

- What is the potential from a to b a long time after the switches have been closed?

Total charge $Q = Q_1 + -Q_2 = VC_1 + -VC_2$

Caps in parallel so $C_{\text{effective}} = C_1 + C_2$

Now... $V' = Q'/C' = V(C_1 - C_2) / (C_1 + C_2)$

- What is the energy stored in the system before and after the closing of the switches?

$$U_{\text{initial}} = \frac{1}{2}C_1V^2 + \frac{1}{2}C_2V^2 = \frac{1}{2}V^2(C_1 + C_2)$$


$$U_{\text{final}} = \frac{1}{2}C_1V'^2 + \frac{1}{2}C_2V'^2 = \frac{1}{2}\left(V\frac{C_1 - C_2}{C_1 + C_2}\right)^2(C_1 + C_2)$$

$$U_{\text{final}} = \left(\frac{C_1 - C_2}{C_1 + C_2}\right)^2 U_{\text{initial}}$$

Demo 2

Parallel-Plate Capacitor

Physlet I.26.2

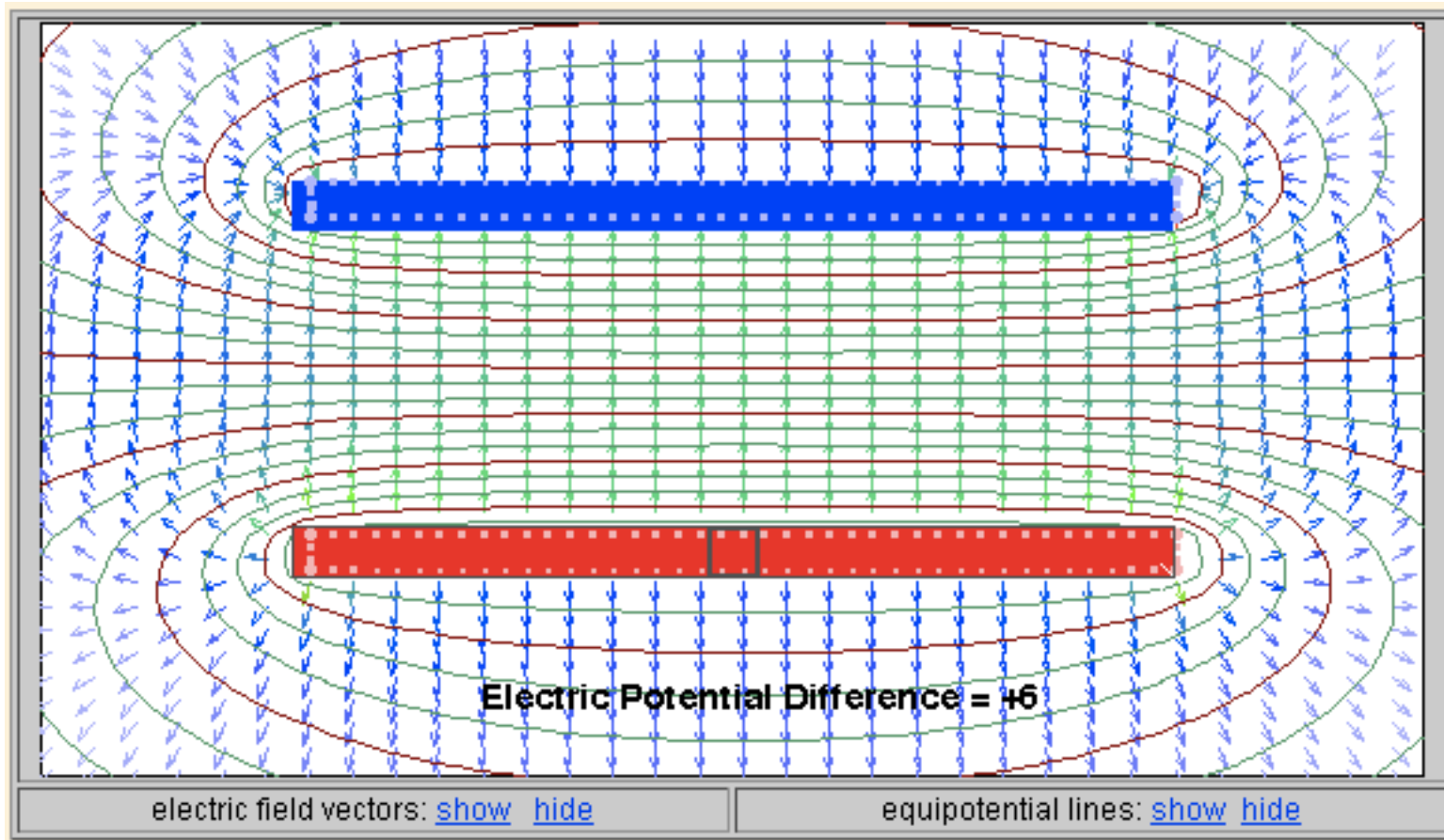

Dielectrics

An insulator inserted between the plates of an isolated parallel-plate capacitor causes a decrease in the potential difference between the two plates, a decrease of a factor κ .


Why? What effect does this have on capacitance of the system?

$$C_o = \frac{Q_o}{V_o}$$

$$V = \frac{V_o}{\kappa}$$

$$C = \frac{Q_o}{V} = \frac{Q_o}{V_o/\kappa} = \kappa \frac{Q_o}{V_o}$$

$$C = \kappa C_o$$

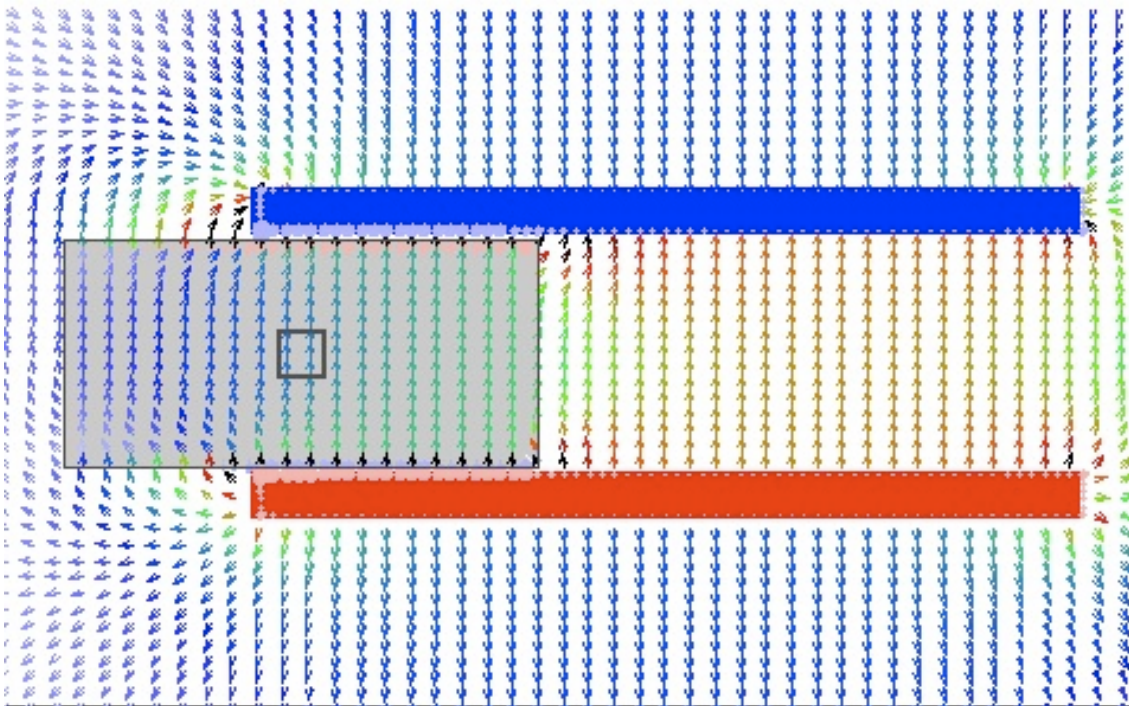

Dielectric Values

Material (V/m)	Dielectric Constant (ϵ_r)	Dielectric Strength
Vacuum	1.00000	-----
Air (dry)	1.00059	3e6
Paper	3.7	16e6
Water	80	-----

$$C = \frac{\epsilon_o A}{d}$$

$$C = \frac{\kappa \epsilon_o A}{d}$$

Advantages to using dielectrics in capacitors include:

1. increasing capacitance (!)
2. increasing the maximum operating voltage of the capacitor (most dielectrics have a greater breakdown strength than air does)
3. the dielectric itself provides a mechanical support between the plates.

Example 7

A parallel-plate capacitor has plates 2.0cm x 3.0 cm, separated only by a 1.00mm thickness of paper.

- a. Find the device's capacitance.
- b. What is the maximum charge that can be placed on the capacitor?
- c. What is the maximum energy that can be stored in this capacitor?

1. 19.7 pF

2. Dielectric strength = $16 \times 10^6 \text{ V/m}$. $V_{\text{max}} = Ed = (16 \times 10^6 \cdot 0.001 \text{ m}) = 16000 \text{ V}$, so
 $\text{max } Q = CV = (19.7 \text{ pF})(16000 \text{ V}) = 0.315 \mu\text{C}$

3. $U = CV^2/2 = 2.52 \times 10^{-3} \text{ J}$

Debrief test

2 years ago: avg=65, range=35-88

Last year: avg=60, range=24-96

This year: avg=70 , range=42-88

Absolute Electric Potential

For a point charge in space: $V_B - V_A = - \int_A^B \vec{E} \cdot d\vec{s}$

$$\vec{E} = k \frac{q}{r^2} \hat{r}$$


$$V_B - V_A = - \int_A^B k \frac{q}{r^2} \hat{r} \cdot d\vec{s}$$

$$V_f - V_i = - \int_{r_{initial}}^{r_{final}} k \frac{q}{r^2} dr$$

$$V_f - V_i = kq \left(\frac{1}{r_{final}} - \frac{1}{r_{initial}} \right)$$

If we set $V_i = 0$ at $r = \infty$,


$$V = k \frac{q}{r}$$

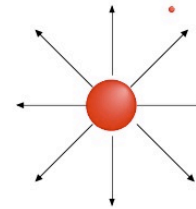

Example 15 - E for conductors


A solid conducting sphere of radius a has a net positive charge $+2Q$. A conducting spherical shell of inner radius b and outer radius c is concentric, and has a net charge $-Q$.

Use Gauss's Law to find
 a. the electric field at the 7 regions (1-7) shown in the diagram, and
 b. the charge distributions at these locations.

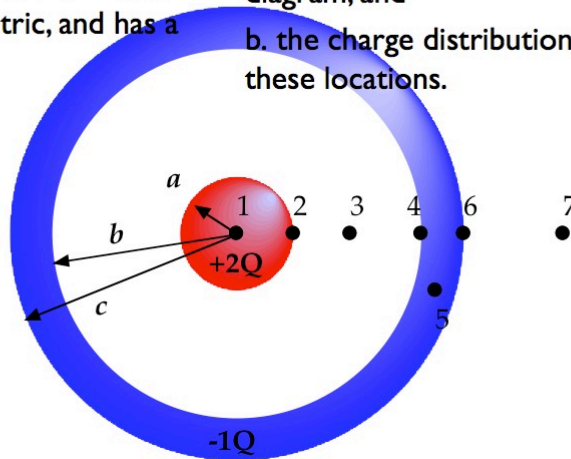

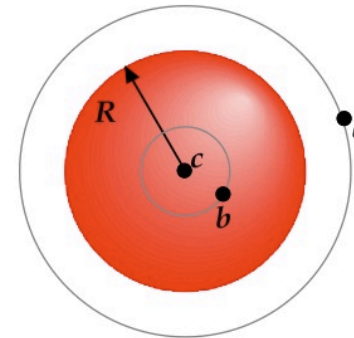Example 10

An insulating solid sphere of radius R has a uniform positive charge density w / total charge Q .



- Find the electric potential at a point outside the sphere, $r > R$. (Take potential to be 0 at $r = \infty$.)
- Find the potential at a point inside the charged sphere, $r < R$.
- What are the electric field and electric potential at the center of the uniformly charged sphere?