


Problem 26.23

Note that the equivalent cap for two series capacitors can be written as:

$$\left(\frac{1}{C_{\text{equ}}}\right)^{-1} = \left(\frac{1}{C_1} + \frac{1}{C_2}\right)^{-1} = \left(\frac{C_2}{C_1 C_2} + \frac{C_1}{C_1 C_2}\right)^{-1} = \left(\frac{C_1 + C_2}{C_1 C_2}\right)^{-1}$$

$$\Rightarrow C_{\text{equ}} = \frac{C_1 C_2}{C_1 + C_2}$$

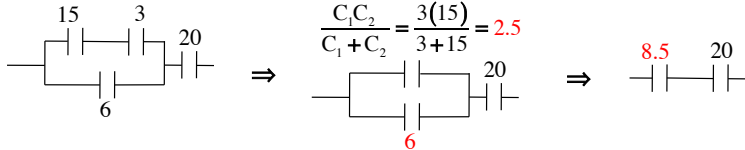a.) The equivalent capacitance (I think that doing a problem like this algebraically first is the best way to go, but for the sake of brevity, I'll do it solely with numbers):



So with adding in the power of ten:

$$C_{\text{equ}} = \frac{C_{8.5} C_{20}}{C_{8.5} + C_{20}} = \frac{8.5(20)}{8.5 + 20} = 5.96 \times 10^{-6} \text{ F}$$

1.)


The equivalent capacitance is:

$$C_{\text{eq}} = \frac{Q}{V}$$

$$\Rightarrow Q = C_{\text{eq}} V_0$$

$$= (5.96 \times 10^{-6} \text{ F})(15 \text{ V})$$

$$= 89.5 \times 10^{-6} \text{ C}$$

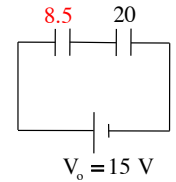


Looking back at the previous page, we can see that the charge on C_{eq} is the same as the charge on the 20 μf cap, which is 89.5 μf , so we've taken care of that capacitor. As for the rest of the caps, we need to know their voltages. Filling in our circuit and playing around with what we know:

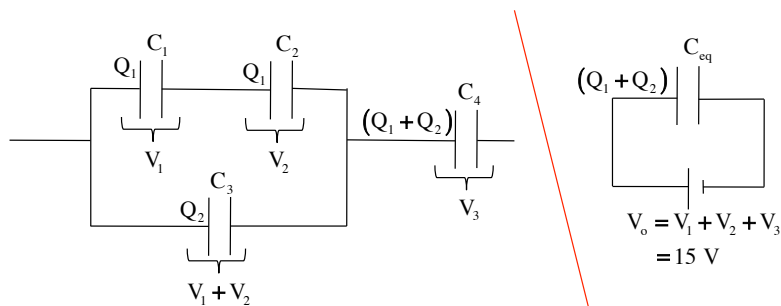
3.)

b.) What is the charge on each capacitor?

It isn't a bad idea to think a little about the quantities that are common to the various components within the system. The circuit below lists the voltage, capacitance and charge for each of the elements of the original circuit and for the equivalent circuit.



2.)

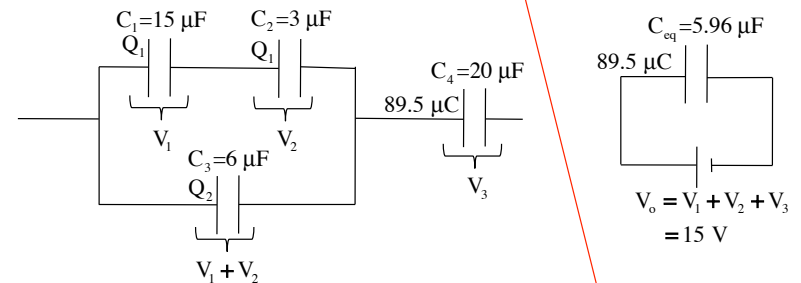

Doodling:

$$V_3 = \frac{89.5 \mu\text{C}}{20 \mu\text{F}}$$

$$= 4.47 \text{ V}$$

So

$$V_0 = (15 \text{ V}) = V_1 + V_2 + (4.47 \text{ V})$$


$$\Rightarrow V_1 + V_2 = 10.53 \text{ V}$$

$$Q_2 = C_3 (V_1 + V_2)$$

$$= (6.00 \times 10^{-6} \text{ F})(10.53 \text{ V})$$

$$= 63.2 \times 10^{-6} \text{ C}$$

4.)

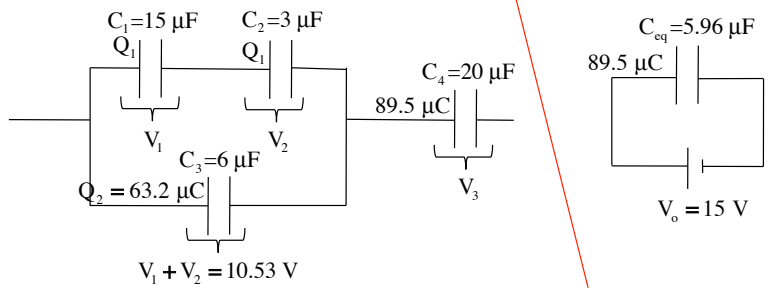

So if we were masochists, we could start with $V_1 + V_2 = 10.53 \text{ V}$, note that $V = \frac{Q}{C}$, and solve for the Q 's . . . or we could be clever and note that if $(Q_1 + Q_2) = 89.5 \text{ μC}$, and if, as we've deduced, $Q_2 = 63.2 \text{ μC}$, then Q_1 must be 26.3 μC . QED (hee, hee).