

## Problem 26.27

There is no rhyme or reason to a problem like this. You just have to take what you know and play with it until something pops. Here goes:

--The equivalent capacitance for a parallel combination of like capacitors will be:

$$\begin{aligned}C_p &= C_1 + C_2 + C_3 + \dots + C_n \\ &= nC\end{aligned}$$

as there are "n" of them and they are all the same size.

--The equivalent capacitance for a series combination of like capacitors will be:

$$\begin{aligned}\frac{1}{C_s} &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n} \\ \Rightarrow C_s &= \frac{1}{\frac{1}{C} + \frac{1}{C} + \frac{1}{C} + \dots} = \frac{1}{n\left(\frac{1}{C}\right)} \\ &= \frac{C}{n}\end{aligned}$$

1.)

But we are told that:

$$\begin{aligned}C_p &= 100C_s \\ \Rightarrow nC &= 100\left(\frac{C}{n}\right) \\ \Rightarrow n^2 &= 100 \\ \Rightarrow n &= 10\end{aligned}$$

As I said, just playing around . . .

2.)