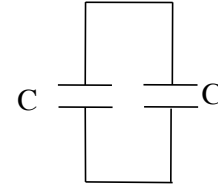


Problem 26.37

a.) Because the caps are at the same voltage, no charge flow will occur when the two are connected in parallel. The energy involved is:

$$\begin{aligned}U &= 2 \left[\frac{1}{2} C V_c^2 \right] \\&= 2 \left(\frac{1}{2} \right) (10.0 \times 10^{-6} \text{ F}) (50.0 \text{ V})^2 \\&= 2.50 \times 10^{-2} \text{ J}\end{aligned}$$




b.) Doubling the plate distance will halve the capacitance. Additionally, the charge will redistribute until the voltage is again the same. Calling this new voltage V_{new} and noting that the *total* charge in the system hasn't changed, we can write:

$$\begin{aligned}Q_{\text{initial}} &= 2CV_c \quad \text{and} \\Q_{\text{final}} &= CV_{\text{new}} + \frac{C}{2}V_{\text{new}} = \frac{3}{2}CV_{\text{new}} \\&\Rightarrow \cancel{2C}V_c = \frac{3}{2}\cancel{C}V_{\text{new}} \\&\Rightarrow \frac{4}{3}V_c = V_{\text{new}}\end{aligned}$$

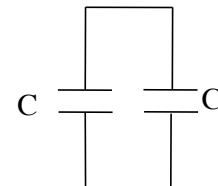1.)

Putting in the numbers yields:

$$\begin{aligned}V_{\text{new}} &= \frac{4}{3}V_c \\&= \frac{4}{3}(50.0 \text{ V}) \\&= 66.7 \text{ V}\end{aligned}$$



The new energy is:

$$\begin{aligned}U &= \frac{1}{2}CV_{\text{new}}^2 + \frac{1}{2}\left(\frac{C}{2}\right)V_{\text{new}}^2 \\&= \frac{3}{4}CV_{\text{new}}^2 \\&= \left(\frac{3}{4}\right)(10.0 \times 10^{-6} \text{ F})(66.7 \text{ V})^2 \\&= 3.30 \times 10^{-2} \text{ J}\end{aligned}$$

c.) There is more energy in the system afterward. Where did it come from? It came from the work required to physically pull the plates apart.

2.)