

Problem 27.12

The **voltage difference** across a resistor is proportional to the **current** through the resistor and the **resistance** of the resistor, or:

$$\begin{aligned}V_R &= iR \\ \Rightarrow i &= \frac{V_R}{R} \\ &= \frac{(120 \text{ V})}{(240 \text{ } \Omega)} \\ &= .5 \text{ amps}\end{aligned}$$