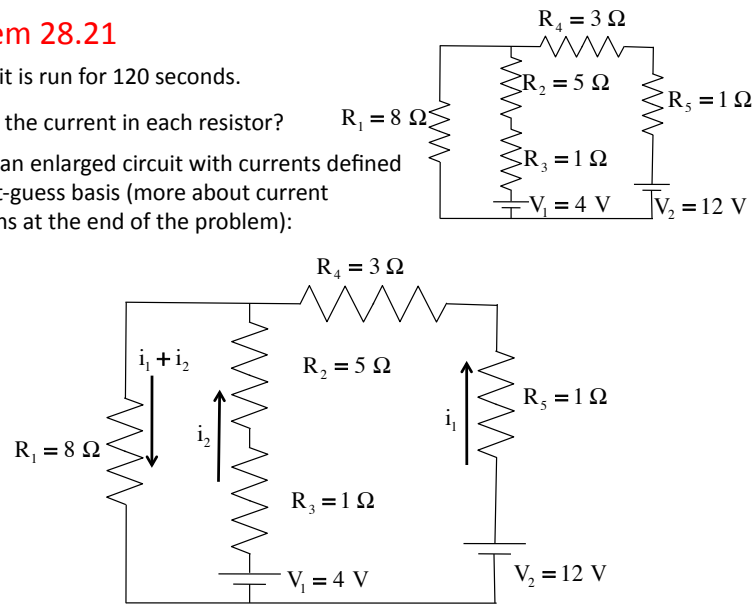


## Problem 28.21

The circuit is run for 120 seconds.

a.) What's the current in each resistor?

Below is an enlarged circuit with currents defined on a best-guess basis (more about current definitions at the end of the problem):




So:

$$\begin{aligned} i_1 &= -1.75i_2 + .5 \\ &= -1.75(-.46) + .5 \\ &= 1.3 \text{ A} \end{aligned}$$

and the current through the 8 ohm resistor is:

$$\begin{aligned} i_3 &= i_1 + i_2 \\ &= 1.3 + (-.46) \\ &= .84 \text{ A} \end{aligned}$$


Note that the negative sign for  $i_2$  means that the current is really in the opposite direction as defined. This is why assumptions about current direction is not important. Apparently, the 12 volts battery is large enough to stifle the effects of the 4 volt battery making the current through that branch opposite the direction you would expect if the 4 volt battery stood alone. When a "bad" assumption is made, though, nothing is hurt. It just means that when you solve for that variable, you will find a negative sign in front of its numeric value. No bid deal!

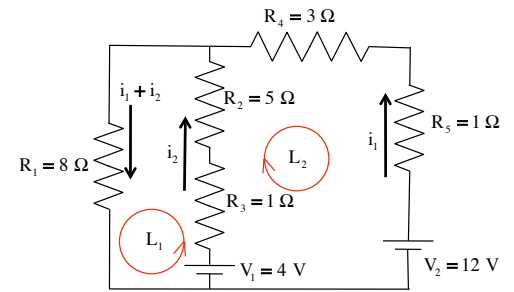

a.) What's the current in each resistor?

(Note that there are several ways to solve these. I've used an algebraic approach instead of a matrix-driven calculator approach. Either will do!)

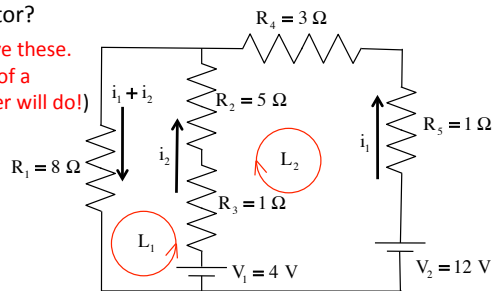The node equation was used to define the current through the 8 ohm resistor, so with only two unknowns, we need to use loop equations to finish the task. I've identified the loops and direction of transverse on the sketch.



$L_1$ :

$$\begin{aligned} V_1 - i_2 R_3 - i_2 R_2 - (i_1 + i_2) R_1 &= 0 \\ 4 - i_2(1) - i_2(5) - i_1(8) - i_2(8) &= 0 \\ \Rightarrow 8i_1 + i_2(14) &= 4 \\ \Rightarrow i_1 &= \frac{-14i_2 + 4}{8} \\ \Rightarrow i_1 &= -1.75i_2 + .5 \end{aligned}$$

$L_2$ :

$$\begin{aligned} V_1 - i_2 R_3 - i_2 R_2 + i_1 R_4 + i_1 R_5 - V_2 &= 0 \\ 4 - i_2(1) - i_2(5) + i_1(3) + i_1(1) - 12 &= 0 \\ \Rightarrow -i_2(6) + i_1(4) &= 8 \\ \Rightarrow 4i_1 - 6i_2 &= 8 \\ \Rightarrow 4(-1.75i_2 + .5) - 6i_2 &= 8 \\ \Rightarrow -7i_2 + 2 - 6i_2 &= 8 \\ \Rightarrow i_2 &= -.46 \end{aligned}$$

b.) The energy delivered by each battery makes use of the power relationship. For  $V_1$ :


$$\begin{aligned} P_{V_1} &= i_2 V_1 \\ &= (-.46 \text{ A})(4 \text{ V}) \\ &= -1.84 \text{ W} \end{aligned}$$

Why the negative sign? The 12 volt battery is forcing current into the 4

volt battery. This is opposite what battery usually do (they are designed to put energy into the system). As such, the battery in this case can be thought of as depleting energy, suggests a negative power rating.


Knowing the power, we can write:
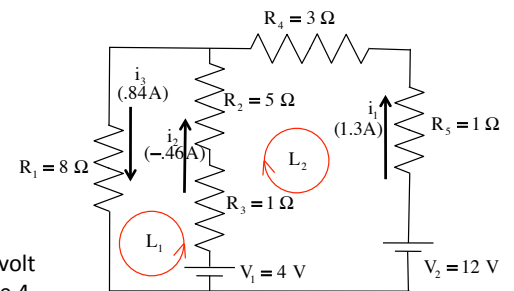
$$\begin{aligned} P_{V_1} &= \frac{W_{\text{battery1}}}{\Delta t} \\ \Rightarrow W_{\text{battery1}} &= P \Delta t \\ &= (-1.84 \text{ joules/sec})(120 \text{ sec}) \\ &= -222 \text{ joules} \end{aligned}$$



b.) The energy delivered by each battery makes use of the power relationship. For  $V_2$  :
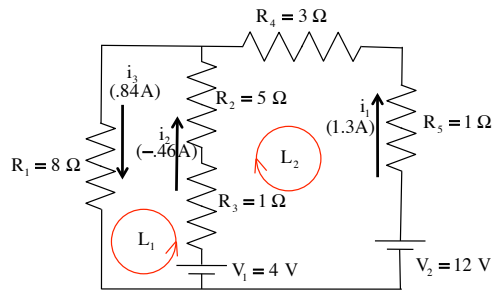
$$\begin{aligned}
 P_{V_2} &= i_1 V_2 \\
 &= (1.3 \text{ A})(12 \text{ V}) \\
 &= 15.6 \text{ Watts} = \frac{W_{\text{battery2}}}{\Delta t} \\
 \Rightarrow W_{\text{battery2}} &= P_{V_2} \Delta t \\
 &= (15.6 \text{ joules/sec})(120 \text{ sec}) \\
 &= 1872 \text{ joules}
 \end{aligned}$$



5.)

c.) (cont'd)


For  $R_2$  :

$$\begin{aligned}
 P_{R_2} &= i_2^2 R_2 \\
 &= (-.46 \text{ A})^2 (5 \Omega) \\
 &= 1.06 \text{ joules/sec}
 \end{aligned}$$

$$\text{As } P_{R_2} = \frac{W_{\text{resistor2}}}{\Delta t}$$

$$\begin{aligned}
 \Rightarrow W_{\text{resistor2}} &= P_{R_2} \Delta t \\
 &= (1.06 \text{ joules/sec})(120 \text{ sec}) \\
 &= 127 \text{ joules}
 \end{aligned}$$

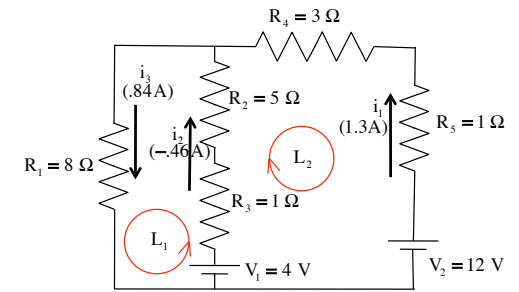Note that the actual solution manual lists this as 128 joules as they use -.462 amps.



7.)


c.) The energy delivered to the resistors is the same as the energy dissipated by them, so using the power relationship for resistors, we can write:

$$\begin{aligned}
 P_{R_1} &= i_3^2 R_1 \\
 &= (.84 \text{ A})^2 (8 \Omega) \\
 &= 5.65 \text{ joules/sec}
 \end{aligned}$$

$$\text{As } P_{R_1} = \frac{W_{\text{resistor1}}}{\Delta t}$$

$$\begin{aligned}
 \Rightarrow W_{\text{resistor1}} &= P_{R_1} \Delta t \\
 &= (5.6 \text{ joules/sec})(120 \text{ sec}) \\
 &= 672 \text{ joules}
 \end{aligned}$$

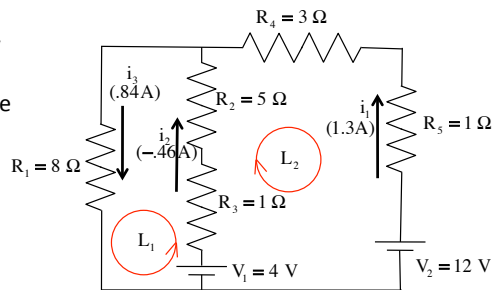Note that the actual solution manual lists this as 687 joules because they used .846 amps as their current.



6.)

c.) (cont'd)


For  $R_3$  :

$$\begin{aligned}
 P_{R_3} &= i_4^2 R_3 \\
 &= (-.46 \text{ A})^2 (1 \Omega) \\
 &= .21 \text{ joules/sec}
 \end{aligned}$$

$$\text{As } P_{R_3} = \frac{W_{\text{resistor3}}}{\Delta t}$$

$$\begin{aligned}
 \Rightarrow W_{\text{resistor3}} &= P_{R_3} \Delta t \\
 &= (.21 \text{ joules/sec})(120 \text{ sec}) \\
 &= 25.2 \text{ joules}
 \end{aligned}$$

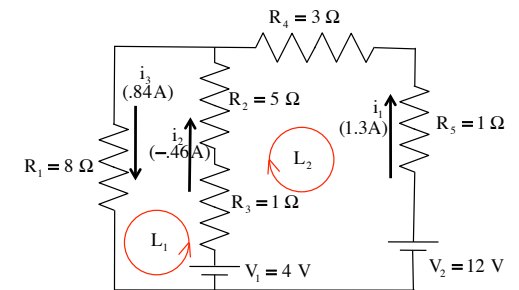Note that the actual solution manual lists this as 25.6 joules.



8.)

c.) (cont'd)

For  $R_4$ :

$$P_{R_4} = i_1^2 R_4$$

$$= (1.3 \text{ A})^2 (3 \Omega)$$

$$= 5.07 \text{ joules/sec}$$


$$\text{As } P_{R_4} = \frac{W_{\text{resistor 4}}}{\Delta t}$$

$$\Rightarrow W_{\text{resistor 4}} = P_{R_4} \Delta t$$

$$= (5.07 \text{ joules/sec})(120 \text{ sec})$$

$$= 609 \text{ joules}$$

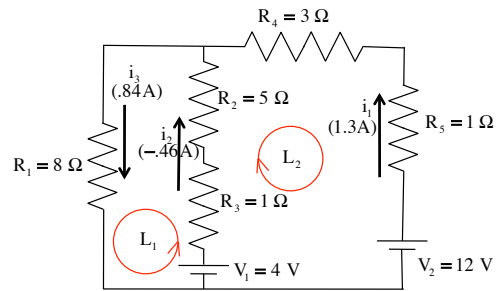Note that the actual solution manual lists this as 616 joules as they use 1.31 amps.




9.)

d.) Using the work/energy values provided by the book (for accuracy sake), the sum of all the energy dissipated by the resistors is:

$$W_{\text{done by resistors}} = 687 + 128 + 25.6 + 616 + 205 = 1661.6 \text{ joules}$$

The chemical energy conversion in battery  $V_1$  provided 1880 joules (according to the book). So what happened to the approximately 220 joules of "left-over" energy provided by that battery? It went into charging up battery  $V_2$  to the tune of -222 joules (this is the approximate overlay—the disparity is due to round-off error).

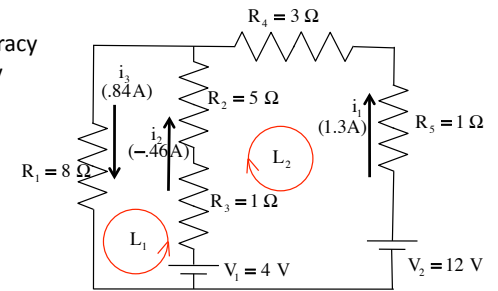e.) The total energy dissipated by the resistors is, as stated above, 1661.6 joules (approximately). This matches (again, as was stated above) the amount of energy (net) put into the system by the batteries.



11.)

c.) (cont'd)

For  $R_5$ :

$$P_{R_5} = i_1^2 R_5$$

$$= (1.3 \text{ A})^2 (1 \Omega)$$

$$= 1.69 \text{ joules/sec}$$


$$\text{As } P_{R_5} = \frac{W_{\text{resistor 5}}}{\Delta t}$$

$$\Rightarrow W_{\text{resistor 5}} = P_{R_5} \Delta t$$

$$= (1.69 \text{ joules/sec})(120 \text{ sec})$$

$$= 203 \text{ joules}$$

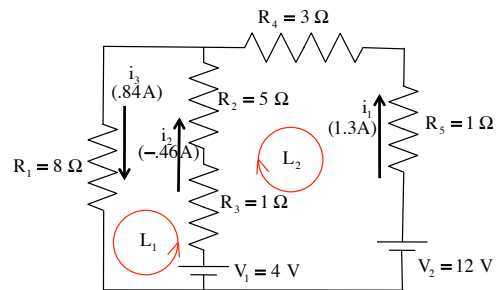Note that the actual solution manual lists this as 205 joules.



10.)