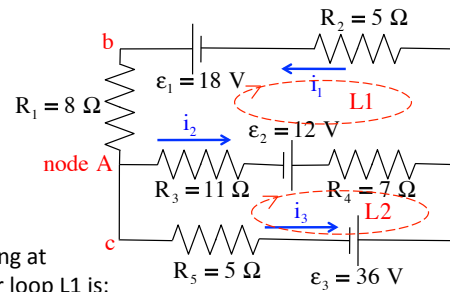


Problem 28.32

This is a bizarre problem in the sense that it makes you step through all the math, literally by the numbers. I've dumped everything we need on the sketch to the right!!



a.) For the circuit shown (and starting at position "b"), the Loop Equation for loop L1 is:

$$\begin{aligned} \text{L1:} \quad & -\epsilon_1 + i_1 R_2 + i_2 R_4 - \epsilon_2 + i_2 R_3 + i_1 R_1 = 0 \\ & -18 + 5i_1 + 7i_2 - 12 + 11i_2 + 8i_1 = 0 \\ \Rightarrow \quad & 13i_1 + 18i_2 = 30 \end{aligned}$$

b.) For the circuit shown (starting at "c"), the Loop Equation for loop L2 is:

$$\begin{aligned} \text{L2:} \quad & -i_2 R_3 + \epsilon_2 - i_2 R_4 - \epsilon_3 + i_3 R_5 = 0 \\ & -11i_2 + 12 - 7i_2 - 36 + 5i_3 = 0 \\ \Rightarrow \quad & -18i_2 + 5i_3 = 24 \end{aligned}$$

1.)

f.) Solving the modified loop equations for i_1 and i_2 , we get:

Using $i_1 = 4.6i_2 + 4.8$:

$$\begin{aligned} 13i_1 + 18i_2 &= 30 \\ 13(4.6i_2 + 4.8) + 18i_2 &= 30 \\ \Rightarrow 59.8i_2 + 62.4 + 18i_2 &= 30 \\ \Rightarrow 77.8i_2 + 62.4 &= 30 \\ \Rightarrow 77.8i_2 &= -32.4 \\ \Rightarrow i_2 &= -0.416 \text{ A} \end{aligned}$$

This means:

$$\begin{aligned} 13i_1 + 18i_2 &= 30 \\ 13i_1 + 18(-0.416 \text{ A}) &= 30 \\ \Rightarrow i_1 &= 2.88 \text{ A} \end{aligned}$$

3.)

c.) For the circuit shown, the Node Equation for node "A" is:

$$i_1 = i_2 + i_3$$

d.) Solve Node Equation for i_3 :

$$\begin{aligned} i_1 &= i_2 + i_3 \\ \Rightarrow i_3 &= i_1 - i_2 \end{aligned}$$

e.) Substituting i_3 into Loop 2 equation:

$$\begin{aligned} -18i_2 + 5i_3 &= 24 \\ \Rightarrow -18i_2 + 5(i_1 - i_2) &= 24 \\ \Rightarrow 5i_1 - 23i_2 &= 24 \\ \Rightarrow i_1 &= \frac{23i_2 + 24}{5} \\ \Rightarrow i_1 &= 4.6i_2 + 4.8 \end{aligned}$$

2.)

g.) Lastly:

$$\begin{aligned} i_1 &= i_2 + i_3 \\ \Rightarrow (2.88 \text{ A}) &= (-0.416 \text{ A}) + i_3 \\ \Rightarrow i_3 &= (3.3 \text{ A}) \end{aligned}$$

h.) The significance of the negative sign in i_2 :

It is not uncommon to **not know** the actual direction of current in a complicated circuit, so to do a problem like this we have to guess at the current direction. This is not a problem, though, as the math will take care of you. How so? If, given the numbers in the problem, you have assumed the wrong current direction, you will simply find yourself with a negative sign in the offending current's numerical answer. In this case, the current $i_2 = -0.416 \text{ A}$ is telling you that the current's magnitude is .416 amps and its direction is not to the right as assumed but, in fact, is to the left. Ain't math wonderful?

4.)