


Problem 28.39

a.) With the switch open a long time, the capacitor will be fully charged and there will be no current in the circuit. While the capacitor is charging, though, the time constant will be:

$$\begin{aligned}\tau_{\text{charging}} &= R_{\text{net}} C \\ &= [R_1 + R_2] (C) \\ &= [(5 \times 10^4 \Omega) + (10 \times 10^4 \Omega)] (10 \times 10^{-6} \text{ f}) \\ &= 1.50 \text{ seconds}\end{aligned}$$

b.) When the switch is thrown and the capacitor begins to discharge through R_2 , the time constant will be:
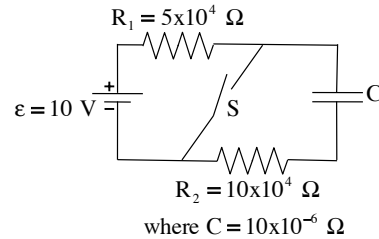
$$\begin{aligned}\tau_{\text{charging}} &= R_2 C \\ &= (10 \times 10^4 \Omega) (10 \times 10^{-6} \text{ f}) \\ &= 1 \text{ seconds}\end{aligned}$$



1.)

Remembering that $V_{\text{cap}} = \frac{q(t)}{C}$, Ohm's Law used on the right loop yields:

$$\begin{aligned}\frac{q(t)}{C} - i_2 R_2 &= 0 \\ \Rightarrow i_2 &= \left(\frac{1}{R_2 C} \right) q(t)\end{aligned}$$

We know from the definition of capacitance that:


$$C = \frac{Q_{\text{max}}}{V_{\text{max}}} \Rightarrow Q_{\text{max}} = CV_{\text{max}}$$

and we know from previous experience that the charge on a discharging capacitor is equal to:

$$q(t) = Q_{\text{max}} e^{-t/R_2 C}$$

Coupling those two bits of information allows us to write:
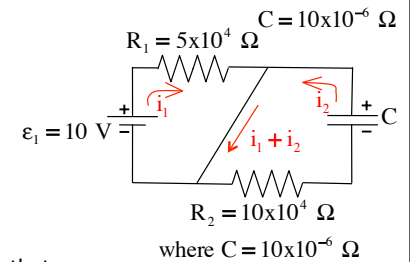
$$\begin{aligned}q(t) &= Q_{\text{max}} e^{-t/R_2 C} \\ &= CV_{\text{max}} e^{-t/R_2 C}\end{aligned}$$




3.)

c.) This is where things get interesting. As was said above, with the switch opened for a long time, the current goes to zero as the capacitor charges to its maximum, and the voltage across the capacitor at that point is $\epsilon = 10 \text{ V}$.

When the switch is thrown, then, a current will be generated through R_1 due to the battery and a current will be generated through R_2 due to the voltage across the capacitor. All of these currents are shown in the sketch.

From Ohm's Law on the left loop, we can write:
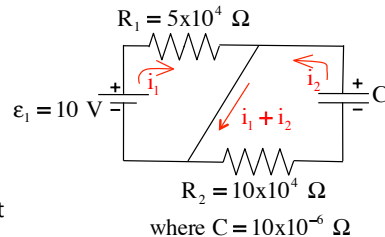
$$\begin{aligned}\epsilon_1 - i_1 R_1 &= 0 \\ \Rightarrow i_1 &= \frac{\epsilon_1}{R_1} \\ \Rightarrow i_1 &= \frac{(10 \text{ V})}{(5 \times 10^4 \Omega)} \\ \Rightarrow &= 2 \times 10^{-4} \text{ A}\end{aligned}$$



2.)


With that, we can write:

$$\begin{aligned}i_2 &= \left(\frac{1}{R_2 C} \right) q(t) \\ &= \left(\frac{1}{R_2 C} \right) (CV_{\text{max}} e^{-t/R_2 C}) \\ &= \left(\frac{1}{R_2} \right) (V_{\text{max}} e^{-t/R_2 C}) \\ &= \left(\frac{1}{10 \times 10^4 \Omega} \right) ((10 \text{ V}) e^{-t/(10 \times 10^4)(10 \times 10^{-6})}) \\ &= (10^{-4}) e^{-t/(1 \text{ sec})}\end{aligned}$$

That means the switch carries a downward current of:

$$i_1 + i_2 = (2 \times 10^{-4} \text{ A}) + [(1 \times 10^{-4}) e^{-t/(1 \text{ sec})} \text{ A}]$$

Crazy, huh?

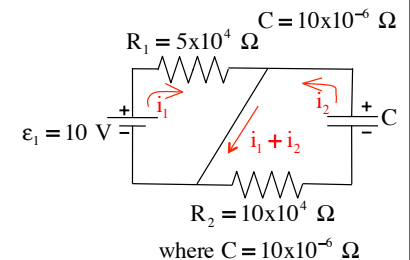

4.)