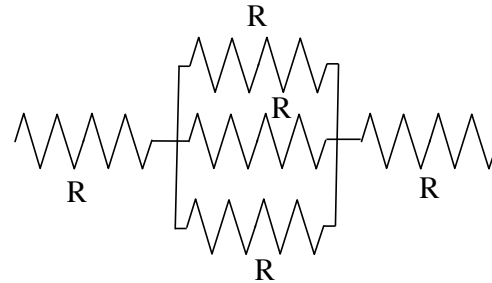


Problem 28.5

This circuit has two single resistors in series with a combination of three resistors in parallel, all of the same value. As resistors in series combinations add, we can write:

$$\begin{aligned} R_{\text{eq}} &= R + \frac{R}{3} + R \\ &= \frac{7R}{3} \end{aligned}$$




In the off-chance you don't see where the second term came from, if you have "n" resistors in parallel, the equivalent resistance will be:

$$\begin{aligned} \frac{1}{R_{\text{eq}}} &= \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \dots \text{ (n times)} \\ &= n \left(\frac{1}{R} \right) \\ \Rightarrow R_{\text{eq}} &= \frac{R}{n} \end{aligned}$$

1.)

THIS ONLY WORKS IF ALL THE RESISTORS ARE OF THE SAME SIZE. In any case, a parallel combination of 3 resistors each of resistance "R" will have an equivalent resistance of:

$$R_{\text{eq,parallel}} = \frac{R}{3}$$

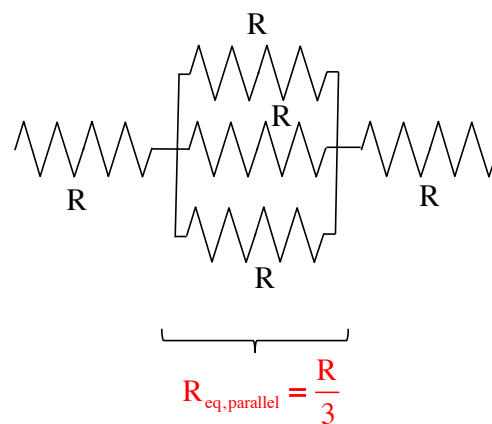

2.)