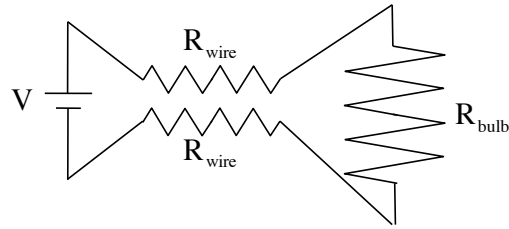


Problem 28.6

A 75 watt light bulb at 120 volts suggests the current can be determined from the power relationship using: $P = iV$

$$\begin{aligned}\Rightarrow i &= \frac{P}{V} \\ \Rightarrow i &= \left(\frac{75 \text{ W}}{120 \text{ V}} \right) \\ &= .625 \text{ A}\end{aligned}$$



With the current, the resistance of the bulb can be determined from:

$$\begin{aligned}P &= i^2 R_{\text{bulb}} \\ \Rightarrow R_{\text{bulb}} &= \frac{P}{i^2} \\ &= \left(\frac{75 \text{ W}}{(.625 \text{ A})^2} \right) \\ &= 192 \Omega\end{aligned}$$

1.)

The resistance the bulb along with the resistance in the wires generates a net resistance of:

$$\begin{aligned}R_{\text{total}} &= R_{\text{bulb}} + 2R_{\text{wire}} \\ &= (192 \Omega) + 2(.8 \Omega) \\ &= 193.6 \Omega\end{aligned}$$

According to Ohm's Law, that resistance in a 120 volt circuit will generate a current of:

$$\begin{aligned}V &= iR_{\text{total}} \\ \Rightarrow i &= \left(\frac{120 \text{ V}}{193.6 \Omega} \right) \\ &= .62 \Omega\end{aligned}$$

Apparently, if we include the resistance associated with the wires, the current turns out to be .005 amps below the theoretically expected value.

2.)