

Problem 28.8

All resistances are "R." Neglecting internal resistance of the batteries:

a.) currents?


ckt 1

$$i_1 = \frac{\epsilon}{R}$$

ckt 2

$$\begin{aligned} i_2 &= \frac{\epsilon}{R+R} \\ &= \frac{\epsilon}{2R} \\ &= \frac{1}{2} i_1 \end{aligned}$$

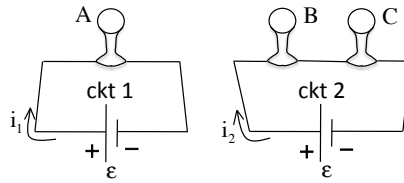
b.) As the current is the same through each element in the series combination (circuit 2), the obvious response is that the brightness of bulbs B and C will be the same.



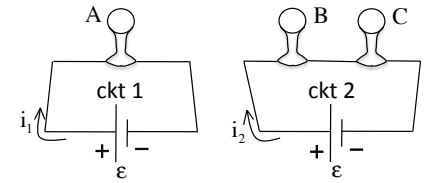1.)

According to the math, the power dissipated by B will be a quarter that dissipated by A, hence B must be a quarter as bright as A.

Looking at this a little differently: The power provided to a circuit by a battery is $P = \epsilon i$. Each of our circuits has a battery voltage of ϵ . As the current through *circuit 2* is half of that through *circuit 1*, the total power provided to *circuit 2* is half that provided to *circuit 1*. Half of *circuit 2's* power, or a *quarter of circuit 1's* power, is dissipated by each of *circuit 2's* two resistors.



$$\begin{aligned} P_{\text{ckt-1}} &= \epsilon i_1 \text{ and } P_{\text{ckt-2}} = \epsilon i_2 \\ \Rightarrow \frac{P_{\text{ckt-2}}}{P_{\text{ckt-1}}} &= \frac{\epsilon i_2}{\epsilon i_1} = \frac{i_2}{i_1} \\ \Rightarrow \frac{P_{\text{ckt-2}}}{P_{\text{ckt-1}}} &= \frac{i_2}{i_1} = \frac{i_2}{2i_2} \\ \Rightarrow P_{\text{ckt-2}} &= \frac{1}{2} P_{\text{ckt-1}} \end{aligned}$$

Bottom line: Bulbs B and C should be a *quarter* as bright as bulb A.

3.)

Short answer: More current through bulb A suggests a brighter bulb.

For the intellectually curious: It is not unreasonable to wonder "how much more?" To understand the answer to that, we need to look at the math.

"Power dissipated" by a light bulb generates brightness. As power dissipation, hence brightness, is governed by the amount of current passing through a resistor (light bulb), we need the power relationship for a resistor. That is:

$$P_R = i^2 R$$

In other words, the power dissipated by the single resistor (A) in circuit 1 is:

$$P_A = i_1^2 R$$

and the power dissipated by a single resistor (say B) in circuit 2 is:

$$\begin{aligned} P_B &= i_2^2 R \\ \text{from Part a } \Rightarrow \left(\frac{i_1}{2}\right)^2 R &= \left(\frac{1}{4}\right)(i_1^2 R) \\ &= \frac{P_A}{4} \end{aligned}$$

2.)

