
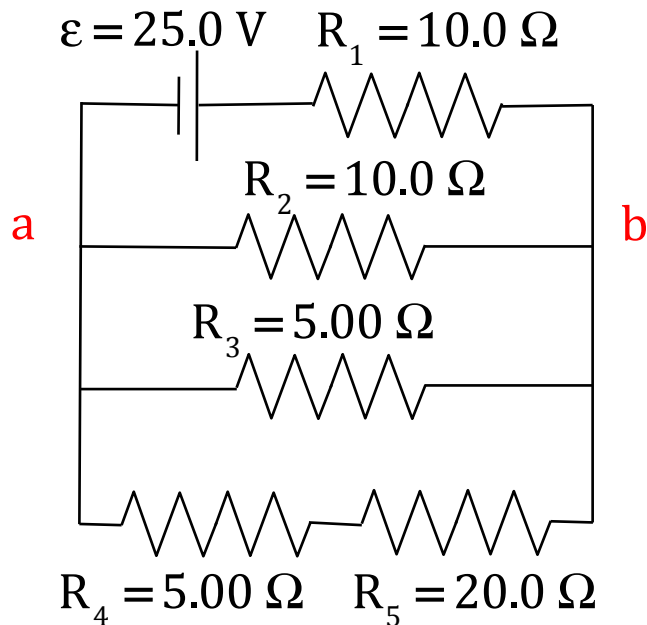


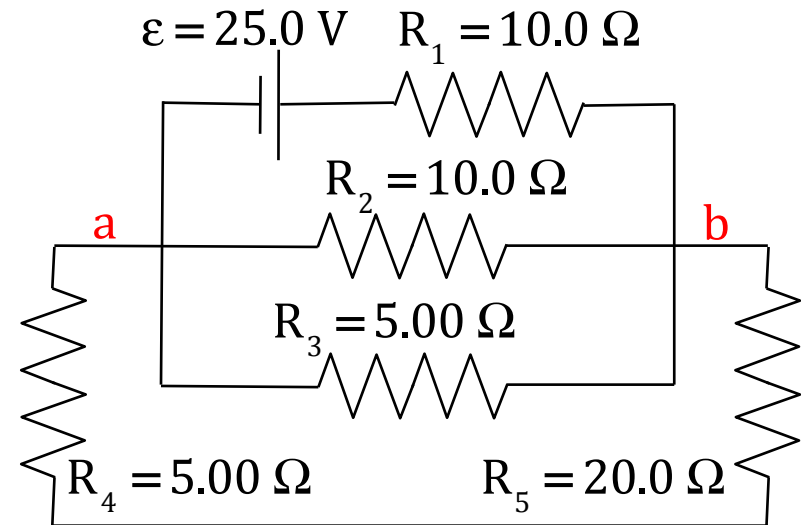Problem 28.9

This is a seat-of-the-pants problem in the sense that the first thing to notice is that you can make it look a whole more hospitable by realizing the side resistors can be repositioned as shown below.




In other words, what you have is a battery and resistor in series across a three-branch parallel circuit with one branch made up of a series combination.

Determining the equivalent resistance of the three bottom parallel branches yields:


$$\begin{aligned} \frac{1}{R_{eq,1}} &= \frac{1}{(10.0 \Omega)} + \frac{1}{(5.0 \Omega)} + \frac{1}{(25.0 \Omega)} \\ &= .34 \\ \Rightarrow R_{eq,1} &= 2.94 \Omega \end{aligned}$$

This leaves us with:

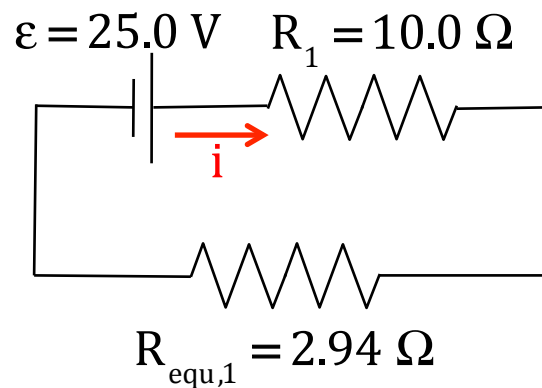

... so that the current drawn from the battery is:

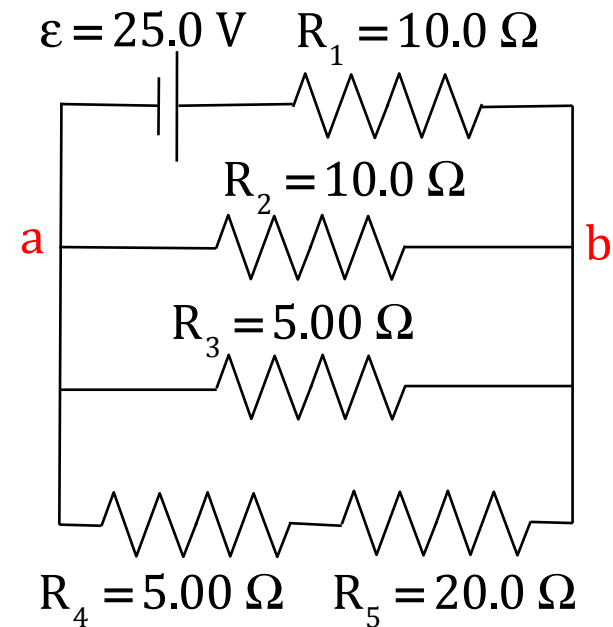
$$\begin{aligned} \epsilon - R_1 i - R_{eq,1} i &= 0 \\ \Rightarrow 25.0 &= (10.0 \Omega) i + (2.94 \Omega) i \\ \Rightarrow i &= 1.93 \text{ A} \end{aligned}$$



Knowing the current drawn from the battery allows us to determine the voltage drop across $a-b$, which is:

$$\begin{aligned} V_{ab} &= \varepsilon - iR_1 \\ &= (25.0 \text{ V}) - (1.93 \text{ A})(10.0 \Omega) \\ &= 5.70 \text{ V} \end{aligned}$$

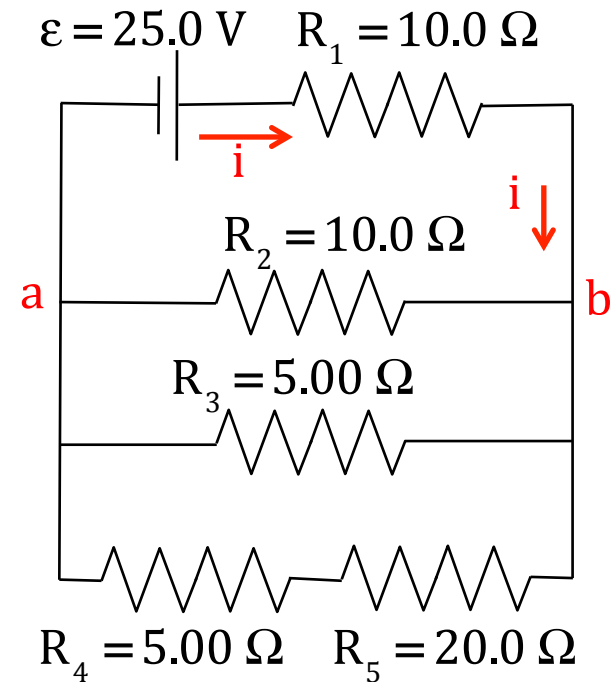(This happens to be the answer to *Part b*.)



The voltage across $a-b$ is the same as the voltage across R_2 and the voltage across R_3 and the voltage across the R_4 and R_5 combination. That means we can write:

$$\begin{aligned} V_{ab} &= iR_{4+5} \\ \Rightarrow (5.70 \text{ V}) &= i(20.0 \Omega + 5.00 \Omega) \\ \Rightarrow i &= .228 \text{ A} \quad (\text{or } 228 \text{ mA}) \end{aligned}$$

This is the current through the 20.0Ω resistor.