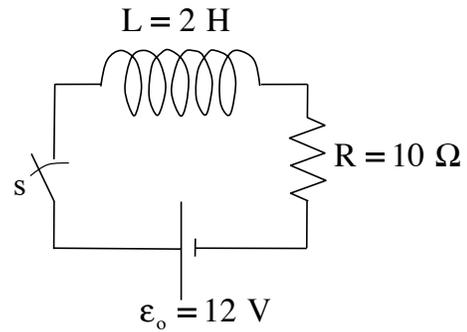


### Problem 32.14

The current-function for a RL circuit with a DC source (power supply) is:

$$\begin{aligned}i(t) &= i_o (1 - e^{-t/\tau}) \\ \Rightarrow \frac{i(t)}{i_o} &= (1 - e^{-t/\tau}) \\ \Rightarrow \ln\left(1 - \frac{i(t)}{i_o}\right) &= \ln(e^{-t/\tau}) \\ \Rightarrow \ln\left(1 - \frac{i(t)}{i_o}\right) &= -t/\tau \\ \Rightarrow t &= -\tau \ln\left(1 - \frac{i(t)}{i_o}\right) \\ \Rightarrow t &= -\left(\frac{L}{R}\right) \ln\left(1 - \frac{i(t)}{i_o}\right)\end{aligned}$$



1.)


Fitting this to our times, we get:

a.) for 50% of  $i_o$  (or  $\frac{i(t)}{i_o} = \frac{.5i_o}{i_o} = .5$ ):

$$\begin{aligned}t &= -\left(\frac{L}{R}\right) \ln\left(1 - \frac{i(t)}{i_o}\right) \\ \Rightarrow t &= -\left(\frac{L}{R}\right) \ln(1 - .5) \\ &= -\left(\frac{2 \text{ H}}{10 \Omega}\right) \ln(1 - .5) \\ &= .139 \text{ sec}\end{aligned}$$

b.) for 90% of  $i_o$ :
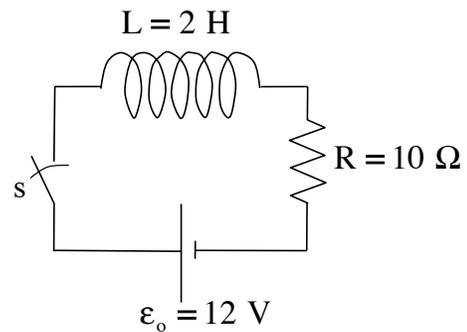
$$\begin{aligned}t &= -\left(\frac{L}{R}\right) \ln\left(1 - \frac{i(t)}{i_o}\right) \\ \Rightarrow t &= -\left(\frac{2 \text{ H}}{10 \Omega}\right) \ln(1 - .9) \\ &= .461 \text{ sec}\end{aligned}$$



2.)