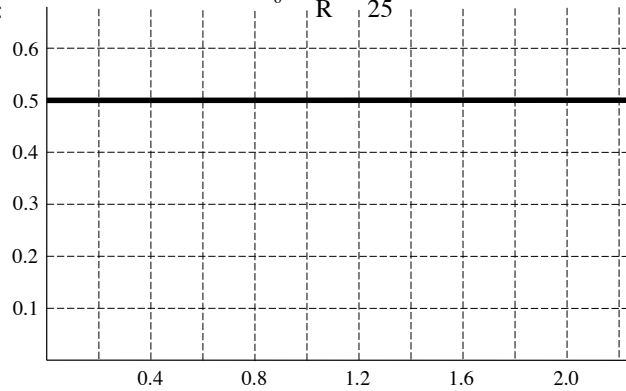


Problem 32.16

If the switch is thrown at $t = 0$, what does the *current versus time* graph look like for:

a.) $L = 0$ (i.e., the circuit with only the resistor in it)?

In this case, the current will jump to its maximum value essentially immediately. As $i_0 = \frac{\epsilon_0}{R} = \frac{12}{25} = .5\text{A}$, we get:




1.)

With inductance in the circuit:

$$i(t) = i_0(1 - e^{-t/\tau}) = i_0(1 - e^{-t(R/L)})$$

b.) $L = \text{large}$ (i.e., longer time constant, say "10" for example):
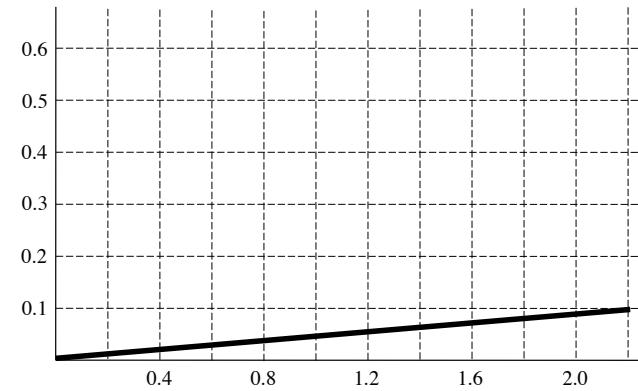
$$i(t) = \frac{\epsilon}{R}(1 - e^{-t/10}) = .5(1 - e^{-1t})$$




3.)

With inductance in the circuit:

$$i(t) = i_0(1 - e^{-t/\tau}) = i_0(1 - e^{-t(R/L)})$$

b.) $L = \text{small}$ (i.e., small time constant, say "1" for example):
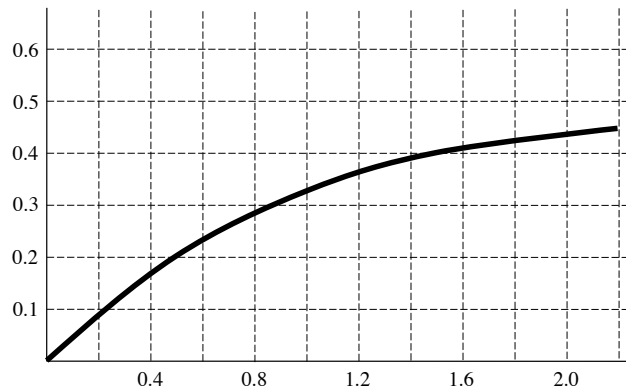
$$i(t) = \frac{\epsilon}{R}(1 - e^{-t/1}) = .5(1 - e^{-t})$$



2.)