

Chapter 8: Capacitance

by Hadi Ammar

**Background/summary:**

Understanding capacitors and capacitance is foundational. This review covers how capacitors store and release electrical energy and how this process is measured. Hint: capacitance measures a capacitor's ability to store charge per unit voltage. This unit helps us understand its applications in circuits.

**Capacitance Formulae**

$\Delta V = Q/C$ , can be written as  $C = Q/\Delta V$

$$C = k \frac{\epsilon_0 A}{d}$$


A = area of one plate, d = the distance between each plate

$C_p = \sum C_i$ , when in parallel, the total Capacitance is the sum of each Capacitor's capacitance


$1/C_s = \sum 1/C_i$ , when in series, the total Capacitance = 1/ the sum of each Capacitor's capacitance

**Symbol for a capacitor in Circuit**

Series Capacitors

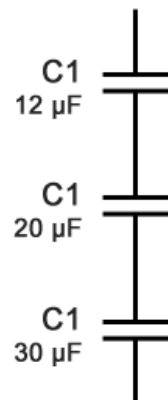

Parallel Capacitors

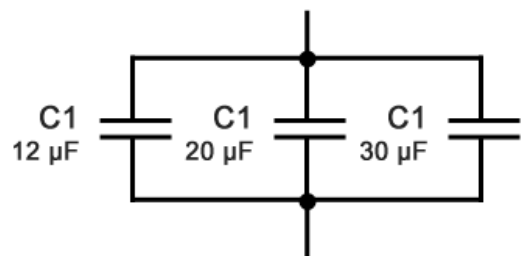


**Wait, but what even is a capacitor?**

A capacitor, in simple terms, is quite literally two metal plates placed close to each other with a bit of insulation between them

When connected to a battery, one plate becomes positively charged and the other negatively charged, creating an electrical potential difference ( $\Delta V$ ) between them. This setup allows the capacitor to store electrical energy, which can be released later for various applications in circuits.
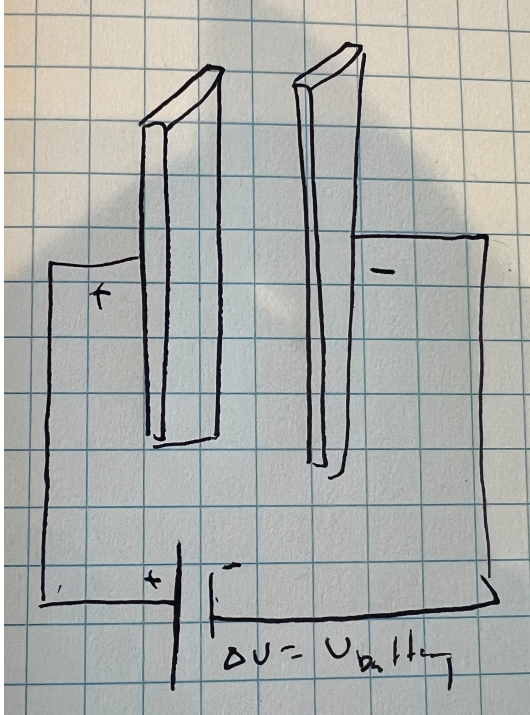
## Did you say Insulator? What? Why?

Unfortunately, yes. Usually, the “insulator” between the two plates is just air, in which case it will look like this.




**Based off of all of this, How can we increase capacitance?**

- 1) Use a dielectric
- 2) Decrease the **d** (bring the plates closer together)
- 3) Increase the **A** (Area of the plates)

$$C = k \frac{\epsilon_0 A}{d}$$


Sometimes though the AP folks use something called dielectrics. Due to the electric field between the capacitors, these dielectrics feel a Van der Waal effect which induces a reverse electric field that lowers the net electric field across the plates. Why is this important? Well, if you remember our equation  $C = Q/\Delta V$ , when the  $\Delta V$  goes down as a result of the decreasing E-field, the capacitance actually increases!

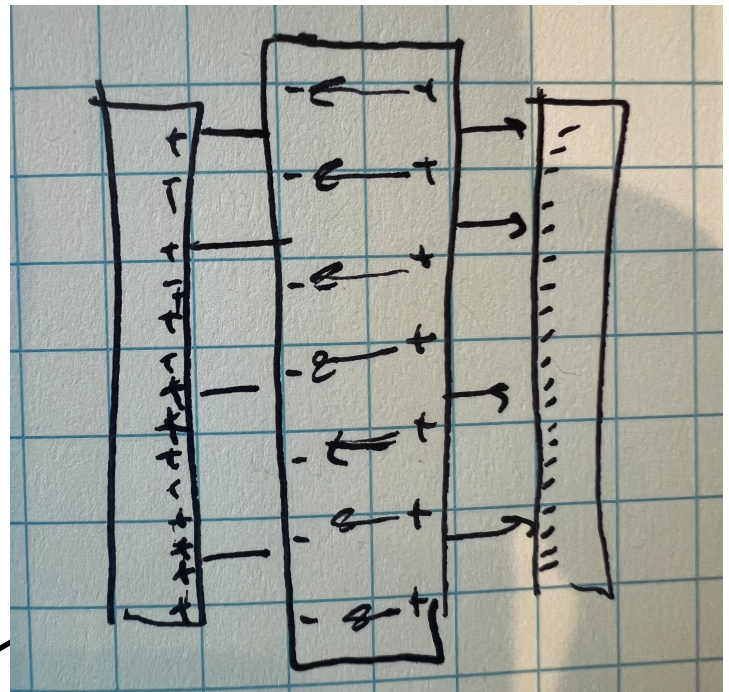Here's what this looks like, thanks to Fletch for these sketches...


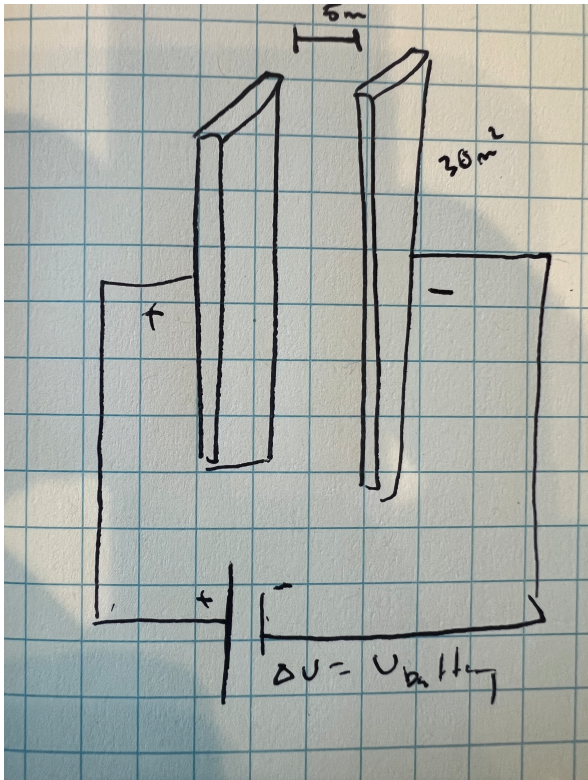
## Lets Do Some Problems!

**Level 1 (Easy):** Find the capacitance of a resistor with an plate area of  $30 \text{ m}^2$  and  $5 \text{ m}$  between each plate




$$C = k \frac{\epsilon_0 A}{d}$$


$$C = (9 \times 10^9) \frac{(8.85 \times 10^{-12})(30)}{5}$$

$$c = \underline{4.779e - 19}$$

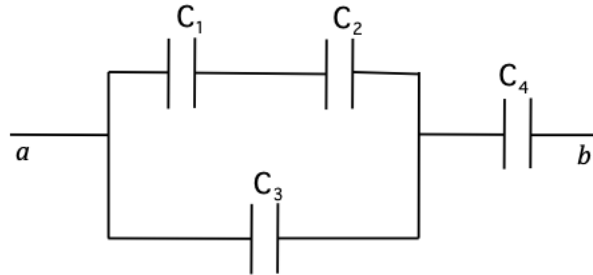**Level 2 (Medium):** Find the equivalent capacitance for this circuit if  $C_1 = 15.0 \mu\text{F}$ ,  $C_2 = 3.00 \mu\text{F}$ ,  $C_3 = 6.00 \mu\text{F}$  and  $C_4 = 20.0 \mu\text{F}$



Step 1, simplify the circuit

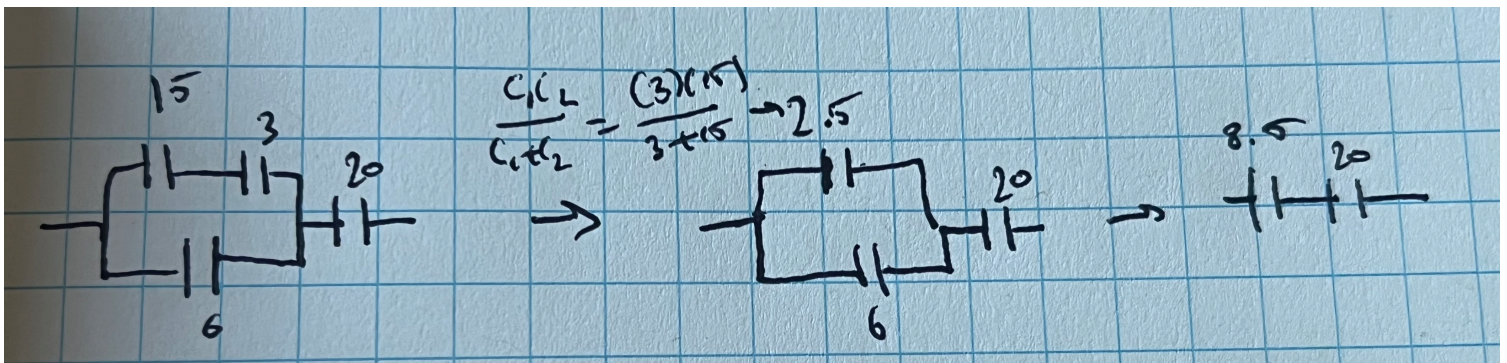

Now that you are left with 2 capacitors in series employ the series equation



$$C_{\text{equ}} = \frac{C_{8.5} C_{20}}{C_{8.5} + C_{20}} = \frac{8.5(20)}{8.5 + 20} = 5.96 \times 10^{-6} \text{ F}$$

**Level 3 (Hard):** Derive an expression for the capacitance of concentric spherical shells of inside radius  $a$  and

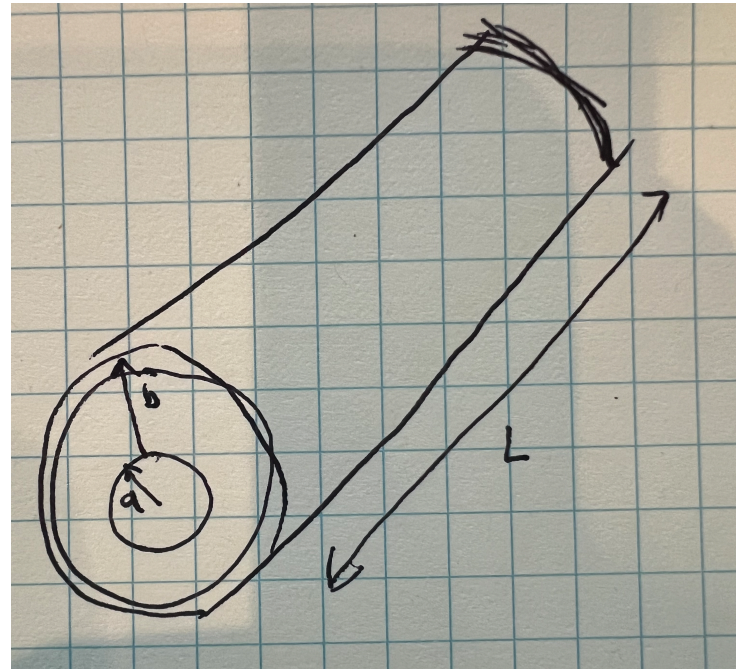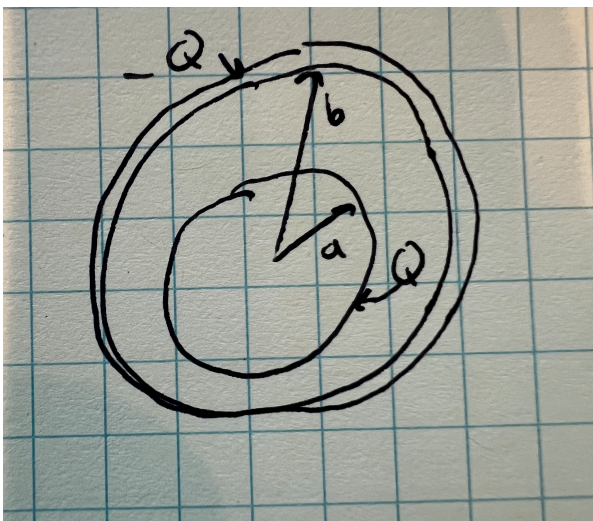**Solution:**

Apparently, capacitors come in all shapes and sizes, let's get started

Step 1: assume that the charges on both shells are  $Q$



Step 3: find the Capacitance using the definition of capacitance.

$$C = \frac{(Q_{\text{on 1 shell}})}{(V_{\text{across shells}})}$$

$$= \frac{Q}{\frac{Q}{4\pi\epsilon_0} \left(\frac{b-a}{ab}\right)}$$

$$= \frac{4\pi\epsilon_0(ab)}{(b-a)}$$

Step 2: find the electrical potential ( $\Delta V$ ) between the shells using the fact that we know that  $E = \frac{Q}{4\pi\epsilon_0 r^2}$

$$V_{\text{cap}} = -\Delta V = + \int \vec{E} \cdot d\vec{r}$$

$$= \int_{r=a}^b \left( \frac{Q}{4\pi\epsilon_0 r^2} \hat{r} \right) \cdot (dr \hat{r}) = \frac{Q}{4\pi\epsilon_0} \int_{r=a}^b \frac{1}{r^2} dr \cos 0^\circ$$

$$= \frac{Q}{4\pi\epsilon_0} \left( -\frac{1}{r} \right) \Big|_{r=a}^b = \frac{Q}{4\pi\epsilon_0} \left[ \left( -\frac{1}{b} \right) - \left( -\frac{1}{a} \right) \right] = \frac{Q}{4\pi\epsilon_0} \left( \frac{b-a}{ab} \right)$$